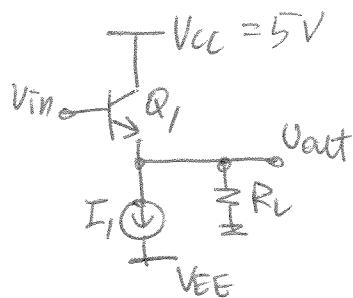


$$1. \quad Av = \frac{g_{m1} R_L}{1 + g_{m1} R_L}$$

$$(a) \quad 0.8 = \frac{g_{m1} (8\Omega)}{1 + g_{m1} (8\Omega)}$$

$$\Rightarrow g_{m1} = 0.5 = \frac{I_C}{V_T} = \frac{I_1}{V_T}$$

$$\therefore I_1 = 13 \text{ mA}$$



$$P_{LOAD} = 0.5 \text{ W}$$

$$R_L = 8\Omega$$

(Assume Vout
biased at
 $V_{BE(on)} \approx 800 \text{ mV}$)

(b) When $V_{in} = V_p = V_{cc}$, $V_{out} \approx V_{cc} - V_{BE(on)}$

$$I_{C1} = I_1 + \frac{V_{out}}{R_L} \Rightarrow I_{C1} = I_1 + \frac{5 - 0.8}{8} \approx 0.54 \text{ A}$$

$$\Rightarrow g_{m1} = \frac{I_{C1}}{V_T} = \frac{0.54 \text{ A}}{0.026 \text{ V}} = 20.8 \text{ S}$$


$$\Rightarrow Av \Big|_{V_{in}=V_p} = \frac{g_{m1} R_L}{1 + g_{m1} R_L} = \frac{(20.8 \text{ S})(8\Omega)}{1 + (20.8 \text{ S})(8\Omega)} \approx 0.99$$

2.

$$(a) \quad I_I = V_P / R_L \quad V_P \gg V_T$$

$$A_V = \frac{I_C R_L}{I_C R_L + V_T}$$
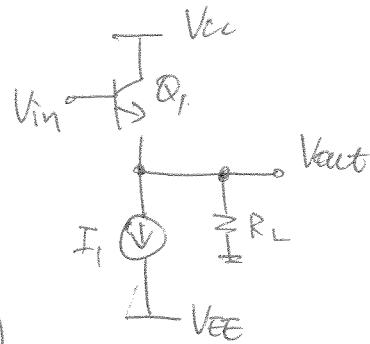
$$= \frac{\frac{I_C}{I_I} V_P}{\frac{I_C}{I_I} V_P + V_T} = \frac{V_P}{V_P + V_T} \quad (\approx 1)$$



$$(b) \text{ When } V_{out} = V_P, \quad I_{C_1} = I_I + \frac{V_{out}}{R_L} = \frac{V_P}{R_L} + \frac{V_P}{R_L}$$

$$= \frac{2V_P}{R_L}$$


$$\therefore A_V = \frac{\left(\frac{2V_P}{R_L}\right) R_L}{\left(\frac{2V_P}{R_L}\right) R_L + V_T} = \frac{2V_P}{2V_P + V_T} \quad \left(\approx \frac{2V_P}{2V_P} = 1. \right)$$

$$\Delta A_V = \frac{\frac{2V_P}{2V_P + V_T} - \frac{V_P}{V_P + V_T}}{\frac{V_P}{V_P + V_T}} = \frac{V_T}{2V_P + V_T} \quad \left(\approx \frac{V_T}{V_P} \right)$$

$$3. A_V = 0.7 \quad R_L = 4\Omega$$

Q_1 shuts off when:

$$I_I = \frac{V_P}{R_L}$$

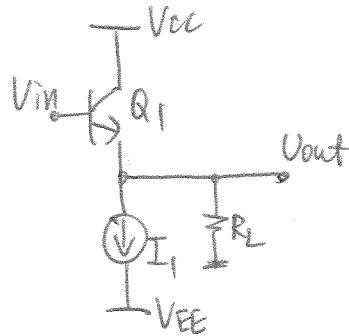

- Suppose $V_{out} = V_P \sin \omega t$. ($\omega = \frac{2\pi}{T}$)

$$P_{RL, AVG} = \frac{1}{T} \int_0^T \frac{(V_{out})^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_P^2 \sin^2 \omega t}{R_L} dt.$$

$$\therefore \text{Largest power (average)} = \frac{1}{2} \frac{(I_I R_L)^2}{R_L} = \frac{1}{2} \frac{V_P^2}{R_L}$$


$$A_V = 0.7 = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \Rightarrow g_{m1} = \frac{A_V}{(1 - A_V) R_L} = \frac{0.7}{(1 - 0.7)(4)} = 0.58 S$$

$$\Rightarrow I_{C1} (= I_I) = g_{m1} V_T = 0.015 A$$

$$\therefore P_{AV, MAX} = \frac{1}{2} I_I^2 R_L = \frac{1}{2} (0.015 A)^2 (4 \Omega) = 0.45 W$$

$$4. A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L}$$

$$(g_m = \frac{I_C}{V_T})$$

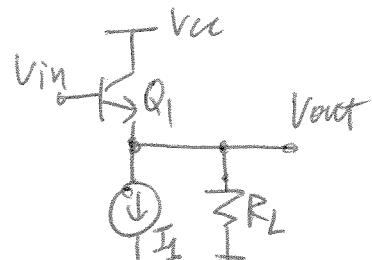

- Q_1 shuts off when $I_1 = -\frac{V_{out}}{R_L}$

$$\Rightarrow V_p = I_1 \times R_L$$

$$g_{m1} = \frac{A_v}{(1-A_v)R_L} = \frac{I_{C1}}{V_T} \Rightarrow I_{C1} = \frac{V_T A_v}{R_L (1-A_v)} (= I_1)$$

- Power delivered to R_L :

$$\begin{aligned} P_{R_L} &= \frac{1}{T} \int_0^T \frac{V_{out}^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_p^2 \sin^2 \omega t}{R_L} dt \\ &= \frac{1}{2} \frac{V_p^2}{R_L} \end{aligned}$$

$$\begin{aligned} \therefore \text{Maximum power} &= \frac{1}{2} \left(\frac{I_1 R_L}{R_L} \right)^2 \\ &= \frac{1}{2} \left[\frac{V_T A_v}{(1-A_v)} \right]^2 \cdot \frac{1}{R_L} \end{aligned}$$

5.

(a) By KCL,

$$I_1 = I_{S1} \cdot \exp\left(\frac{V_{in}-V_{out}}{V_T}\right) + \frac{V_{cc}-V_{out}}{R_L}$$


$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(\frac{I_1}{I_{S1}} - \frac{V_{cc}-V_{out}}{I_{S1} R_L}\right)$$

$$= 0 \quad (\text{X}) - \text{no solution}$$

$$\therefore V_{out} = 5 - I_1 R_L = 4.84 \text{ V}$$

(i.e. Q_1 is off.)

Assume $V_{cc} = 5 \text{ V}$

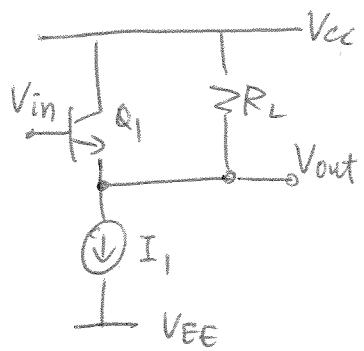

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

$$I_1 = 20 \text{ mA}$$

$$(b) (0.01)I_1 = I_1 - \frac{V_{cc}-V_{out}}{R_L}$$

$$\Rightarrow V_{out} = 4.84 \text{ V}$$

$$I_{C1} = (0.01)I_1 = I_{S1} \exp\left(\frac{V_{in}-V_{out}}{V_T}\right)$$

$$\begin{aligned} \Rightarrow V_{in} &= V_{out} + V_T \ln\left(0.01 \frac{I_1}{I_{S1}}\right) \\ &= 4.84 + (0.026) \ln\left(0.01 \frac{20 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right) \\ &\approx 5.59 \text{ V} \\ &\text{(exceeds } V_{cc} \text{)} \end{aligned}$$

b.

(a) Calculate V_{BE} for

$$\underline{V_{in} = 1 \text{ V}}$$

$$I_{C_1} = I_1 + \frac{V_{out}}{R_L}$$

$$\Rightarrow I_{S1} \cdot \exp\left(\frac{V_{in}-V_{out}}{V_T}\right) = I_1 + \frac{V_{out}}{R_L}$$

Solving for V_{out} gives:

$$V_{out} \approx 0.113 \text{ V}$$



$$\therefore V_{BE} \Big|_{V_{in}=1 \text{ V}} = V_{in} - V_{out} = 1 - 0.113 \\ = 0.887 \text{ V}$$

$$\underline{V_{in} = -1 \text{ V}}$$

$$I_{C_1} = I_1 + -\frac{V_{out}}{R_L} \Rightarrow I_{S1} \exp\left(\frac{V_{in}-V_{out}}{V_T}\right) = I_1 - \frac{V_{out}}{R_L}$$

Solving for V_{out} gives: $V_{out} \approx -1.95 \text{ V}$

$$\therefore V_{BE} \Big|_{V_{in}=-1 \text{ V}} = V_{in} - V_{out} = -1 - (-1.95 \text{ V}) = 0.95 \text{ V}$$

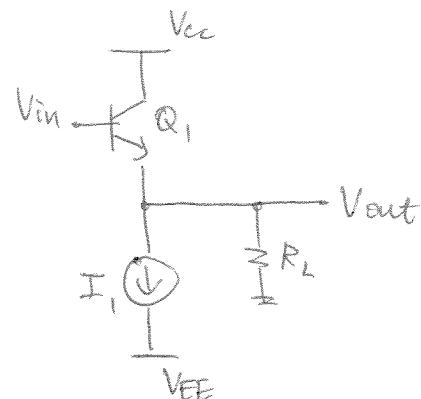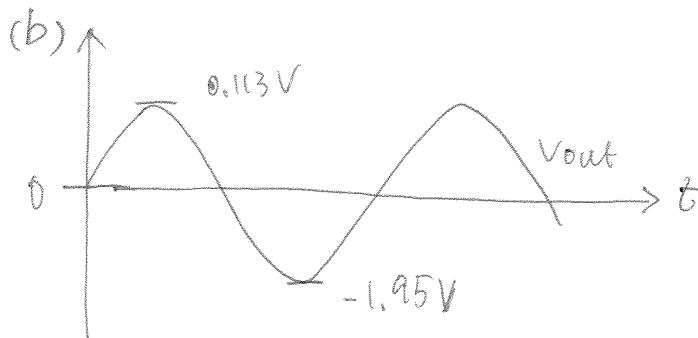

$$I_{S1} = 6 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

$$I_1 = 25 \text{ mA}$$

$$V_p = 1 \text{ V}$$

7. Determine V_p such that

$$V_{BE} \Big|_{V_{in}=+V_p} - V_{BE} \Big|_{V_{in}=-V_p} = 10 \text{ mV}$$

$$\Rightarrow (V_p^+ - V_{out,+}) - (V_p^- - V_{out,-}) = 10 \text{ mV}$$

$$I_S \exp\left(\frac{V_p^+ - V_{out,+}}{V_T}\right) = I_1 + \frac{V_{out,+}}{R_L} \quad \text{--- ①}$$


$$I_S \exp\left(\frac{V_p^- - V_{out,-}}{V_T}\right) = I_1 - \frac{V_{out,-}}{R_L} \quad \text{--- ②}$$

Iterate ① & ②. This gives:

$$V_p \approx 0.7 \text{ V}$$

$$\Rightarrow \text{Nonlinearity} = \frac{10 \text{ mV}}{0.7 \times 2} = 0.007.$$

8.

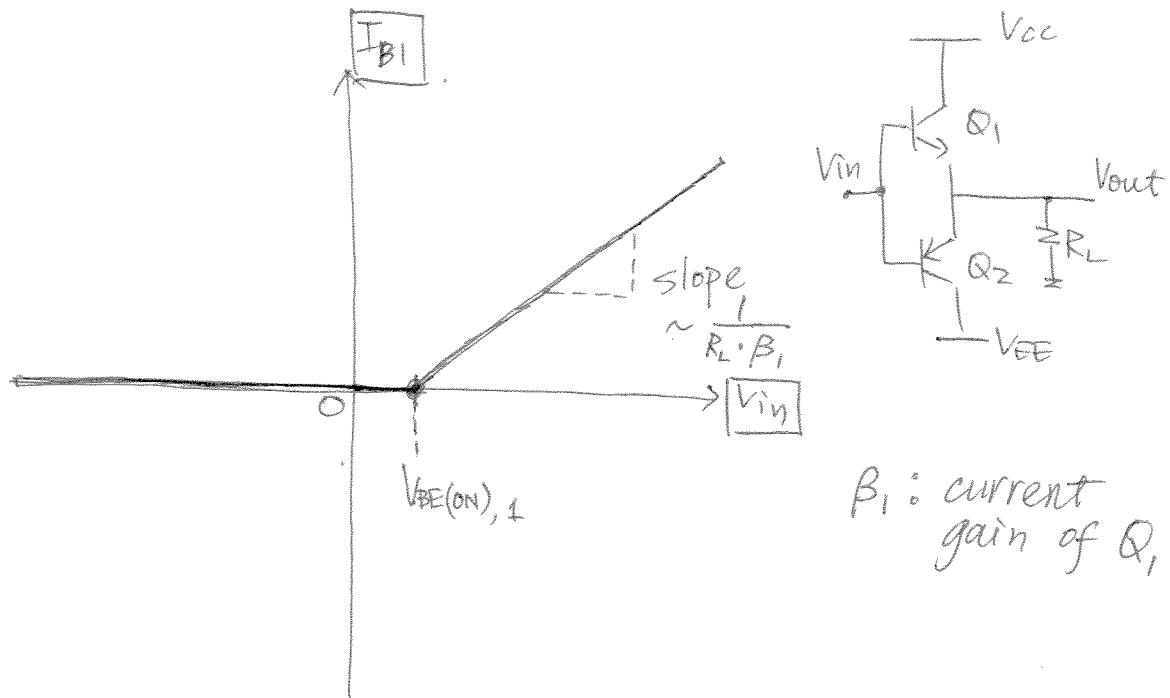

β_1 : current gain of Q_1

- Q_1 is on whenever $V_{in} \geq V_{BE(ON),1}$. In this region,

$$V_{out} = V_{in} - V_{BE(ON),1} \quad I_{C1} = \frac{V_{out}}{R_L}$$

$$\therefore I_{B1} = \frac{I_{C1}}{\beta} = \frac{V_{out}}{\beta R_L} = \frac{V_{in} - V_{BE(ON),1}}{\beta R_L}$$

9.

(a) To guarantee Q_1 on,


- $V_{out} \approx V_{in} - V_{BE(ON)_1}$
 $= -800 \text{ mV}$

$$\Rightarrow I_{C1} = I_i + \frac{V_{out}}{R_L} \quad (Q_2 \text{ is off})$$

- $I_{C1} \geq 0 \Rightarrow I_i + \frac{V_{out}}{R_L} \geq 0$

$$\Rightarrow I_i + \frac{-800 \text{ mV}}{R_L} \geq 0$$
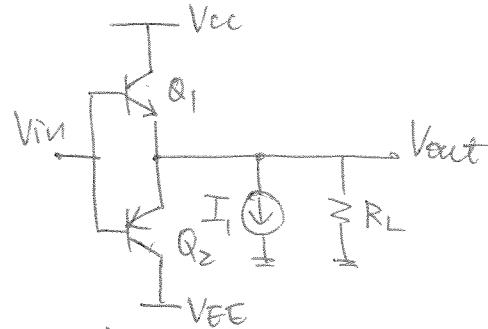
$$\therefore I_i R_L \geq 800 \text{ mV}$$



$$I_{S2} = 6 \cdot 10^{-7} \text{ A}$$

$$R_L = 8 \Omega$$

(b) When Q_2 turns on,

$$-\frac{V_{out}}{R_L} - I_i = I_{C2}$$

$$\Rightarrow -\frac{V_{out}}{R_L} - \left(\frac{800 \text{ mV}}{R_L} \right) = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$$

$$\begin{aligned} \Rightarrow V_{out} &= -R_L I_{S2} \cdot \exp\left(\frac{V_{BE2}}{V_T}\right) - 0.8 \\ &= -(8\Omega)(6 \cdot 10^{-7} \text{ A}) \exp\left(\frac{0.8}{0.026}\right) - 0.8 \\ &\approx -0.81 \text{ V} \end{aligned}$$

$$\therefore V_{in} = V_{out} - |V_{BE(ON)_2}| = -0.81 - 0.8 = -1.61 \text{ V}$$


10. Consider two scenarios :

- In gain regions ($|V_{in}| \geq |V_{BE(on)}|$), V_{out} tracks V_{in} .

- In dead zone, both transistors shut off.

In both cases, V_{out} has an important role.

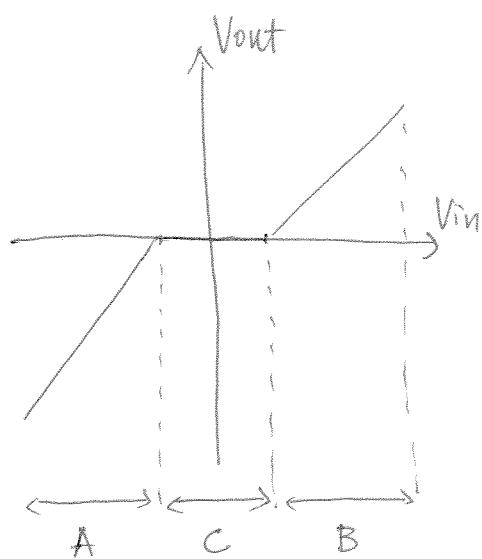Current source I_1 affects the input/output characteristic by modulating V_{out} :



I/O characteristic
of Push-pull stage.

Consider region A :

$$I_{C2} + I_1 = -\frac{V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE2}| = |V_{out} - V_{in}|$ stays relatively constant.

(Q_2 absorbs/sinks all the currents from I_1 in order to have the same $|V_{BE2}|$)

Consider region B :

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE1}| = |V_{in} - V_{out}|$ stays relatively constant.

(Q_1 provides/sources current to I_1 in order to have $|V_{BE1}|$ constant.)

Consider region C: (Dead zone).

$$I_L = -\frac{V_{out}}{R_L} \quad (\text{Both transistors off})$$



$$\therefore I_L \uparrow \Rightarrow V_{out} \downarrow$$

$$I_L \downarrow \Rightarrow V_{out} \uparrow$$

i.e. In the dead zone, V_{out} is predominantly controlled by I_L . One can use this to control V_{out} and effectively shift the region of dead zone.

($\because V_{out}|_{V_{in}=0} \neq 0$ anymore)

11.

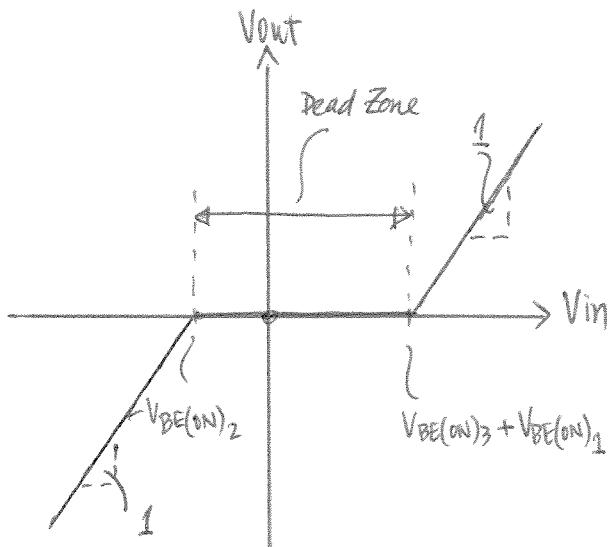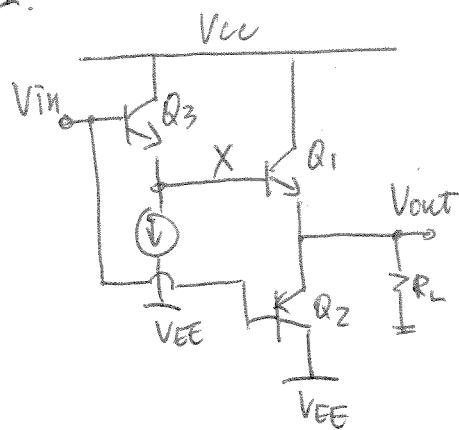



Analysis

Dead Zone

$$= |V_{BE(ON)}_2| + V_{BE(ON)}_3 + V_{BE(ON)}_1$$

- $(0 < V_{in} < V_{BE(ON)}_3 + V_{BE(ON)}_1)$:
 - Q_1 is OFF ($V_{in} < V_{BE(ON)}_1$)
 - Q_2 is OFF (V_{BE_2} reverse-biased) $\Rightarrow V_{out} = 0$
- $(-|V_{BE(ON)}_2| < V_{in} < 0)$:
 - Q_1, Q_2 OFF. $\Rightarrow V_{out} = 0$
- $(V_{BE(ON)}_3 + V_{BE(ON)}_1 < V_{in} < V_{cc})$
 - Q_1 ON
 - Q_2 OFF $\Rightarrow V_{out} = V_{in} - V_{BE(ON)}_3 - V_{BE(ON)}_1$
- $(-|V_{EE}| < V_{in} < -|V_{BE(ON)}_2|)$
 - Q_2 ON
 - Q_1 OFF $\Rightarrow V_{out} = V_{in} + |V_{BE(ON)}_2|$

12.

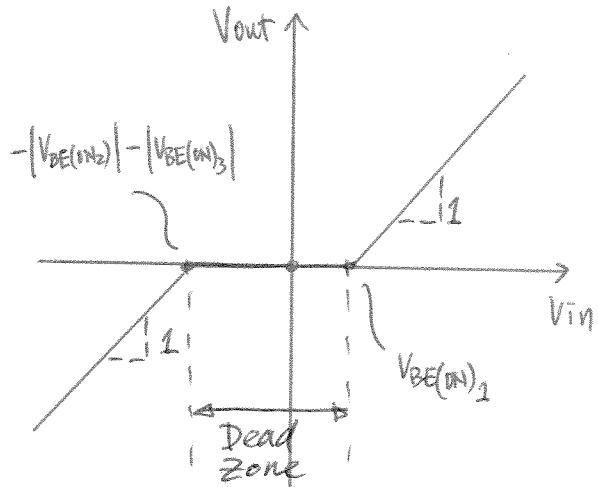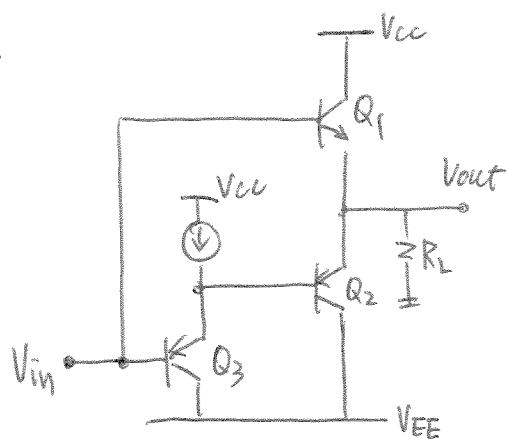

$$-VEE < Vin < -(|V_{BE(on)}_2| + |V_{BE(on)}_3|) :$$

$$\Rightarrow \begin{cases} Q_2, Q_3 \text{ ON} \\ Q_1 \text{ OFF} \end{cases} \quad \left\{ \begin{array}{l} V_{out} = V_{in} + |V_{BE(on)}_3| + |V_{BE(on)}_2| \end{array} \right.$$

$$-(|V_{BE(on)}_2| + |V_{BE(on)}_3|) < Vin < V_{BE(on)}_1 :$$

$$\Rightarrow Q_1, Q_2 \text{ OFF} \Rightarrow V_{out} \approx 0$$

$$V_{BE(on)}_1 < Vin < V_{cc} :$$

$$\Rightarrow \begin{cases} Q_1 \text{ ON} \\ Q_2, Q_3 \text{ OFF} \end{cases} \quad \left\{ \begin{array}{l} V_{out} = V_{in} - V_{BE(on)}_1 \end{array} \right.$$

$$\text{Dead Zone} = V_{BE(on)}_1 + |V_{BE(on)}_2| + |V_{BE(on)}_3|$$

13.

(a)

$$-|V_{EE}| < V_{in} < -|V_{t,p}| :$$

$$\Rightarrow M_1 \text{ OFF } \left\{ \begin{array}{l} V_{out} = V_{in} + V_{SG,2} \\ M_2 \text{ ON} \\ (\text{saturation}) \end{array} \right.$$

$$V_{CC} > V_{in} > V_{t,n} :$$

$$\Rightarrow M_1 \text{ ON } \left\{ \begin{array}{l} V_{out} = V_{in} - V_{GS,1} \\ M_2 \text{ OFF} \end{array} \right.$$



$$-|V_{t,p}| < V_{in} < V_{t,n} :$$

$$M_1, M_2 \text{ OFF} \Rightarrow V_{out} = 0$$

For MOS, $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (|V_{GS}| - |V_t|)^2$ — saturation region.

$$\Rightarrow M_1 \text{ ON: } \frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{t,n})^2, V_{out} > 0$$
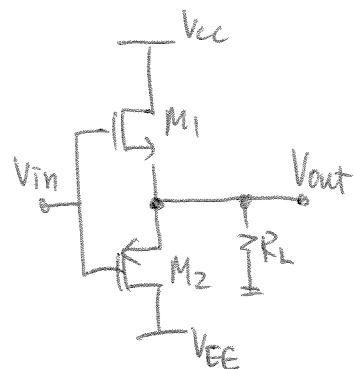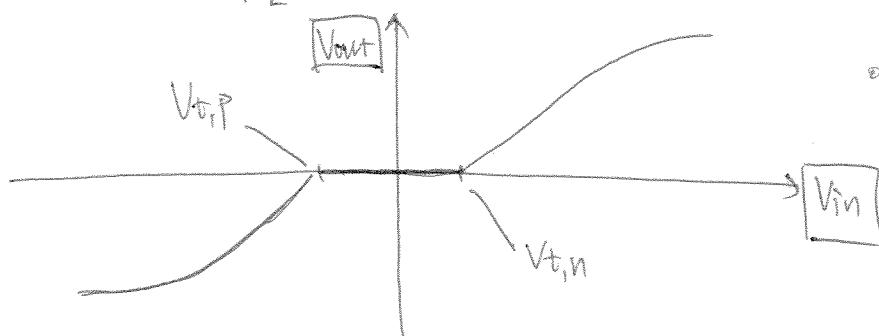
$$M_2 \text{ ON: } -\frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{out} - V_{in} - V_{t,p})^2, V_{out} < 0$$




Ignore body effect.

$\Rightarrow M_1 \text{ & } M_2 \text{ can never be on at the same time.}$

- Solve for V_{out} in both cases.

(b) Outside dead zone
 ⇒ either M_1 or M_2 is on.


• For positive inputs:

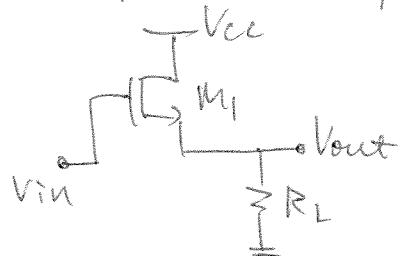

Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{1 + g_{m1} R_L}$$

• For negative inputs:


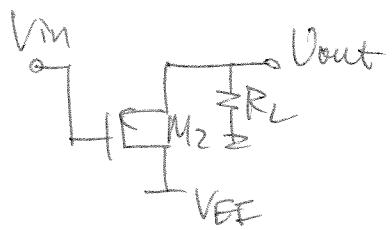


Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m2}}{1 + g_{m2} R_L}$$

14. Dead zone :



$$V_{out} \in [-|V_{BE(ON)}|_2 |, V_{BE(ON)}|_3 + V_{BE(ON)}|]$$

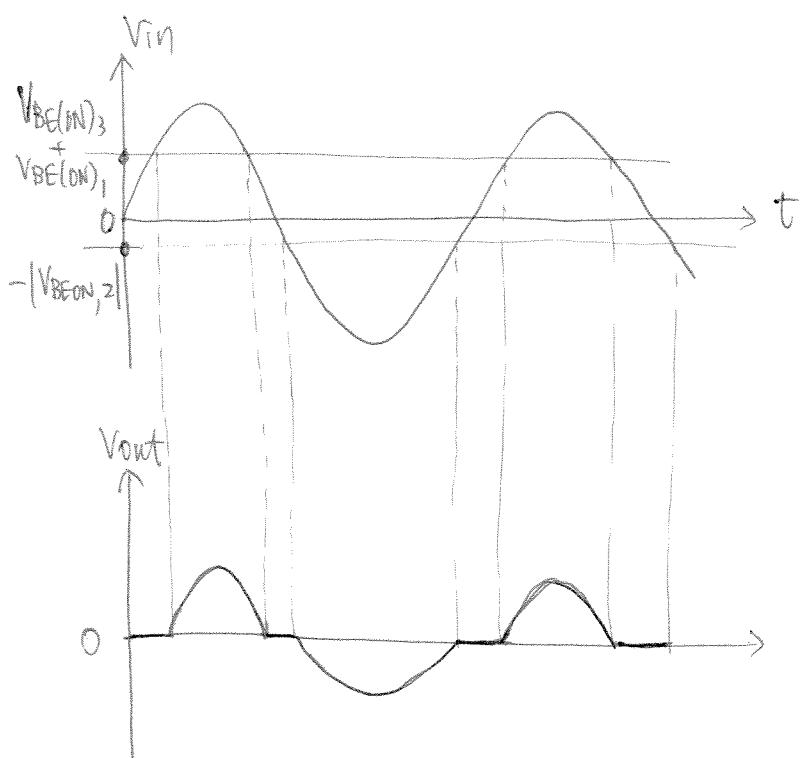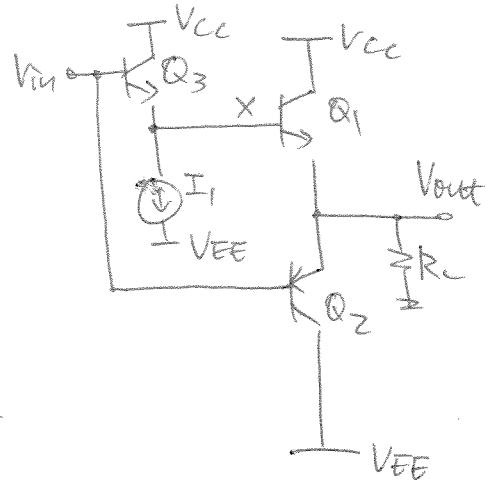

15.



Dead zone:

$$V_{out} \in [-(|V_{BEON_2}| + |V_{BEON_3}|), V_{BEON_1}]$$

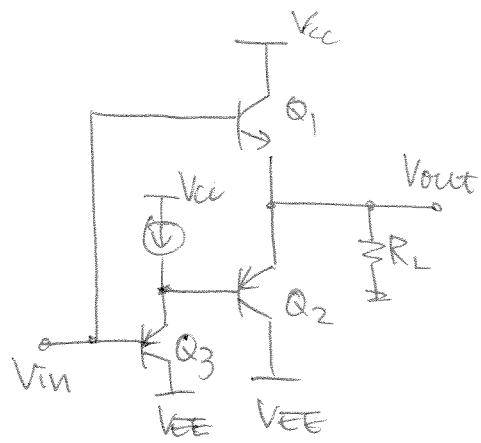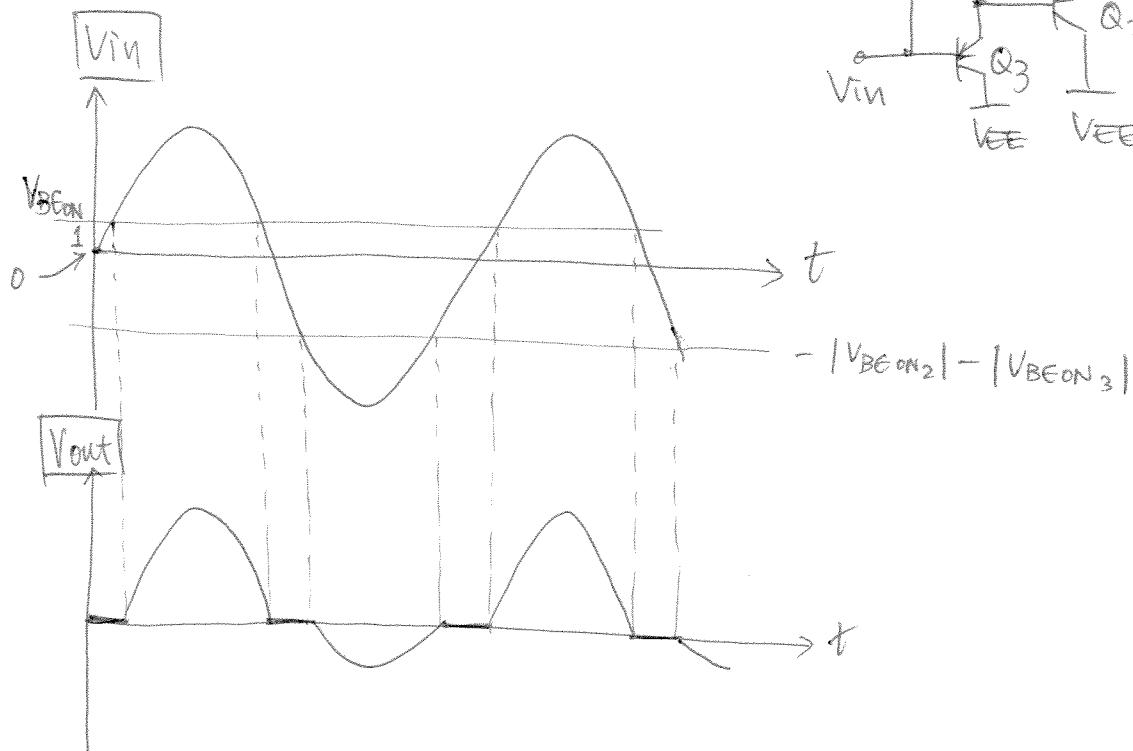


(b.)

(a)

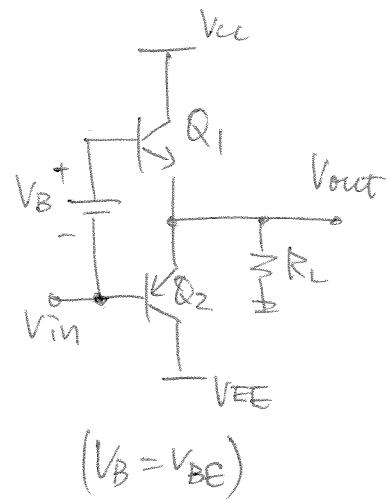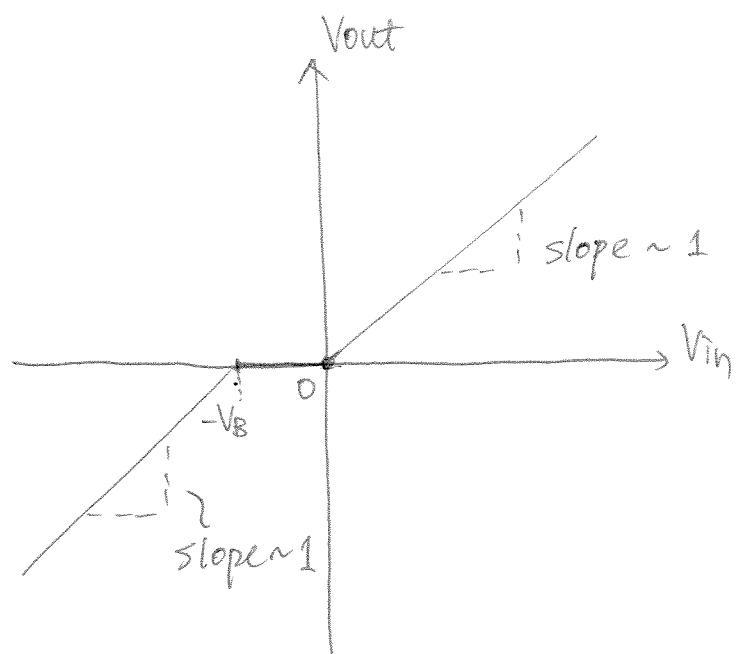

(b)

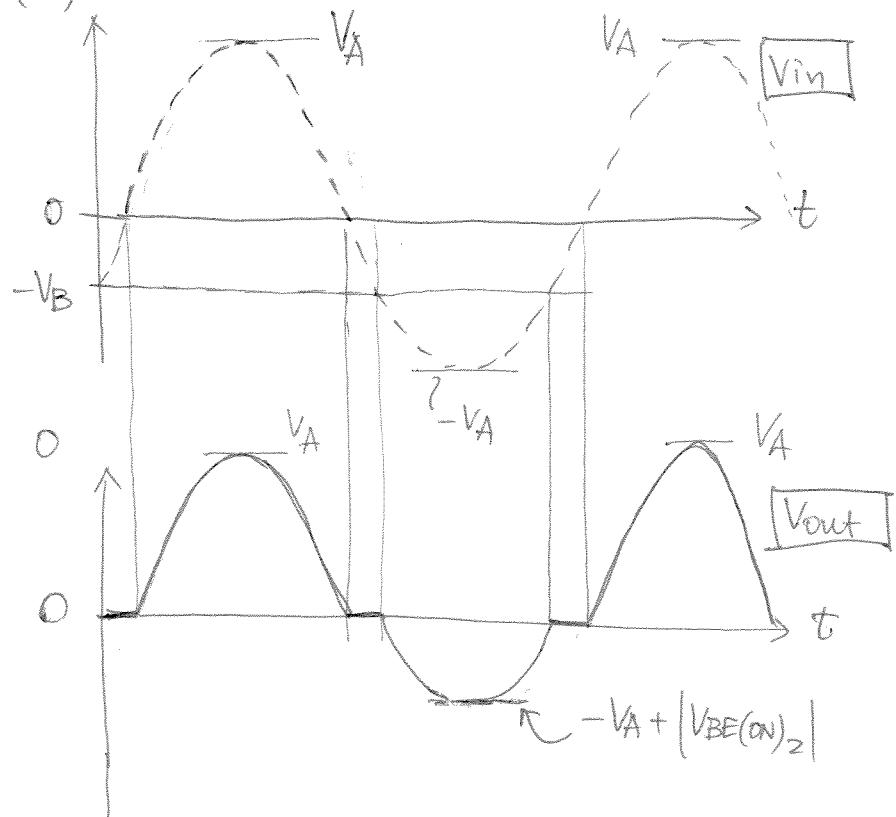


17.

- $V_{out} = 0$:

$$\Rightarrow I_{C_1} = I_{C_2} = I_{BIAS}$$

$$\Rightarrow I_{S_1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = I_{S_2} \exp\left(\frac{|V_{out} - V_{in}|}{V_T}\right)$$

$$\ln\left(\frac{I_{S_1}}{I_{S_2}}\right) + \frac{V_{in} + V_B - V_{out}}{V_T} = \frac{|V_{out} - V_{in}|}{V_T}$$

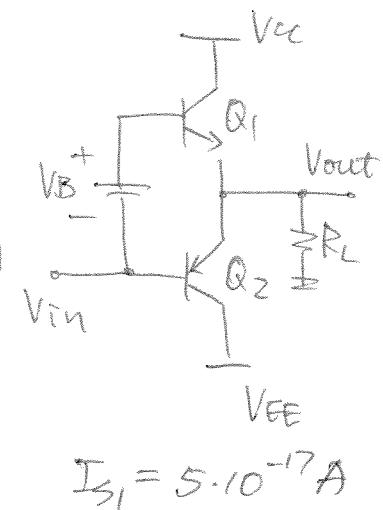

$$I_{S_1} = 5 \cdot 10^{-17} A$$

- For $V_{out} = 0$, $V_T = 0.026 V$:

$$I_{S_2} = 8 \cdot 10^{-17} A$$

$$\Rightarrow \ln\left(\frac{5}{8}\right) + \frac{V_{in} + V_B}{0.026} = + \frac{V_{in}}{0.026}$$

$$I_{BIAS} = 5 \text{ mA}$$

$$(V_{out} = 0)$$

- Given $I_{C_2} = 5 \text{ mA}$

$$\Rightarrow I_{S_2} \exp\left(-\frac{V_{in}}{0.026}\right) = 5 \text{ mA} \Rightarrow V_{in} = -0.83 \text{ V}$$



$$I_{C_1} = I_{S_1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = (5 \cdot 10^{-17} \text{ A}) \exp -\frac{-0.83 + V_B}{V_T}$$

$$\Rightarrow V_B = 0.83 + 0.026 \ln\left(\frac{5 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 6.67 \text{ V.}$$

18.

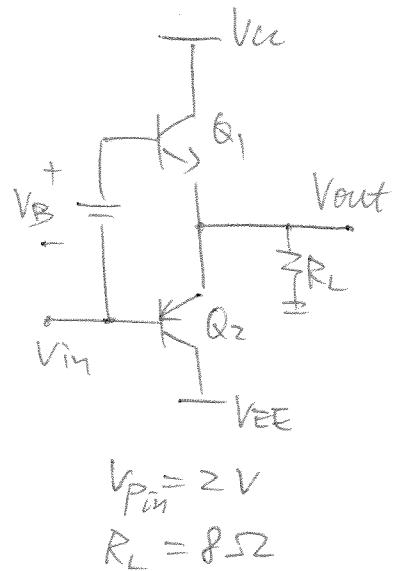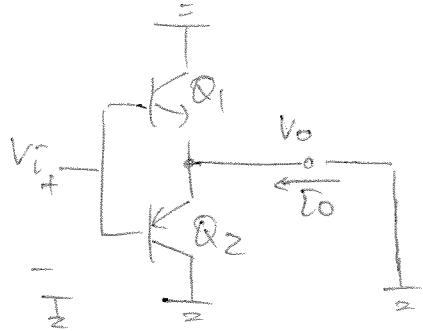(a) Equivalent circuit (small-signal)
around $V_{out} = 0$:



$$\begin{aligned}\hat{I}_o &= -g_{m1} V_i + (-V_i) g_{m2} \\ &= -(g_{m1} + g_{m2}) V_i\end{aligned}$$

$$\therefore G_m = \frac{\hat{I}_o}{V_i} = -(g_{m1} + g_{m2})$$

$$\therefore A_V = \frac{V_o}{V_i} = \frac{\hat{I}_o \times R_L}{V_i} = -(g_{m1} + g_{m2}) R_L$$

$$\begin{aligned}(b) A_V &= -(g_{m1} + g_{m2}) R_L = -\left(\frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T}\right) R_L \\ &= -\left(\frac{5mA}{0.026V} + \frac{5mA}{0.026V}\right)(8\Omega) = -3.08\end{aligned}$$



$$\Rightarrow |V_o|_p = |V_i A_V|_p = |(2V)(-3.08)| = 6.16V$$

(Assume V_{cc} is large enough)

$$(c) \quad I_{C1} = I_{C2} + \frac{V_{out}}{R_L}$$


$$\begin{aligned} I_{C1,peak} &= I_{C2} + \frac{V_P}{R_L} \\ &= 5\text{mA} + \frac{6.16\text{V}}{8\Omega} \\ &= 775\text{mA} \end{aligned}$$

19.

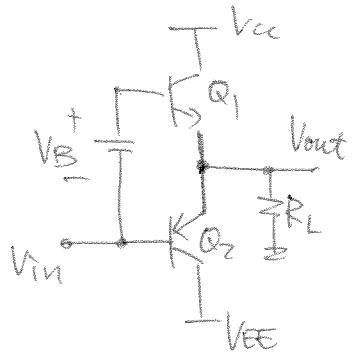
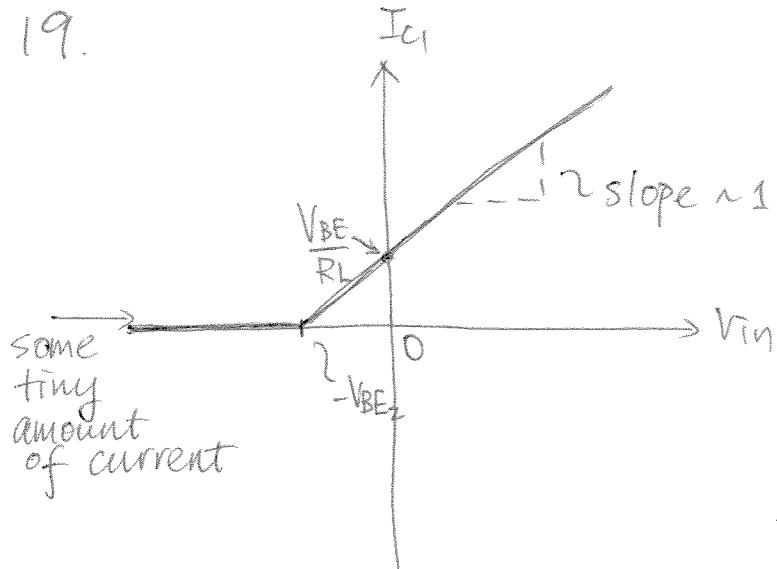


$$V_{out} = V_{in} + |V_{BEz}|$$
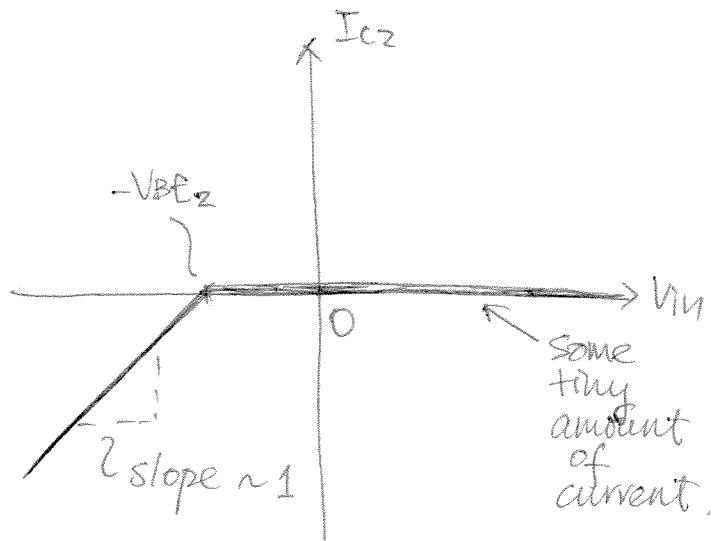
$$\Rightarrow I_{C1} = I_{C2} + \frac{V_{out}}{R_L}$$



20.

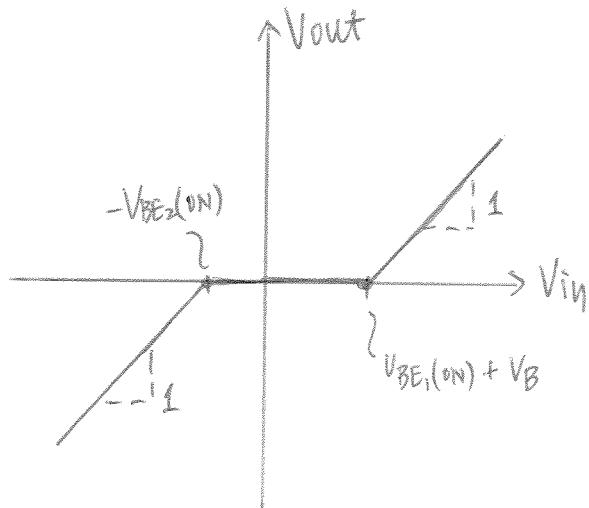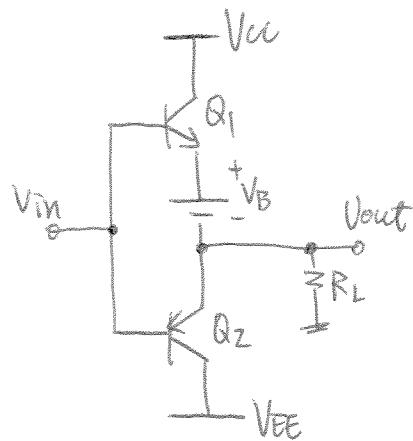

To analyze such circuit, assume $V_{out} = 0$:

$$\Rightarrow -V_{BE2(on)} < V_{in} < V_{BE1(on)} + V_B .$$

$$(V_{BE1(on)} + V_B) < V_{in} : \quad V_{out} = V_{in} - V_{BE1(on)} - V_B$$

$$V_{in} < -V_{BE2(on)} : \quad V_{out} = V_{in} + |V_{BE2(on)}|$$

$$21. V_{BE1} + |V_{BE2}| = V_{D_1} + V_{D_2}$$

$$\Rightarrow V_T \left[\ln \frac{I_Q}{I_{SQ1}} + \ln \frac{I_C2}{I_{SQ2}} \right] = V_T \left[\ln \frac{I_D1}{I_{SD1}} + \ln \frac{I_D2}{I_{SD2}} \right]$$

$$\Rightarrow \frac{I_Q I_C2}{I_{SQ1} I_{SQ2}} = \frac{I_D1 I_D2}{I_{SD1} I_{SD2}}$$

\therefore If $I_{SQ1} I_{SQ2} = I_{SD1} I_{SD2}$,

$$\text{then } I_Q I_C2 = I_D1 I_D2$$

$$22. \quad V_{BE_1} + |V_{BE_2}| = V_{D_1} + V_{D_2}$$

$$\Rightarrow V_T \ln\left(\frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}\right) = V_T \ln\left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}\right)$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{--- } \textcircled{1}$$

$$I_1 = I_{D_1} = I_{D_2} = 1 \text{ mA}; \quad I_{S,Q} = 16 I_{S,D}$$

$$V_{out} = 0 \Rightarrow I_{C1} = I_{C2} \quad \text{--- } \textcircled{2}$$

Substitute all into $\textcircled{1}$:

$$\frac{I_{C1} I_{C1}}{(16 I_{S,D})^2} = \frac{(1 \text{ mA})^2}{(I_{S,D})^2} \Rightarrow I_{C1} = I_{C2} = 16 \text{ mA}$$

$$23. V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{--- } \textcircled{1}$$

$$I_{C1} = I_{C2} = 5 \text{ mA} \quad \text{--- } \textcircled{2}$$

$$I_{S,Q} = 8 I_{S,D} \quad \text{--- } \textcircled{3}$$

Substitute all into ① :

$$\frac{(5 \text{ mA})^2}{(8 I_{S,D})^2} = \frac{I_{D1} I_{D2}}{(I_{S,D})^2} \Rightarrow I_1 = I_D = 0.625 \text{ mA}$$

$$24. V_{BE_1} + |V_{BE_2}| = V_{D_1} + V_{D_2}$$

$$\Rightarrow \frac{I_{C_1} I_{C_2}}{I_{S,Q_1} I_{S,Q_2}} = \frac{I_{D_1} I_{D_2}}{I_{S,D_1} I_{S,D_2}} \quad \text{--- } ①$$

$$I_f = I_D = 2 \text{ mA}$$

$$I_{S,Q_1} = 8 I_{S,D_1} ; \quad I_{S,Q_2} = 16 I_{S,D_2}$$

Substitute all into ① :

$$\frac{I_{C_1} I_{C_2}}{(8 I_{S,D_1})(16 I_{S,D_2})} = \frac{(2 \text{ mA})^2}{I_{S,D_1} I_{S,D_2}}$$

$$\Rightarrow I_{C_1} = I_{C_2} \approx 22.6 \text{ mA}$$

$$25. V_{BE_1} + |V_{BE_2}| = V_{D_1} + V_{D_2}$$

$$\Rightarrow \frac{kT_Q}{q} \left[\ln \left(\frac{I_{C1} I_{C2}}{I_{S1Q_1} I_{S2Q_2}} \right) \right] = \frac{kT_D}{q} \left[\ln \left(\frac{I_{D1} I_{D2}}{I_{S1D_1} I_{S2D_2}} \right) \right]$$

Suppose $T_D = (T_Q + \Delta T)$:

$$\Rightarrow T_Q \left[\ln \frac{I_{C1} I_{C2}}{I_{S1Q_1} I_{S2Q_2}} - \ln \frac{I_{D1} I_{D2}}{I_{S1D_1} I_{S2D_2}} \right] = \Delta T \cdot \ln \frac{I_{D1} I_{D2}}{I_{S1D_1} I_{S2D_2}}$$


$$\Rightarrow I_{C1} I_{C2} = I_{S1Q_1} I_{S2Q_2} \cdot \left(\frac{I_{D1} I_{D2}}{I_{S1D_1} I_{S2D_2}} \right)^{1 + \frac{\Delta T}{T_Q}}$$

Typically, $\frac{I_{D1} I_{D2}}{I_{S1D_1} I_{S2D_2}} > 1$

$$\Rightarrow A \Delta T \text{ introduces a factor } \left(\frac{I_{D1} I_{D2}}{I_{S1D_1} I_{S2D_2}} \right)^{\frac{\Delta T}{T_Q}} < 0,$$

implying that the $I_{C1} I_{C2}$ product drops corresponding to a change (positive) in temperature.


26. Small Signal:

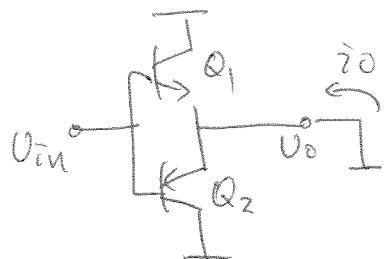

$$g_m = \frac{i_o}{v_{in}} = -(g_{m1} + g_{m2})$$

$$\Rightarrow \frac{v_o}{v_{in}} = \frac{i_o R_L}{v_{in}} = +(g_{m1} + g_{m2}) R_L$$

27. Small-Signal:

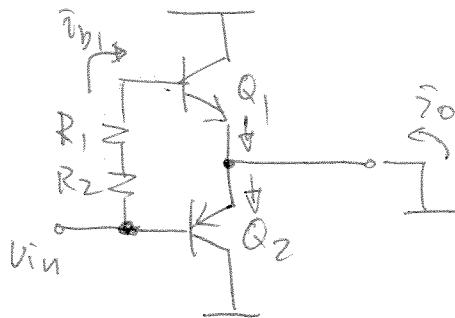

$$\bar{i}_o = -g_{m1}U_{be1} + g_{m2}|U_{be2}| \quad (\bar{i}_o = \bar{i}_{c2} - \bar{i}_{c1})$$

$$|U_{be2}| = V_{in}$$

$$\begin{aligned} U_{be1} &= V_{in} - \bar{i}_{b1}(R_1 + R_2) = V_{in} - \frac{\bar{i}_{c1}}{\beta_1}(R_1 + R_2) \\ &= V_{in} - \frac{\bar{i}_{c2} - \bar{i}_o}{\beta_1}(R_1 + R_2) \\ &= V_{in} + \frac{g_{m2}V_{in} + \bar{i}_o}{\beta_1}(R_1 + R_2) \end{aligned}$$


$$\therefore g_{m1} \left[0 + \frac{g_{m2}V_{in} + \bar{i}_o}{\beta_1}(R_1 + R_2) \right] + \bar{i}_o = -g_{m2}V_{in}$$

Solving for $\frac{\bar{i}_o}{V_{in}}$ gives:

$$g_m = \frac{\bar{i}_o}{V_{in}} = - \frac{\left[g_{m1} + \frac{g_{m1}g_{m2}}{\beta_1}(R_1 + R_2) + g_{m2} \right]}{1 + \frac{g_{m1}(R_1 + R_2)}{\beta_1}}$$

Roact:
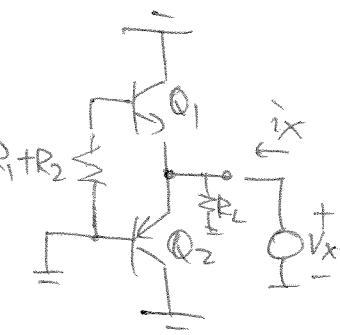
$$\frac{V_x}{i_x} = R_{\text{out}} = \left(R_{\pi_2} \parallel \frac{1}{g_{m_2}} \right) \parallel \left[\left(R_{\pi_1} + R_1 + R_2 \right) \parallel \frac{1}{g_{m_1}} \right] \parallel R_L$$



$$\therefore A_V = G_m R_{\text{out}}$$

$$= - \left[\frac{g_{m_1} + \frac{g_{m_1} g_{m_2} (R_1 + R_2)}{\beta_1} + g_{m_2}}{1 + \frac{g_{m_1} (R_1 + R_2)}{\beta_1}} \right] \cdot \left\{ \left[R_{\pi_2} \parallel \frac{1}{g_{m_2}} \right] \parallel \left[\left(R_{\pi_1} + R_1 + R_2 \right) \parallel \frac{1}{g_{m_1}} \right] \parallel R_L \right\}$$


28. Small signal gain around $V_{out} = 0$:

$$Av = + (g_{m1} + g_{m2}) R_L$$

$$0.8 = (I_{C1} + I_{C2}) \frac{R_L}{V_T}$$


If $I_{C1} = I_{C2} = I_{BIAS}$, then
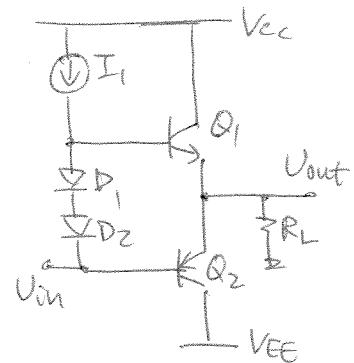
$$I_C = \frac{0.8}{2} \times \frac{V_T}{R_L} = 0.4 \frac{V_T}{R_L} = 0.01 \cdot R_L = 0.08 A$$



$$R_L = 8\Omega$$


29. Small-signal equivalent:

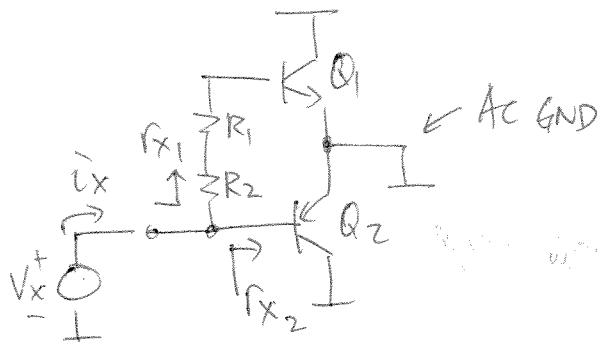

$$R_{in} = \frac{V_x}{i_x} = R_{x_1} \parallel R_{x_2}$$

$$= (R_1 + R_2 + r_{\pi_1}) \parallel r_{\pi_2}$$

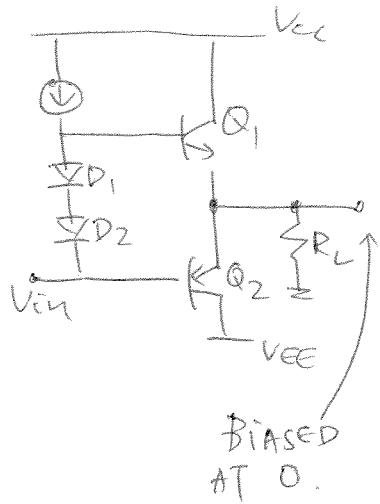- * R_1 & R_2 can be neglected when $r_{\pi_1} \gg (R_1 + R_2)$




$$30. \quad I_{C_1} = I_{C_2} = 10 \text{ mA}$$

$$I_{C_3} = I_{C_4} = 1 \text{ mA}$$


$$\beta_1 = 40 \quad \beta_2 = 20$$

$$R_L = 8 \Omega$$

$$R_{D_1} = R_{D_2} = 0$$

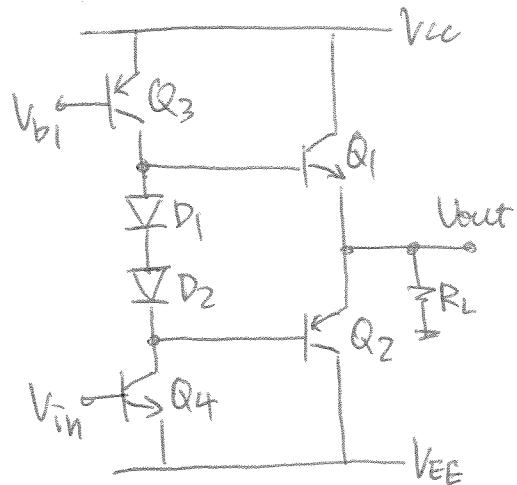

Small-signal

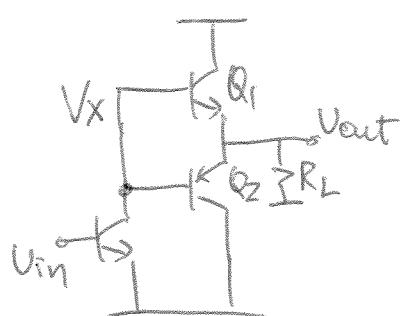

$$A_V = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$

$$= -g_{m4} [(g_{m1} + g_{m2})(r_{\pi_1} \parallel r_{\pi_2})R_L + (r_{\pi_1} \parallel r_{\pi_2})] \times \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$= -g_{m4} (r_{\pi_1} \parallel r_{\pi_2}) (g_{m1} + g_{m2}) R_L$$

$$\therefore A_V = -\frac{I_{C41}}{V_{T1}} \left(\frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} \right) \left(\frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T} \right) R_L$$

$$= -\frac{1 \text{ mA}}{0.026} [35] \cdot \left(2 \times \frac{10 \text{ mA}}{V_T} \right) (8)$$

$$\approx -8.3$$

31.

$$\frac{V_{\text{out}}}{V_{\text{in}}} = -g_{m_4}(\Gamma_{\pi_1} \parallel \Gamma_{\pi_2})(g_{m_1} + g_{m_2})R_L \quad (\Gamma_{\pi} = \frac{\beta}{g_m})$$

When $g_{m_1} \approx g_{m_2}$: ($\Rightarrow \Gamma_{\pi}$

$$\begin{aligned}\frac{V_{\text{out}}}{V_{\text{in}}} &\approx -g_{m_4}R_L(2g_{m_1})\left(\frac{\beta_1}{g_{m_1}} \parallel \frac{\beta_2}{g_{m_1}}\right) \\ &= -g_{m_4}R_L(2g_{m_1})\left[\frac{1}{g_{m_1}} \cdot \frac{\beta_1\beta_2}{\beta_1 + \beta_2}\right] \\ &= -\frac{2\beta_1\beta_2}{\beta_1 + \beta_2} g_{m_4} R_L\end{aligned}$$

32. From lecture, small-signal gain of the output stage is:

$$\left| \frac{V_{out}}{V_{in}} \right| = + g_{m4} \left(R_{\pi_1} / (R_{\pi_2}) \right) (g_{m1} + g_{m2}) R_L$$


$$\approx + g_{m4} R_L \times \frac{2\beta_1 \beta_2}{\beta_1 + \beta_2}$$

$$\Rightarrow A_v = + \frac{I_{C4}}{V_T} (8\Omega) \times \frac{z(40)(20)}{40+20}$$

$$\Rightarrow I_{C4} \approx I_{C3}$$

$$= \frac{4 V_T}{(8\Omega)} \cdot \frac{40+20}{z(40)(20)}$$

$$= 0.49 \text{ mA}$$

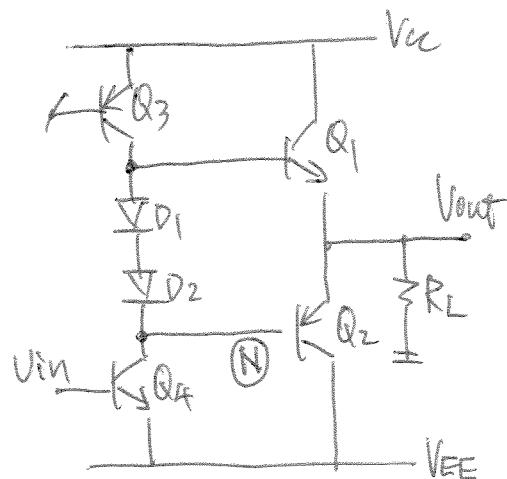

$$A_v = \frac{V_{out}}{V_{in}} = 4$$

$$\beta_1 = 40$$

$$\beta_2 = 20$$


$$R_L = 8\Omega$$

33. From lecture,

$$\frac{U_x}{I_x} = \frac{1}{g_{m_1} + g_{m_2}} + \frac{r_{o3} // r_{o4}}{(g_{m_1} + g_{m_2})(r_{\pi_1} - r_{\pi_2})}$$

If $g_{m_1} \approx g_{m_2} = g_m$:
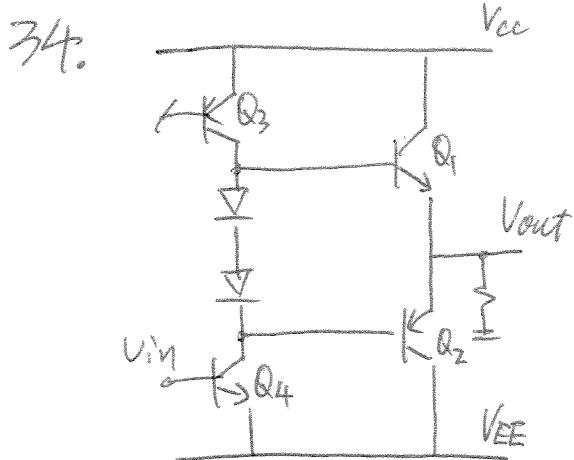
$$\begin{aligned}\frac{U_x}{I_x} &\approx \frac{1}{2g_m} + \frac{r_{o3} // r_{o4}}{2g_m \left(\frac{\beta_1}{g_m} // \frac{\beta_2}{g_m} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} // r_{o4}}{2g_m \left(\frac{1}{g_m} \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} // r_{o4}}{2\beta_1 \beta_2} (\beta_1 + \beta_2)\end{aligned}$$




$$I_3 = I_4 = 1 \text{ mA}$$

$$I_1 = I_2 = 8 \text{ mA}$$

$$V_{A3} = 10 \text{ V}$$

$$V_{A4} = 15 \text{ V}$$

(a) Small-signal equivalent:

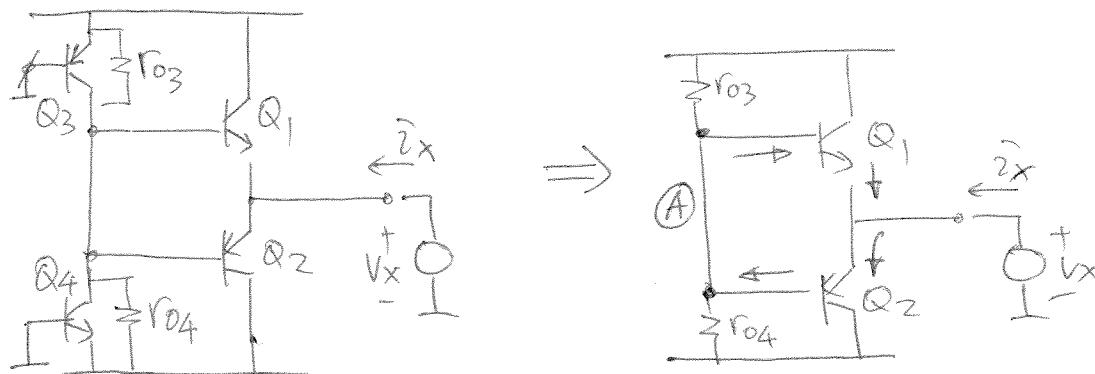

$$v_{eb} = v_x \frac{(r_{\pi_1} \parallel r_{\pi_2})}{(r_{\pi_1} \parallel r_{\pi_2}) + (r_{03} \parallel r_{04})}$$

$$v_{be} = v_A - v_x$$

$$\bar{v}_x + \bar{i}_{c_1} = \bar{i}_{c_2} \Rightarrow \bar{i}_x = \bar{i}_{c_2} - \bar{i}_{c_1} = g_{m_2} v_{eb} - g_{m_1} v_{be}$$

$$\therefore \bar{i}_x = [g_{m_2} + g_{m_1}] v_x \frac{(r_{\pi_1} \parallel r_{\pi_2})}{(r_{\pi_1} \parallel r_{\pi_2}) + (r_{03} \parallel r_{04})}$$

$$\Rightarrow \frac{v_x}{i_x} = R_{out} = \frac{(r_{\pi_1} \parallel r_{\pi_2}) + (r_{03} \parallel r_{04})}{[g_{m_1} + g_{m_2}] (r_{\pi_1} \parallel r_{\pi_2})}$$

$$r_{\pi_1} = \frac{\beta_1 V_T}{I_{C1}} = 130 \Omega$$

$$r_{\pi_2} = \frac{\beta_2 V_T}{I_{C2}} = 65 \Omega$$

$$r_{O3} = \frac{V_{A3}}{I_{C3}} = 10 k\Omega$$

$$r_{O4} = \frac{V_{A4}}{I_{C4}} = 15 k\Omega$$

$$g_{m1} = 0.31 S$$


$$g_{m2} = 0.31 S$$

$$\Rightarrow R_{out} = \frac{43.3 + 6000}{(0.62)(43.3)} \approx 6001 \Omega$$

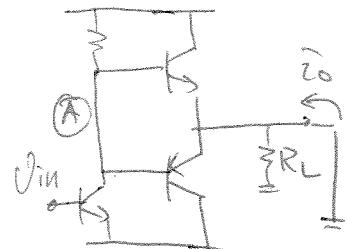(b) Effective $R_{out} = R_{out,a} \parallel 8\Omega \approx 8\Omega$.

$$G_m = \frac{I_o}{V_A} \cdot \frac{V_A}{V_{in}}$$

$$= -g_{m4}(r_{\pi_1} \parallel r_{\pi_2} \parallel r_{O3}) \cdot (g_{m1} + g_{m2})$$



$$\therefore Av = G_m R_{out}$$

$$= -g_{m4}(r_{\pi_1} \parallel r_{\pi_2} \parallel r_{O3})(g_{m1} + g_{m2}) R_{out}$$


$$= -0.038 [130 \parallel 65 \parallel 10k] [0.62] (8)$$

$$\approx -8.1$$

$$g_{m4} = \frac{I_{C4}}{V_T} = 0.038 S$$

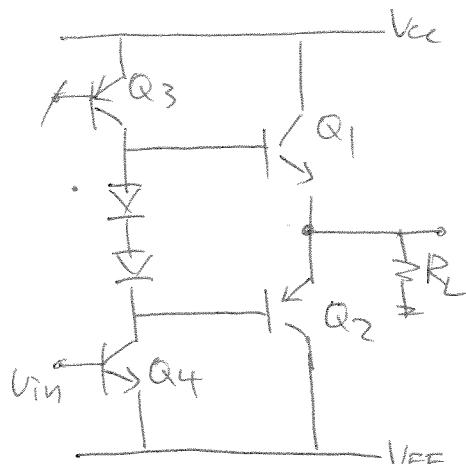35. Max current delivered
 by $Q_1 = I_{C3} \cdot \beta_1 = 1\text{mA} \cdot 40$
 $= 40\text{ mA. } (Q_4 \text{ off})$

Max current delivered
 by $Q_2 = I_{C4} \cdot \beta_2$
 $= 1\text{mA} \cdot 20$
 $= 20\text{ mA. } (Q_3 \text{ off})$



$$I_{C3} = I_{C4} = 1\text{mA}$$

$$\beta_1 = 40 \quad \beta_2 = 20$$

$$36. \quad P = 0.5 \text{ W} \quad R_L = 8 \Omega$$

$$\beta_1 = 40 \quad \beta_2 = 20.$$


$$P_{\text{AVG}} = \frac{1}{2} \frac{V_p^2}{R_L} = 0.5$$

$$\Rightarrow V_p^2 = 2(0.5) R_L$$

$$\Rightarrow V_p = \sqrt{R_L} = \sqrt{2}$$

At positive V_p , $I_{C1} = \frac{V_p}{R_L} = \frac{\sqrt{2}}{8} = 0.35 \text{ A}$.

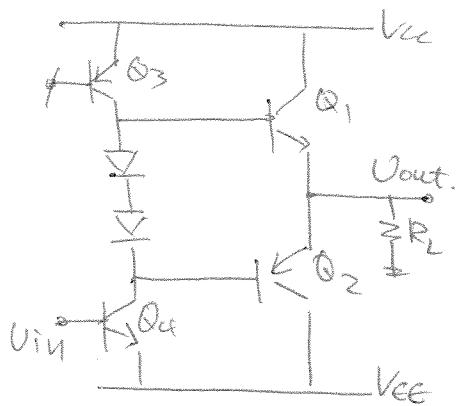At negative V_p , $I_{C2} = \frac{V_p}{R_L} \Rightarrow I_{C2} = 0.35 \text{ A}$.



- At $+V_p$, all of I_{C3} supports the base current of Q_1

$$\Rightarrow I_{C3} = I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{0.35 \text{ A}}{40} = 8.75 \text{ mA}$$

- At $-V_p$, all of I_{C4} supports the base current of Q_2

$$\Rightarrow I_{C4} = I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{0.35 \text{ A}}{20} = 17.5 \text{ mA}$$

$$37. P_{AVG} = 0.5 \text{ W} \quad R_L = 8\Omega$$

$$V_{CC} = 5 \text{ V}$$

$$\Rightarrow 0.5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L}$$

$$\Rightarrow V_p = 2\sqrt{2} \text{ V}$$


$$P_{Q_1} = \frac{1}{T} \int_0^{T/2} I_{C1} V_{CE1} dt$$

$$= \frac{1}{T} \int_0^{T/2} \left(\frac{V_p \sin \omega t}{R_L} \right) \cdot (V_{CC} - V_p \sin \omega t) dt$$

$$= \frac{1}{T} \int_0^{T/2} \left[\frac{V_{CC} V_p}{R_L} \sin \omega t - \frac{V_p^2}{2R_L} \right] dt$$

$$= \frac{V_p}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_p}{4} \right) = \frac{2\sqrt{2}}{8} \left(\frac{5}{\pi} - \frac{2\sqrt{2}}{4} \right)$$

$$\approx 0.31 \text{ W}$$

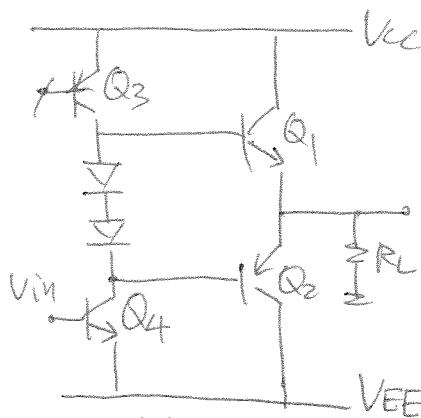


(Assume negligible currents at $V_{out}=0$)

$$38. P_{Q_1, \text{MAX}} = 0.75 \text{W.}$$

$$R_L = 8 \Omega$$

$$V_{CC} = 5 \text{V}$$

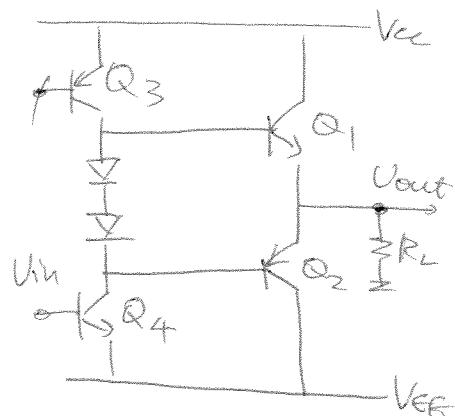- Out of all 4 transistors, Q_1 & Q_2 must sustain the most currents.



$$P_{Q_1, \text{MAX}} = V_{CE} \times I_{C_1, \text{MAX}} = (V_{CC} - V_{out}) I_{C_1, \text{MAX}}$$

$$\begin{aligned} \Rightarrow P_{Q_1, \text{MAX}} &= \frac{1}{T} \int_0^{T/2} \frac{V_P \sin \omega t}{R_L} \cdot (V_{CC} - V_P \sin \omega t) dt \\ &= \frac{1}{T} \int_0^{T/2} \left(\frac{V_{CC} V_P}{R_L} \sin \omega t - \frac{V_P^2}{2 R_L} \right) dt \\ &= \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right) \end{aligned}$$

$$\begin{aligned} \Rightarrow \frac{dP_Q}{dV_P} &= \frac{V_{CC}}{\pi R_L} - \frac{V_P}{2 R_L} \\ &= 0 \quad \text{when } V_P = \frac{2V_{CC}}{\pi} = 3.18 \text{V} \end{aligned}$$

$$P_Q \Big|_{V_P = \frac{2V_{CC}}{\pi}} = 0.32 \text{W}$$

$$\therefore P_{RL, \text{MAX}} = \frac{1}{2} \frac{V_P^2}{R_L} = 0.63 \text{W}$$

$$39. P_{Q_1, \text{MAX}} = \left(\frac{V_{cc}}{\pi} - \frac{2V_{cc}}{4\pi} \right) \cdot \frac{2V_{cc}}{TcR_L} \leq 0.75 \text{ W}$$

$$\Rightarrow V_{cc| \text{max}} = 7.7 \text{ V}$$


$$\Rightarrow V_{P, \text{MAX}} = \frac{2V_{cc \text{ MAX}}}{\pi} = 4.9 \text{ V}$$

$$\Rightarrow P_{R_L \text{ MAX}} = \frac{1}{2} \frac{V_{P \text{ MAX}}^2}{R_L} = 1.5 \text{ W}$$

$$\begin{aligned}
 40. \quad I_I &= I_{C1} + I_{E2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{C2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{B1} \\
 &= \beta_1 I_{B1} + \frac{\beta_1 + 1}{\beta_1} I_{B1}
 \end{aligned}$$

$$\Rightarrow I_{B1} = \frac{I_I}{\beta_1 + \frac{\beta_1 + 1}{\beta_1}} = \frac{0.005}{40 + \frac{41}{40}} \\
 \approx 0.12 \text{ mA}$$
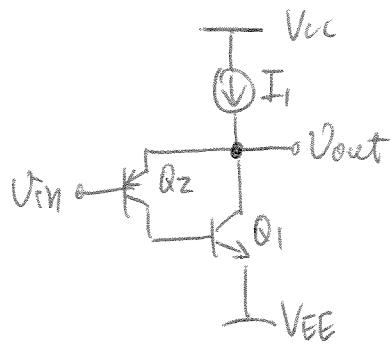
$$\Rightarrow I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{I_{B1}}{\beta_2} = 0.0024 \text{ mA}$$



$$I_I = 5 \text{ mA}$$

$$\beta_1 = 40$$

$$\beta_2 = 50.$$

$$41. \quad V_{in} = 0.5 \text{ V}$$

$$I_{S2} = 6 \cdot 10^{-17} \text{ A.}$$


$$I_{B_1} = I_{C_2} = 0,12 \text{ mA}$$

$$\Rightarrow I_{C2} = I_{S2} \cdot \exp\left(\frac{V_{out} - V_{in}}{V_T}\right)$$


$$\therefore V_{out} = V_T \ln\left(\frac{I_C}{I_S}\right) + V_{in}$$

$$= 0.026 \ln \left(\frac{0.12 \text{ mA}}{6 \cdot 10^{-17} \text{ A}} \right) + 0.5$$

$\approx 1.24 \text{ V}$

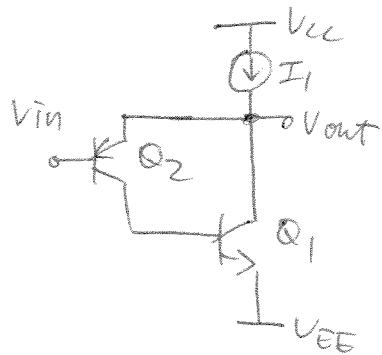

42.

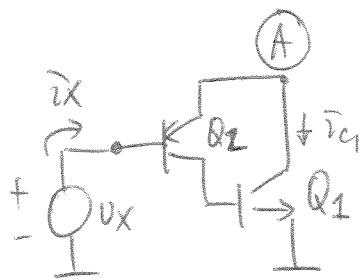

$$\bar{i}_2 = \bar{i}_x \beta_2$$

$$\begin{aligned} \bar{i}_{c1} &= -g_{m2} V_{eb2} = \bar{i}_{e2} = \bar{i}_{c2} + \bar{i}_{b2} \\ &= \bar{i}_x (\beta_2 + 1) \end{aligned}$$


$$V_{eb2} = V_A - V_x$$

$$\text{where } V_A = V_x - \bar{i}_x R_{T2}$$

$$\therefore \bar{i}_b1 = -g_{m2} (\bar{i}_x \cdot R_{T2})$$

$$\bar{i}_{c1} = \bar{i}_{b1} + \bar{i}_{b1} \beta_1 = -g_m \bar{i}_x \cdot R_{T2} (1 + \beta_1)$$
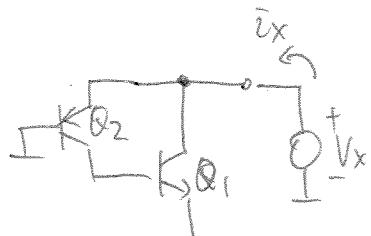
$$\Rightarrow \frac{V_x}{\bar{i}_x} \rightarrow \infty \quad (\text{Rin})$$



$$\begin{aligned} \bar{i}_x &= \bar{i}_{e2} + \bar{i}_{c1} \\ &= \bar{i}_{e2} + \bar{i}_{b1} \beta_1 \\ &= \bar{i}_{e2} + \bar{i}_{c2} \beta_1 \\ &= \bar{i}_{c2} + \bar{i}_{b2} + \bar{i}_{c2} \beta_1 \\ &= \bar{i}_{c2} \left(1 + \beta_1 + \frac{1}{\beta_1}\right) \\ &= V_x g_{m2} \left(1 + \beta_1 + \frac{1}{\beta_1}\right) \end{aligned}$$

$$g_{m2} = \frac{I_B \beta_2}{V_T}$$

$$= 4.6 \text{ S}$$

$$\Rightarrow R_{out} = \frac{V_x}{\bar{i}_x} = \frac{1}{g_{m2} \left(1 + \beta_1 + \frac{1}{\beta_1}\right)}$$

$$= 0.005 \Omega$$

$$43. R_{out} = 1 \Omega.$$

$$\beta_1 = 40 \quad \beta_2 = 50.$$

$$R_{out} = 1 = \frac{1}{g_m (1 + \beta_1 + \frac{1}{\beta_1})}$$

$$\Rightarrow g_m = 0.024 \text{ S} = \frac{I_B \beta_2}{V_T}$$

$$\Rightarrow I_{B2} = 0.012 \text{ mA.}$$


$$I_I = I_{C1} + I_{E2} = I_{B1} \beta_1 + (I_{C2} + I_{B2})$$

$$= I_{C2} \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= I_{B2} \beta_2 \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= 0.012 [50 \times 40 + 50 + 1]$$

$$= 25.6 \text{ mA}$$

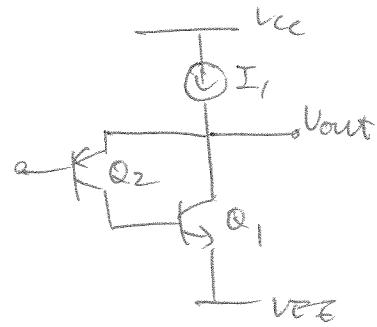

$$44. \quad V_p = 0.5V$$


$$R_L = 8\Omega.$$

$$P_{RL} = \frac{V_p^2}{2R_L} = \frac{0.25}{16} = 0.0156 \text{ W}$$

$$P_I = -I \times V_{EE} = 0.14 \text{ W}$$

$$P_{Q_1} = I_1 \left(V_{CC} - \frac{V_p}{2} \right) = 0.1225 \text{ W}$$
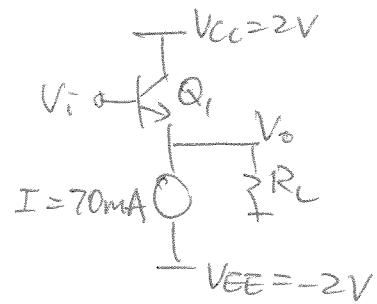
$$\therefore \eta = \frac{P_{RL}}{P_{RL} + P_I + P_{Q_1}} = \frac{0.0156}{0.2781} = 5.6\%$$



$$45. P_{R_L} = \frac{V_P^2}{2R_L} = \frac{(V_{CC} - V_{BE})^2}{2R_L}$$

$$P_{Q_1} = I_1 \left(V_{CC} - \frac{V_{CC} - V_{BE}}{2} \right)$$

$$P_I = +I_1 |V_{EE}|$$

Assume

$$|V_{CC}| = |V_{EE}|,$$

$$\begin{aligned} I_1 &= V_P / R_L \\ &= \frac{V_{CC} - V_{BE}}{R_L} \end{aligned}$$

$$\begin{aligned} \therefore \eta &= \frac{P_{R_L}}{P_{R_L} + P_{Q_1} + P_I} = \frac{\frac{(V_{CC} - V_{BE})^2}{2R_L}}{\frac{(V_{CC} - V_{BE})^2}{2R_L} + I_1 \left[V_{CC} - \frac{V_{CC} - V_{BE}}{2} + |V_{EE}| \right]} \\ &= \frac{\frac{1}{2R_L}}{\frac{1}{2R_L} + \frac{3(V_{CC} - V_{BE})}{2R_L(V_{CC} - V_{BE})}} \\ &= \frac{1}{1 + \frac{3(V_{CC} - V_{BE})}{V_{CC} - V_{BE}}} \approx \frac{V_{CC} - V_{BE}}{3(V_{CC} - V_{BE})} \end{aligned}$$

$$46. \eta = \frac{\frac{V_P^2}{2R_L}}{\frac{V_P^2}{2R_L} + \frac{2V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)}$$

$$= \frac{\pi}{4} \frac{V_P}{V_{CC}}$$

$$\Rightarrow \eta \Big|_{V_P = V_{CC} - V_{BE}} = \frac{\pi}{4} - \frac{\pi}{4} \cdot \frac{V_{BE}}{V_{CC}}$$

$$\begin{aligned}
 47. \quad \eta &= \frac{\frac{(V_p/2)^2}{2R_L}}{\frac{(V_p/2)^2}{2R_L} + \frac{2(V_p/2)}{R_L} \left(\frac{V_{cc}}{\pi} - \frac{V_p/2}{4} \right)} \\
 &= \frac{\frac{V_p^2}{8R_L}}{\frac{V_p^2}{8R_L} + \frac{V_p}{R_L} \left(\frac{V_{cc}}{\pi} - \frac{V_p}{8} \right)} = \frac{\frac{1}{8R_L}}{\frac{1}{8R_L} + \frac{1}{R_L} \left(\frac{V_{cc}}{V_p\pi} - \frac{1}{8} \right)} \\
 &= \frac{1}{1 + \left(\frac{8V_{cc}}{V_p\pi} - 1 \right)} = \frac{\pi}{8} \frac{V_p}{V_{cc}} \approx 39\%.
 \end{aligned}$$

$$48. \quad V_{CC} = 3V \quad P_{RL} = 0.2W \quad R_L = 8\Omega.$$

$$P_{RL} = \frac{1}{2} \frac{V_P^2}{R_L} \Rightarrow V_P = \sqrt{2P_{RL} \times R_L} = 1.8V$$

$$\therefore \eta = \frac{P_{RL}}{P_{RL} + \frac{2VP}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)} = \frac{0.2}{0.2 + \frac{3.6}{8} \left(\frac{3}{\pi} - \frac{1.8}{4} \right)}$$

$$\approx 18\%.$$

49. Power = 1 W


$$R_L = 8\Omega$$

$$P_{LOAD} = \frac{1}{2} \frac{V_P^2}{R_L} = 1W$$

$$\Rightarrow V_P = 4V \Rightarrow I_1 = \frac{V_P}{R_L} = 0.5 \text{ mA}$$

(Note: the problem does not specify small-signal voltage gain, so choose $V_P = I_1 R_L$)

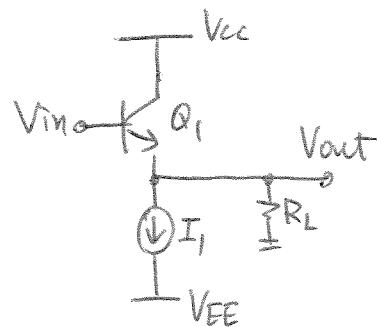
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 (V_{CC}) \\ &= (0.5 \text{ mA})(5V) \\ &= 2.5 \text{ mW} \end{aligned}$$



$$50. \quad A_V = 0.8$$

$$R_L = 4\Omega$$
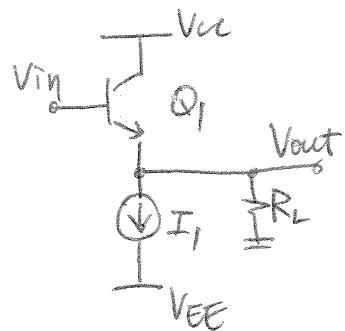
$$A_V = \frac{R_L}{R_L + \frac{1}{g_m}} = \frac{4}{4 + \frac{0.026}{I_{C1}}} = 0.8$$



$$\Rightarrow I_{C1} = 26 \text{ mA}$$

$\therefore I_1 = I_{C1} = 26 \text{ mA}$ (Vout biased at 0 V.)

$$\begin{aligned} \text{Max Output Swing} &= [I_1 R_L] \\ &\approx (26 \text{ mA})(8\Omega) \\ &= 0.208 \text{ V} \end{aligned}$$

$$\begin{aligned} P_{Q1} (\text{power rating}) &= I_1 V_{CC} (V_F = 0) \\ &= (26 \text{ mA})(5 \text{ V}) = 130 \text{ mW} \end{aligned}$$


$$51. A_V = 0.6$$

$$R_L = 8 \Omega$$

$$r_{D_1} = r_{D_2} = 0$$

$$A_V = \frac{R_L}{R_L + \frac{1}{g_m}} = \frac{(8\Omega)}{(8\Omega) + \frac{0.026V}{I_{Q_1}}} = 0.6$$
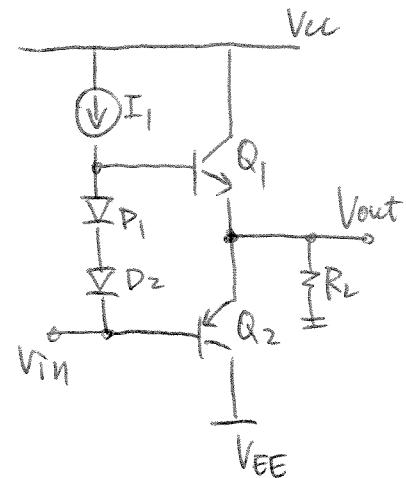
$$\Rightarrow I_{Q_1} = I_{Q_2} = 4.8 \text{ mA}$$



(V_{out} biased at 0 V.)

52. Power = 1 W (to load)

$$R_L = 8\Omega$$

$$|V_{BE}| \approx 0.8 \text{ V}$$

$$\beta_1 = 40$$

$$P_L = \frac{1}{2} \frac{V_p^2}{R_L} = 1 \text{ W}$$


$$\Rightarrow V_p = 4 \text{ V}$$

\therefore Min allowable supply voltage = $V_p + |V_{BE}| = 4.8 \text{ V}$

- At $+V_p$, all of I_1 goes to base of Q_1 ,

$$\Rightarrow I_1 = I_{B1} = \frac{I_{C1}}{\beta_1} = \frac{V_p}{R_L} \cdot \frac{1}{\beta_1} \quad (Q_2 \text{ off})$$
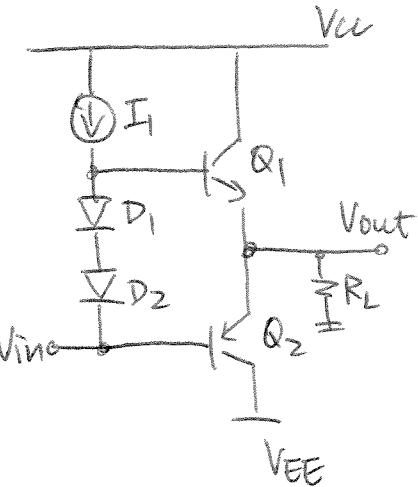
$$= \frac{4}{8} \cdot \frac{1}{40} = \frac{1}{80} = 12.5 \text{ mA.}$$



$$53. P_{Q,MAX} = 2W$$

$$R_L = 8\Omega$$


For this circuit,

$$P_{AVG, MAX} = \frac{V_{CC}^2}{\pi^2 R_L} \quad (V_p = \frac{2V_{CC}}{\pi})$$

$$= 2W$$

$$\Rightarrow V_{CC}|_{MAX} = 12.6V \Rightarrow V_p|_{MAX} = \frac{25.2}{\pi} = 8.02V$$
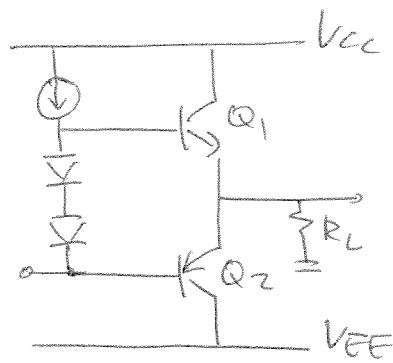
$$\therefore P_{RL, MAX} = \frac{V_{p, MAX}^2}{2R_L} = \frac{(8.02)^2}{2 \cdot 8} = 4.02W$$



54. For this circuit,

$$P_{Q,MAX} = 2W$$

$$P_{AVG, MAX} = \frac{V_{CC}^2}{\pi R_L} \quad (V_P = 2 \frac{V_{CC}}{\pi})$$

$$R_L = 4\Omega$$

$$\Rightarrow V_{CC, MAX} = \sqrt{\frac{\pi^2 R_L P_{Q, MAX}}{1}} = 8.9 V$$

$$\Rightarrow V_{P, MAX} = \frac{2V_{CC, MAX}}{\pi} = 5.6 V$$

$$\therefore P_{R_L, MAX} = \frac{V_{P, MAX}^2}{2R_L} = \frac{32}{2(4)} = 4W$$

$$55. \quad A_V = 4 \quad R_L = 8\Omega \quad I_{C_1} \approx I_{C_2} \\ \beta_1 = 40 \quad \beta_2 = 20$$

Suppose we want 1st-stage (CE amplifier) to have gain = 5 \Rightarrow 2nd stage gain = 0.8.

$$\Rightarrow 0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$0.8 = \frac{8}{8 + \frac{1}{2g_m}} \Rightarrow g_{m1} = 8 \Rightarrow I_{C_1} = I_{C_2} = 6.5 \text{ mA}$$

$$r_{\pi_1} \parallel r_{\pi_2} = \frac{\beta_1 V_T}{I_{C_1}} \parallel \frac{\beta_2 V_T}{I_{C_2}} = \frac{40(0.026)}{6.5 \text{ mA}} \parallel \frac{20(0.026)}{6.5 \text{ mA}} \approx 133 \Omega$$

- $A_V = 4 = g_{m4} (r_{\pi_1} \parallel r_{\pi_2}) (g_{m1} + g_{m2}) R_L$

$$= \frac{I_{C4}}{V_T} (133) (0.5) 8$$

$$\Rightarrow I_{C4} = I_{C3} = \frac{4 V_T}{8 (133) (0.5)} = 0.195 \text{ mA}$$

Max I_Q , when all of I_{C3}/I_{C4} supports base current of Q_1

$$\Rightarrow I_{Q1, MAX} = I_{C4} = 0.195 \text{ mA}$$

$$56. \quad A_v = 4 \quad R_L = 4.52 \quad I_{C_1} \approx I_{C_2} \\ \beta_1 = 40 \quad \beta_2 = 20$$

1st stage gain = 5 (CE amplifier)

2nd " " = 0.8

$$0.8 = \frac{R_L}{R_L + \frac{1}{g_m + g_m}} = \frac{4}{4 + \frac{1}{2g_m}}$$

$$\Rightarrow g_m = 0.5 \text{ S} \Rightarrow I_{C_1} = I_{C_2} = 13 \text{ mA}$$

$$r_{\pi_1} \parallel r_{\pi_2} = \frac{\beta_1 V_T}{I_C} \parallel \frac{\beta_2 V_T}{I_C} = 80 \parallel 40 = 26.7 \text{ s}\Omega$$

$$A_v = 4 = g_m (r_{\pi_1} \parallel r_{\pi_2}) (g_m + g_m) R_L \\ = \frac{I_{C_4}}{V_T} (26.7) (1) (4)$$

$$\Rightarrow I_{C_4} = I_3 = \frac{4 V_T}{(26.7)(1)(4)} = 0.974 \text{ mA.}$$

- Max I_{Q_1} ($I_{Q1,MAX}$) when $I_{C_4} = I_{Q,MAX} = 0.974 \text{ mA}$.
- For a reduction of 2x the R_L , we have to provide $\approx 5x$ current to base of Q_1 . ($\frac{0.974}{0.195} \approx 5$)

$$57. P_{RL} = 2 \text{ W} \quad \beta_1 = 40 \\ R_L = 8 \Omega \quad \beta_2 = 20 \\ |V_{BE}| = 0.8 \text{ V}$$

$$(a) P_{RL} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p \approx 5.6 \text{ V}$$

• At $+V_p$, $V_A = V_p + |V_{BE}|$.

• For Q_3 in active region, $V_A \leq V_{bias}$

$$\Rightarrow V_{CC} \geq V_{bias} + |V_{BE}| = V_p + 2|V_{BE}|$$


$$\geq 5.6 + 1.6 = 7.2 \text{ V.}$$

$$(b) I_P = \frac{V_p}{R_L} = 0.7 \text{ A. } (= I_{E_1}), (= I_{E_2})$$

$$\Rightarrow I_{B_1} = \frac{I_{E_1}}{1+\beta_1} = 17 \text{ mA.}$$

∴

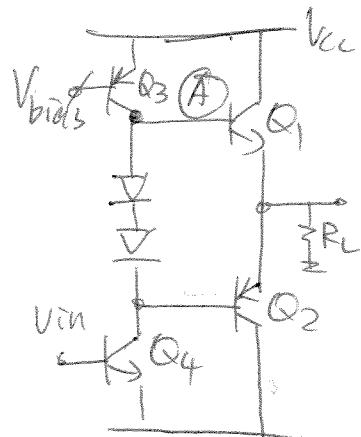∴ We bias Q_3 & Q_4 with $I_C = 17 \text{ mA.}$



$$(c) P_{AV} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$

$$= \frac{5.6}{8} \left(\frac{5}{\pi} - \frac{5.6}{4} \right) = 3.66 \text{ W}$$

$$(d) P_{IQ_3} = 2V_{CC} \times I_{Q_3} = 10 \times 17 \text{ mA} = 170 \text{ mW}$$

$$P_{AV, Q_1} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right) = 3.66 \text{ W}$$

$$P_{RL} = 2 \text{ W}$$

$$\Rightarrow \eta = \frac{P_{RL}}{P_{IQ_3} + 2 \cdot P_{AV, Q_1} + P_{RL}}$$

$$= \frac{2}{170 \text{ mW} + 3.66 \times 2 + 2} = 0.21 = 21\%$$


58.

$$(a) A_V = 5 \quad R_L = 4\Omega \quad \beta_1 = 40 \quad \beta_2 = 20.$$

Assume $I_{C1} \approx I_{C2}$.

$$\frac{V_{out}}{V_N} = \frac{R_L}{(g_{m1} + g_{m2}) + R_L} = 0.8$$
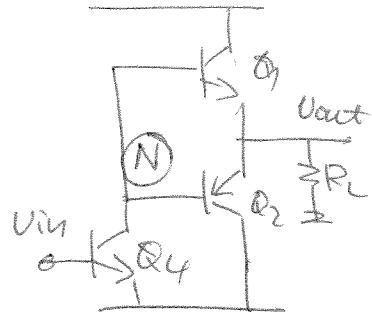
$$\Rightarrow 2g_{m1} = 1 \Rightarrow I_{C1} = 2V_T = 0.052 \text{ A.}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = +g_{m4} (r_{\pi1} \parallel r_{\pi2}) (g_{m1} + g_{m2}) R_L = 5$$

Assume $g_{m1} \approx g_{m2}$:

$$\Rightarrow I_{C4} = V_T \times \frac{5}{(r_{\pi1} \parallel r_{\pi2}) (g_{m1} + g_{m2}) R_L}$$

$$= V_T \times \frac{5}{(r_{\pi1} \parallel r_{\pi2}) (g_{m1} \times 2) R_L}$$

$$= 0.026 \times \frac{5}{(6.7\Omega)(2 \times 2 \times 4)}$$

$$\approx 1.2 \text{ mA.}$$

$$\Rightarrow \text{Max } I \text{ by } Q_1 = \beta_1 \times I_{C4} = 48 \text{ mA}$$

$$\Rightarrow P_{RL} = \frac{1}{2} I^2 R_L = 24 \times 4 \text{ mW} = 96 \text{ mW, } \text{ BELOW requirement!}$$

$$(b) P = 5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = 6.3 \text{ V}$$

$$\Rightarrow I_P = \frac{V_p}{R_L} = 1.6 \text{ A}$$

$$\Rightarrow I_{B2, MAX} = \frac{I_P}{\beta_2} = \frac{1.6}{20} = 79 \text{ mA}$$

$\Rightarrow I_{C2}$ must equal 79 mA to allow max output swing V_p

$$\Rightarrow g_{m4} = \frac{I_{C4}}{V_T} = 3.04 \text{ S}$$

Suppose 2nd stage gain = 0.8 ($I_{C1} = I_{C2}$)

$$\Rightarrow \frac{V_{out}}{V_N} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \Rightarrow g_{m1} = 0.5 \text{ S}$$


$$= 0.8 \Rightarrow I_{C1} = I_{C2} = 13 \text{ mA.}$$

$$r_{\pi_1} \parallel r_{\pi_2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 26.7 \Omega.$$


$$\therefore \frac{V_{out}}{V_N} = -(3.04)(26.7 \Omega)(0.5 + 0.5)4$$

$$= -324 !! (\text{huge! Impractical})$$

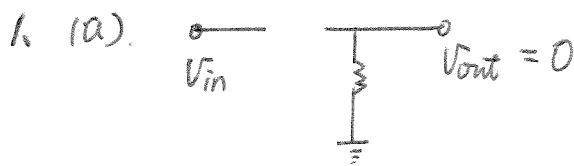- Even when the 2nd stage gets close to 1, we still need huge gain from first stage.



(Low freq.)

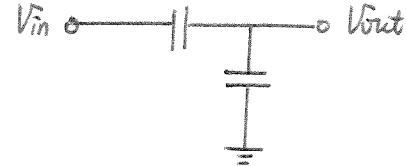


(High freq.)

This is a high pass filter.




(Low freq.)

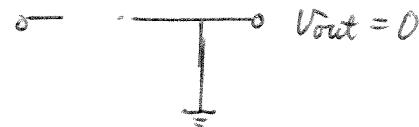

(High freq.)

This is a low pass filter.

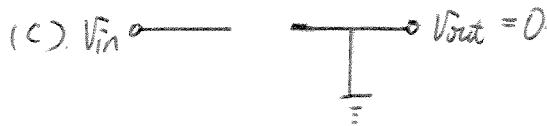


(Low freq.)



(High freq.)

This is a high pass filter.

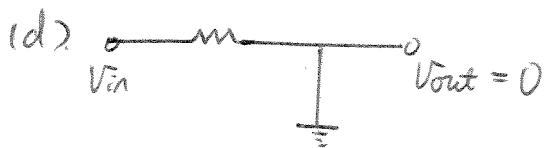

(Low freq.)




(High freq.)

This is a high pass filter.




(Low freq.)

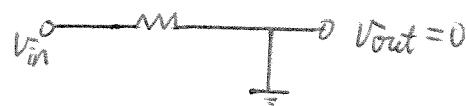

(High freq.)


This is a low pass filter.

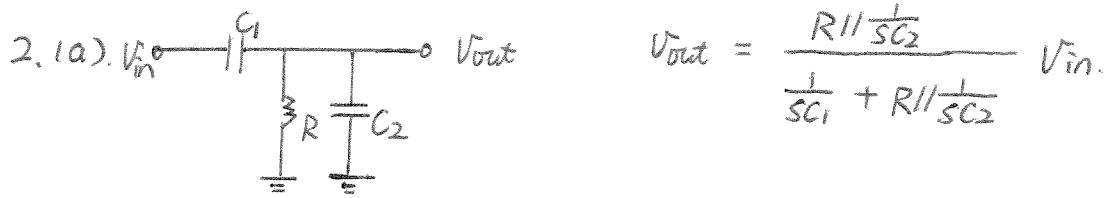


$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{\frac{1}{s(C_1+C_2)}}{s + \frac{1}{R(C_1+C_2)}} , \quad \text{zero} = 0; \quad \text{pole} = -\frac{1}{R(C_1+C_2)}$$


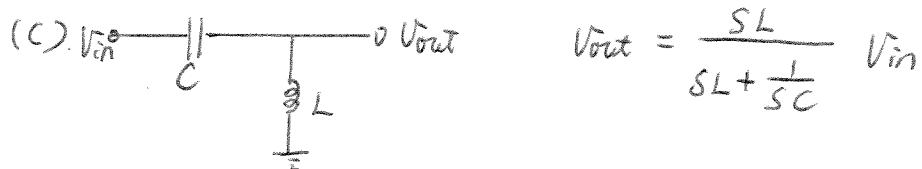
$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1/(LC)}{s^2 + \frac{1}{LC}} \quad \text{zero: No finite zero; poles} = \pm i \frac{1}{\sqrt{LC}}$$



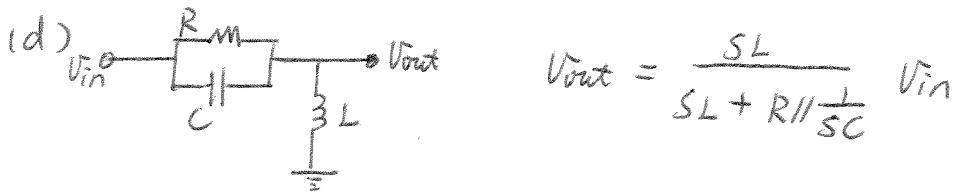
$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{s^2 LC}{s^2 + \frac{1}{LC}} \quad \text{zeros: Two zeros at } 0; \quad \text{poles} = \pm i \frac{1}{\sqrt{LC}}$$



$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{s(s + \frac{1}{RC})(RC)^2}{s^2 + \frac{s}{RC} + \frac{1}{LC}} \quad \text{zeros: } 0, -\frac{1}{RC}$$
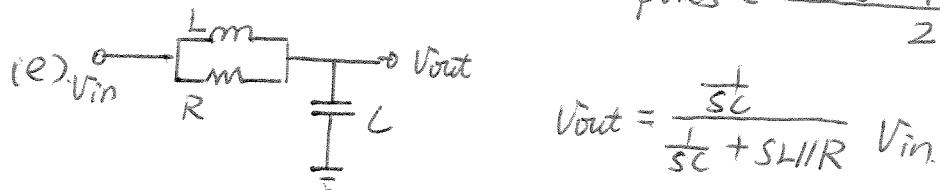
$$\text{poles} = \frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}}{2}$$




$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{\frac{1}{RC}(s + \frac{R}{L})}{s^2 + \frac{s}{RC} + \frac{1}{LC}}, \quad \text{zero} = -\frac{R}{L}; \quad \text{poles} = \frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}}{2}$$

B.

Since $\frac{V_{out}}{V_{in}} = \frac{1}{(s+a)(s+b)}$, where a and b are real and positive, the transfer function contains no finite zero and two real poles on the left hand plane. But, after reviewing Problem #2 we discover that NONE of the networks yield this case.

4.


a)

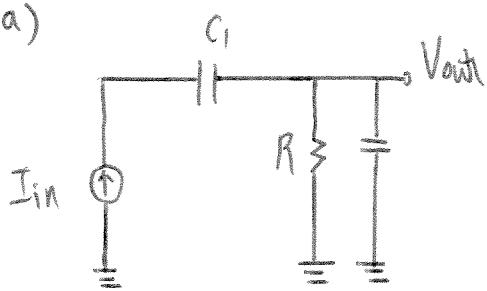

$$\frac{V_{out}}{I_{in}} = \frac{1/C_2}{S + 1/(RC_2)}$$

Zero: No finite zero
Pole: $-1/(RC_2)$


b)

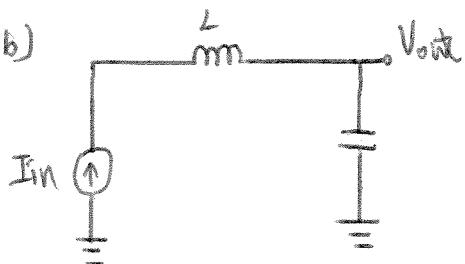

$$\frac{V_{out}}{I_{in}} = \frac{1}{SC}$$

Zero: No finite zero
Pole: 0


c)

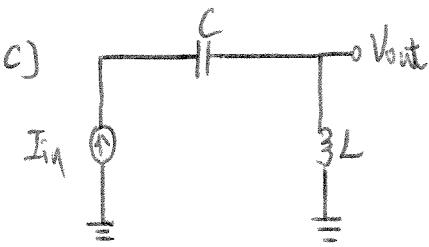

$$\frac{V_{out}}{I_{in}} = SL$$

Zero: 0
Pole: No finite pole


d)

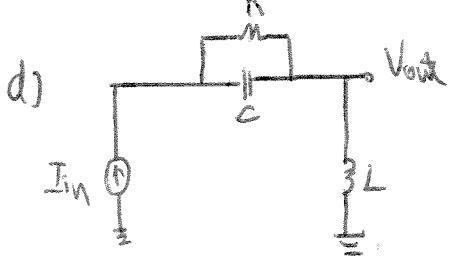

$$\frac{V_{out}}{I_{in}} = SL$$


Zero: 0
Pole: No finite pole

e)

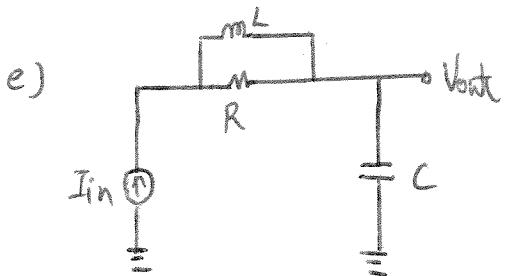

$$\frac{V_{out}}{I_{in}} = \frac{1}{SC}$$

Zero: No finite zero
Pole: 0

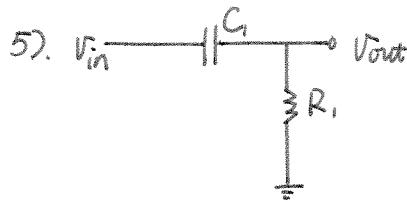5). 

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 + \frac{1}{Cs}} = \frac{\frac{1}{s}}{s + \frac{1}{R_1 C_1}}$$

zero = 0; pole = $-\frac{1}{R_1 C_1}$.


$$\frac{dP}{dC_1} = \frac{1}{(R_1 C_1)^2} \cdot R_1 = \frac{1}{R_1 C_1^2},$$

$$S_{C_1}^P = \frac{\frac{dP}{dC_1}}{\frac{dP}{dG}} = \frac{dP}{dC_1} \cdot \frac{C_1}{P} = -\frac{1}{R_1 C_1^2} \cdot C_1 \cdot (R_1 C_1) = -1.$$

Similarly

$$S_{R_1}^P = -1.$$

As for the sensitivity of zero, since the zero is at 0, which is independent of R_1 and C_1 . $S_{R_1}^z = S_{C_1}^z = 0$.

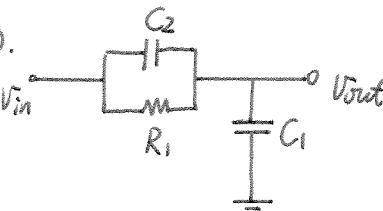6). 

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + R_1 // sC_2}$$

$$= \frac{1}{R_1 C} \cdot \frac{s + \frac{1}{R_1 C}}{R_1(C+C_2) [s + \frac{1}{R_1(C+C_2)}]}$$

$$\text{zero} = -\frac{1}{R_1 C_2}, \quad \text{pole} = -\frac{1}{R_1(C+C_2)}$$

$$\frac{dP}{dR_1} = [R_1(C_1+C_2)]^{-2} \cdot (C_1+C_2) = -\frac{C_1+C_2}{R_1(C_1+C_2)} \cdot P = -\frac{P}{R_1}$$

$$S_{R_1}^P = \frac{\frac{dP}{dR_1}}{R_1} = \frac{dP}{dR_1} \cdot \frac{R_1}{P} = -1.$$

$$\frac{dP}{dC_1} = [R_1(C_1+C_2)]^{-2} \cdot R_1 = -\frac{P}{C_1+C_2}$$


$$S_{C_1}^P = \frac{\frac{dP}{dC_1}}{C_1} = \frac{dP}{dC_1} \cdot \frac{C_1}{P} = -\frac{C_1}{C_1+C_2}$$

Conversely,

$$S_{C_2}^P = -\frac{C_2}{C_1+C_2}.$$

From Problem 5).

$$S_{R_1}^Z = S_{C_2}^Z = -1.$$

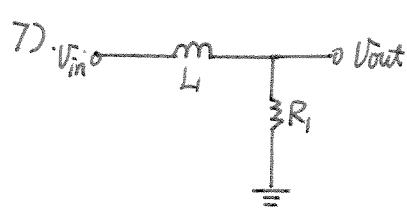7) 

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R_1}{R_1 + L_1 s} = \frac{R_1/L_1}{s + R_1/L_1}$$


$$\text{pole} = -\frac{R_1}{L_1}$$

$$dP = \frac{\partial P}{\partial R_1} \cdot dR_1 + \frac{\partial P}{\partial L_1} dL_1 = -\frac{1}{L_1} dR_1 + \frac{R}{L_1^2} dL_1$$

$$\Rightarrow \frac{dP}{P} = \frac{dR_1}{R_1} - \frac{dL_1}{L_1}$$

$$\left| \frac{dP}{P} \right| \leq 5\%, \text{ and } \left| \frac{dR_1}{R_1} \right| \leq 3\%$$

$$\Rightarrow \left| \frac{dL_1}{L_1} \right| \leq 2\%$$

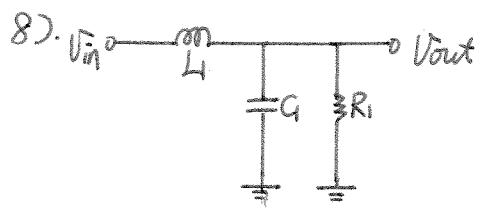

$$a). \quad V_{out} = V_{in} \cdot \frac{R_1 // C_1 s}{R_1 // C_1 s + SL_1}$$

$$= V_{in} \cdot \frac{\frac{R_1}{R_1 C_1 s + 1}}{\frac{R_1}{R_1 C_1 s + 1} + SL_1}$$



$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 C_1 L_1 s^2 + 4s + R_1} = \frac{1}{4C_1} \cdot \frac{1}{s^2 + \frac{1}{R_1 C_1} s + \frac{1}{4C_1}}$$

$$b). \quad \text{poles} = \frac{-\frac{1}{R_1 C_1} \pm \sqrt{(\frac{1}{R_1 C_1})^2 - \frac{4}{4C_1}}}{2}$$

For them to be real $\Rightarrow (\frac{1}{R_1 C_1})^2 - \frac{4}{4C_1} \geq 0$

$$\Rightarrow \frac{1}{R_1 C_1} \geq \sqrt{\frac{2}{4C_1}}$$

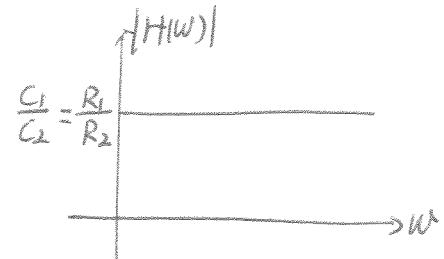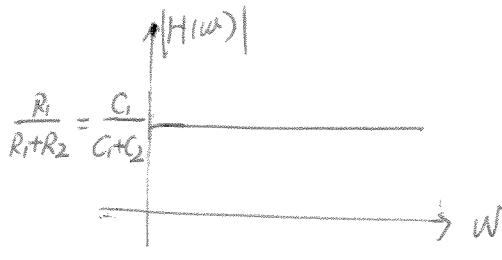9). If the zero and pole coincide, they will neutralize each other, and also render the transfer function flat.



$$10). \quad H(s) = \frac{\alpha s^2 + \beta s + \gamma}{s^2 + \frac{w_h}{Q}s + w_h^2}$$

$$P_{1,2} = -\frac{w_h}{2Q} \pm jw_h \sqrt{1 - \frac{1}{4Q^2}}$$

$$\text{If } Q = \frac{1}{2}, \text{ then } P_{1,2} = -\frac{w_h}{2Q}.$$

11.

$$|H(j\omega)|^2 = \frac{\gamma^2}{(\omega_n^2 - \omega^2)^2 + \left(\frac{Q\omega_n}{2}\omega\right)^2}$$

No peaking means no local minimum for $(\omega_n^2 - \omega^2)^2 + \left(\frac{Q\omega_n}{2}\omega\right)^2$, which is also known as $D(\omega)$.

A local min exists if $\frac{\partial D(\omega)}{\partial \omega} = 0$.

$$\frac{\partial D(\omega)}{\partial \omega} = \left(\frac{\partial D(\omega)}{\partial \omega^2} \right) \left(\frac{\partial \omega^2}{\partial \omega} \right), \quad \frac{\partial D(\omega)}{\partial \omega^2} = -2(\omega_n^2 - \omega^2) + \left(\frac{Q\omega_n}{2}\right)^2$$

$$\frac{\partial \omega^2}{\partial \omega} = 2\omega, \text{ so } \frac{\partial D(\omega)}{\partial \omega} = 2\omega \left[2(\omega_n^2 - \omega^2) + \left(\frac{Q\omega_n}{2}\right)^2 \right] = 0$$

$$\text{Solving for } \omega, \text{ we have } \omega = 0, \pm \sqrt{\omega_n^2 - \frac{1}{2} \left(\frac{Q\omega_n}{2}\right)^2}$$

Will bring $D(\omega)$ to its min value.

At $\omega=0$, we have the DC value of the transfer function.

However if $Q^2 < \frac{1}{2}$ or $Q < \frac{1}{\sqrt{2}}$, $\omega_n^2 - \frac{1}{2} \left(\frac{Q\omega_n}{2}\right)^2$ becomes negative, which is not physical. Therefore, there is no peaking for $Q < \frac{1}{\sqrt{2}}$. And at $Q = \frac{1}{\sqrt{2}}$, we have $\omega = \pm 0$, which corresponds to the DC value of the transfer function, not peaking. Therefore, the only option left is for $Q > \frac{1}{\sqrt{2}}$, and that is the condition for peaking.

$$12). |H(j\omega)|^2 = \frac{\gamma^2}{(w_n^2 - \omega^2)^2 + \left(\frac{w_n}{\alpha} \omega\right)^2}$$

If $\alpha > \sqrt{2}/2$, it will peak at $\omega_0 = w_n \sqrt{1 - 1/(2\alpha)^2}$

$$H(j\omega) = \frac{\gamma}{\sqrt{(w_n^2 - \omega^2)^2 + \left(\frac{w_n}{\alpha} \omega\right)^2}}$$

$$\Rightarrow H(j\omega_0) = \frac{\gamma}{\sqrt{\left[w_n^2 - (w_n \sqrt{1 - \frac{1}{2\alpha^2}})^2\right]^2 + \left(\frac{w_n}{\alpha} w_n \sqrt{1 - \frac{1}{2\alpha^2}}\right)^2}}$$


$$= \frac{\gamma}{\sqrt{\left(w_n^2 \cdot \frac{1}{2\alpha^2}\right)^2 + \frac{w_n^4}{\alpha^2} \left(1 - \frac{1}{2\alpha^2}\right)}}$$

$$= \frac{\gamma}{\sqrt{\frac{w_n^4}{4\alpha^4} + \frac{w_n^4}{\alpha^2} - \frac{w_n^4}{2\alpha^4}}}$$

$$= \frac{\alpha \gamma}{w^2 \sqrt{1 - \frac{1}{4\alpha^2}}}$$

Normalize to passband $\Rightarrow \frac{\alpha}{\sqrt{1 - \frac{1}{4\alpha^2}}}$
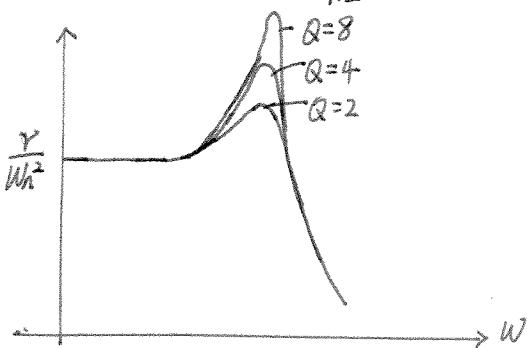
$$\alpha = 2, \text{ peak} = \frac{2}{\sqrt{1 - \frac{1}{4 \cdot 2^2}}} = 2.07; \quad \alpha = 4, \text{ peak} = 4.03; \quad \alpha = 8, \text{ peak} = 8.02$$




$$13). \quad H(s) = \frac{\beta s}{s^2 + \frac{w_n}{\alpha} s + w_n^2}, \quad H(jw) = \frac{j\beta w}{w_n^2 + j\frac{w_n}{\alpha} w - w^2}$$

$$|H(jw)| = \frac{\beta w}{\sqrt{(w_n^2 - w^2)^2 + (\frac{w_n}{\alpha} w)^2}}$$


At $w = w_n$,

$$|H(jw_n)| = \frac{\beta w_n}{\frac{w_n}{\alpha} w_n} = \frac{\alpha}{w_n} \beta.$$

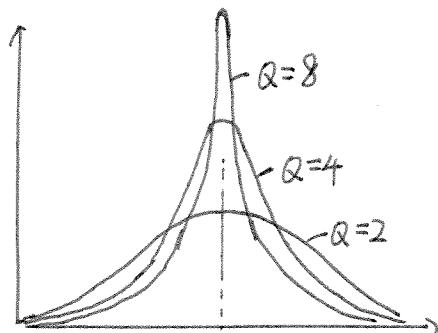
So if we normalize to β , we get $\frac{\alpha}{w_n}$.





14).

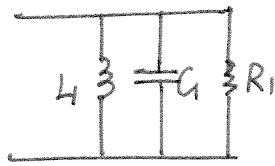

Assume R is
never negative

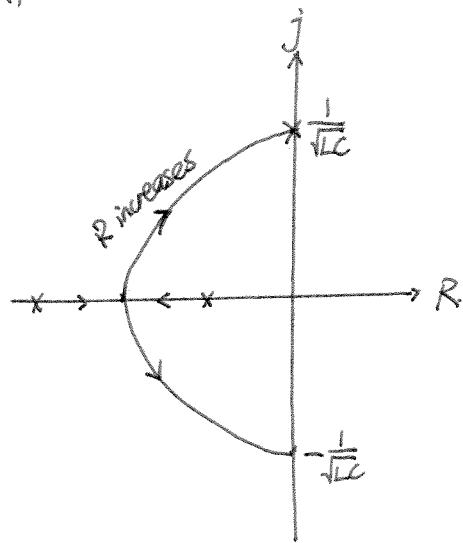

15).

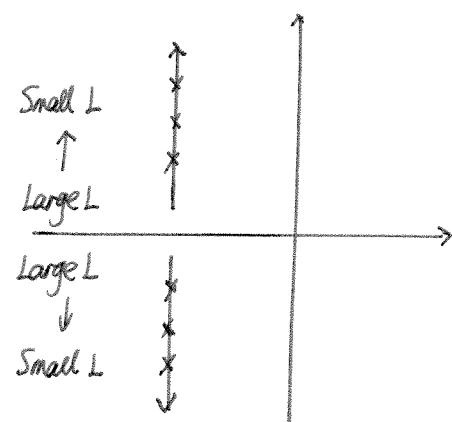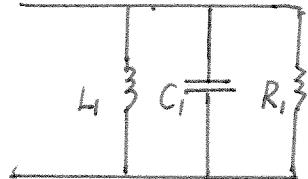

16.

$$1\text{dB peaking} \Rightarrow \frac{\omega^2}{(1 - \frac{1}{4\omega^2})} = (1.1)^2 = 1.21$$

$$\omega^2 = 1.21 \left(1 - \frac{1}{4\omega^2}\right) \Rightarrow 4\omega^4 - 4(1.1)^2\omega^2 + (1.1)^2 = 0$$


$$\omega^2 = 0.85704, 0.35296, \omega = 0.925765, 0.59410$$

$\omega = 0.925765$, since $\omega > \frac{1}{\sqrt{2}}$ for peaking

$$\omega = \frac{\omega_n}{\beta} = \frac{RC}{\sqrt{LC}} = R\sqrt{\frac{C}{L}} = 0.925765$$

17.

Sallen and Key filter

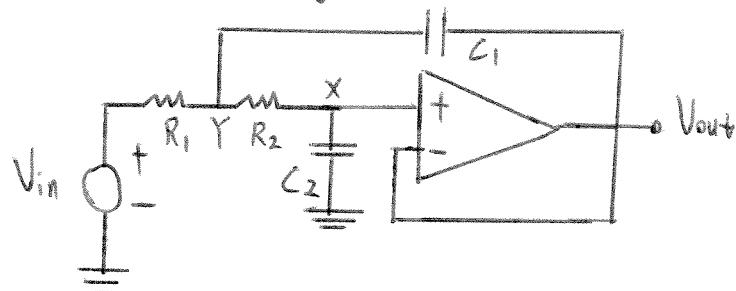

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{\frac{R_1 R_2 C_1}{C_2}},$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}},$$

$$H(s) = \left(s^2 + \frac{(R_1 + R_2) C_2 s}{R_1 R_2 C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2} \right)^{-1}$$

$$P_{1,2} = -\frac{(R_1 + R_2)}{R_1 R_2 C_1} \pm \sqrt{\left(\frac{R_1 + R_2}{R_1 R_2 C_1}\right)^2 - \frac{4}{R_1 R_2 C_1 C_2}}$$

$$P_{1,2} = -\frac{1}{2(R_1 // R_2) C_1} \pm \sqrt{\left(\frac{1}{(R_1 // R_2) C_1}\right)^2 - \frac{4}{R_1 C_1 R_2 C_2}}$$

$$\text{Assuming } \frac{4}{R_1 C_1 R_2 C_2} > \frac{1}{[(R_1 // R_2) C_1]^2}$$

$$P_{1,2} = -\frac{1}{2(R_1 // R_2) C_1} \pm j2 \sqrt{\frac{1}{R_1 C_1 R_2 C_2} - \frac{1}{4[(R_1 // R_2) C_1]^2}}$$

17.

a) $R_1: 0 \rightarrow \infty$


When $R_1 = 0$, Poles are at $\pm\infty$, so no finite poles. As $R_1 \uparrow$, $\frac{1}{R_1 C_1 R_2 C_2}$ approaches 0, and

$\frac{1}{4[(R_1//R_2)C_1]^2}$ approaches $\frac{1}{4[R_2 C_1]^2}$. There exists

$$\text{a } R_1 \text{ such that } \frac{1}{R_1 C_1 R_2 C_2} = \frac{1}{4[(R_1//R_2)C_1]^2} \Rightarrow$$

$$P_{1,2} = -\frac{1}{2(R_1//R_2)C_1}$$
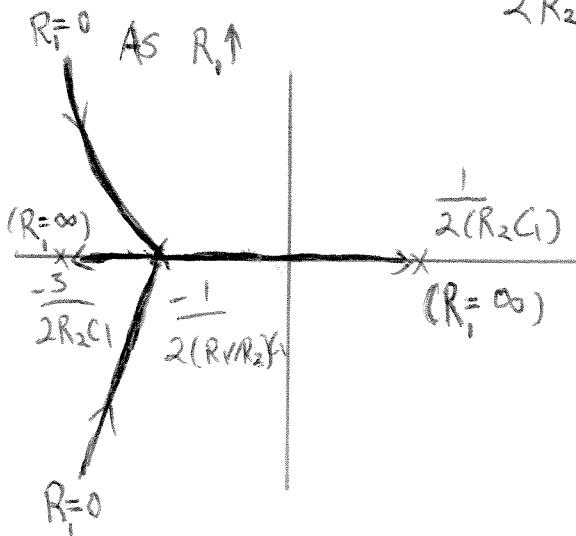
$$\text{As } R_1 \rightarrow \infty, P_{1,2} = \frac{-1}{2R_2 C_1} \pm \frac{1}{R_2 C_1} = -\frac{3}{2R_2 C_1}, \frac{1}{2R_2 C_1}$$



17. b)

R_2 from $0 \rightarrow \infty$

When $R_2 = 0$, $P_{1,2}$ are at $\pm\infty$

$$\text{As } R_2 \uparrow, \frac{-1}{2(R_1//R_2)C_1} \rightarrow -\frac{1}{2R_1C_1}$$

$$\frac{1}{R_1C_1R_2C_2} \rightarrow 0, \text{ and } \frac{1}{4[(R_1//R_2)C_1]^2} \rightarrow \frac{1}{4[R_1C_1]^2}$$


$$\text{For a certain } R_2, \frac{1}{R_1C_1R_2C_2} = \frac{1}{4[(R_1//R_2)C_1]^2}$$

$$\text{and } P_{1,2} = \frac{-1}{2(R_1//R_2)C_1}$$

Finally, when $R_2 = \infty$,

$$P_{1,2} = -\frac{1}{2R_1C_1} \pm 2\sqrt{\frac{1}{4[R_1C_1]^2}} = -\frac{1}{2R_1C_1} \pm \frac{1}{R_1C_1}$$
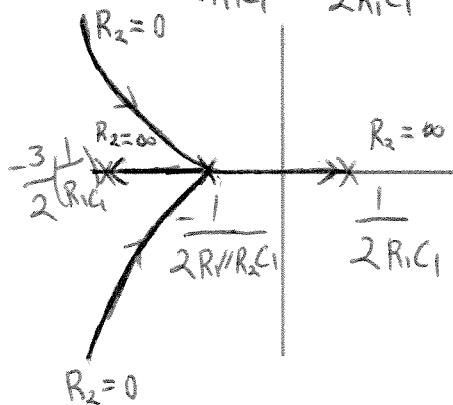
$$P_{1,2} = -\frac{3}{2R_1C_1}, \frac{1}{2R_1C_1}$$




(7. c)

As $C_1: 0 \rightarrow \infty$

When $C_1 = 0$, Poles are at $\pm\infty$

As $C_1 \uparrow$, Poles approach 0.

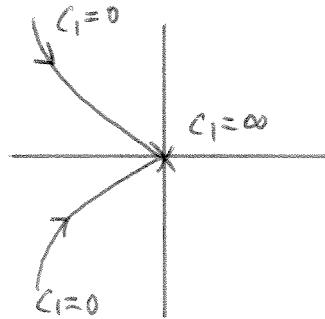


d) As $C_2: 0 \rightarrow \infty$


When $C_2 = 0$, Poles are at $\pm\infty$

When $C_2 = \infty$, Poles: $-\frac{1}{2(R_1//R_2)C_1} \pm \frac{1}{R_1//R_2C_1} = -\frac{3}{2}\left(\frac{1}{R_1//R_2C_1}\right)$

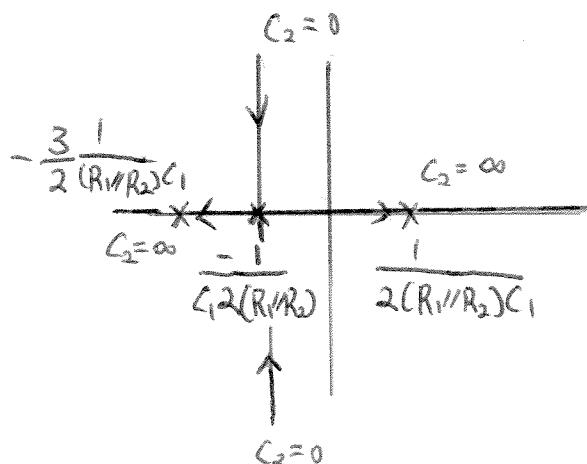$+\frac{1}{2R_1//R_2C_1}$ (note, real part doesn't depend on C_2)



18.

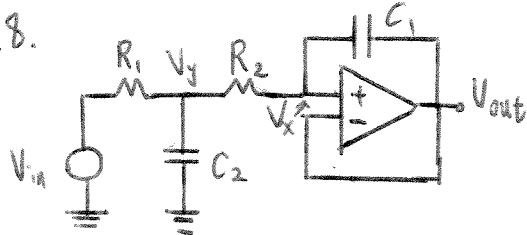


Assuming an ideal Op-amp, $V_x = V_{out}$. Therefore, no current will flow thru C_1 . Moreover, since the input impedance of an Op-amp (Z_{ideal}) is infinite, no current will flow thru R_2 as well, which means $V_y = V_x = V_{out}$.

$$\Rightarrow V_y = V_{out} = \frac{1/C_{2s}}{R_1 + 1/C_{2s}}$$

Not very useful since it's only a simple single pole lowpass filter. We can implement it with passive components, instead of op-amp.

19.

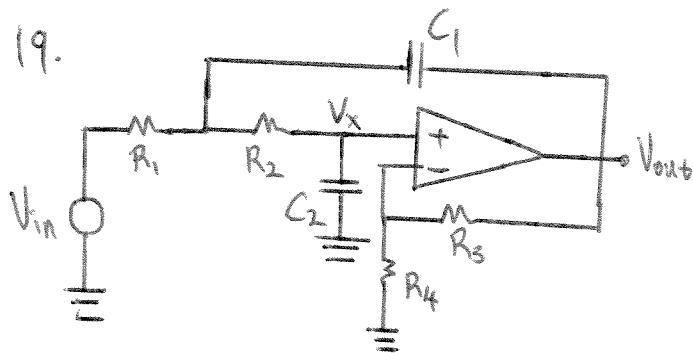

$$K=4, \quad C_1 = C_2 \\ Q=4$$

$$K = 1 + \frac{R_3}{R_4} = 4 \Rightarrow \frac{R_3}{R_4} = 3, \quad \frac{C_1}{C_2} = 1$$

$$\frac{1}{Q} = \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2}{R_1} \frac{C_2}{C_1}} - \sqrt{\frac{R_1 C_1}{R_2 C_2}} \frac{R_3}{R_4}$$

$$\frac{1}{Q} = \sqrt{\frac{R_1}{R_2}} + \sqrt{\frac{R_2}{R_1}} - 3 \sqrt{\frac{R_1}{R_2}} \Rightarrow \sqrt{\frac{R_1}{R_2}} - 2 \sqrt{\frac{R_1}{R_2}} = \frac{1}{Q}$$

$$\frac{1}{Q} = \left(\frac{R_1}{R_2} \right)^{\frac{1}{2}} - 2 \left(\frac{R_1}{R_2} \right)^{\frac{1}{2}} \Rightarrow \text{Squaring both sides} \Rightarrow$$

$$\frac{1}{Q^2} = 4 \left(\frac{R_1}{R_2} \right) - 4 + \left(\frac{R_1}{R_2} \right)^{-1} \Rightarrow \frac{1}{16} = 4 \left(\frac{R_1}{R_2} \right) - 4 + \left(\frac{R_2}{R_1} \right)$$

$$\left(\frac{1}{16} + 4 \right) \frac{R_1}{R_2} = \frac{R_1}{R_2} \left(4 \frac{R_1}{R_2} + \frac{R_2}{R_1} \right) \Rightarrow 4.0625 \frac{R_1}{R_2} = 4 \left(\frac{R_1}{R_2} \right)^2 + 1$$

$$4 \left(\frac{R_1}{R_2} \right)^2 - 4.0625 \left(\frac{R_1}{R_2} \right) + 1 = 0, \quad \frac{R_1}{R_2} = 0.41908, 0.5 \cancel{, 0.55}$$

This leads to a negative Q .

19.

$$S_{R_1}^{\theta} = -\frac{1}{2} \left[\sqrt{\frac{R_1 C_2}{R_2 C_1}} - \sqrt{\frac{R_2 C_2}{R_1 C_1}} - (K-1) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right] \Omega$$

$$S_{R_1}^{\theta} = -\frac{1}{2} \left[\sqrt{0.41908} - \sqrt{1/0.41908} - 3\sqrt{0.41908} \right] 4$$

$$S_{R_1}^{\theta} = 5.68$$

20.

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}$$

$$\Omega = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{\Omega}{\sqrt{1 - \frac{1}{4\Omega^2}}} = 1.1 \Rightarrow \Omega^2 = (1.1)^2 \left(1 - \frac{1}{4\Omega^2}\right)$$

$$\Rightarrow 3.3058\Omega^4 - 4\Omega^2 + 1 = 0$$

$$\Omega^2 = 0.85704, 0.35296,$$

$$\Omega = \pm 0.925765, \pm 0.5941$$

In order to peak, $\Omega > \frac{1}{\sqrt{2}} \Rightarrow \Omega = 0.925765$

$$\Rightarrow \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} = 0.925765$$

$$\text{let } \frac{C_1}{C_2} = 1 \Rightarrow \frac{1}{R_1 + R_2} \sqrt{R_1 R_2} = 0.925765$$

$$\Rightarrow R_1 R_2 = (0.925765)^2 (R_1 + R_2)^2$$

$$\frac{R_1 R_2}{R_1 + R_2} = R_1 // R_2 = 0.85704 (R_1 + R_2)$$

$$R_1 // R_2 = 0.85704 (R_1 + R_2)$$

only if $\frac{C_1}{C_2} = 1$

21.

$$S_{R_1}^Q = 2, \quad C_2 = C_1, \quad Q = f\left(\sqrt{\frac{R_2}{R_1}}\right)$$


Range of Q and $\sqrt{R_2/R_1}$

$$S_{R_1}^Q = -\frac{1}{2} \left[\sqrt{\frac{R_1 C_2}{R_2 C_1}} - \sqrt{\frac{R_2 C_2}{R_1 C_1}} - (K-1) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right] Q$$

$$S_{R_1}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}} \Rightarrow Q = -\frac{1}{2} + \sqrt{\frac{R_2}{R_1}}$$

$$\Rightarrow 2.5 = Q \sqrt{\frac{R_2}{R_1}}, \quad Q = \frac{2.5}{\sqrt{R_2/R_1}}$$

Q

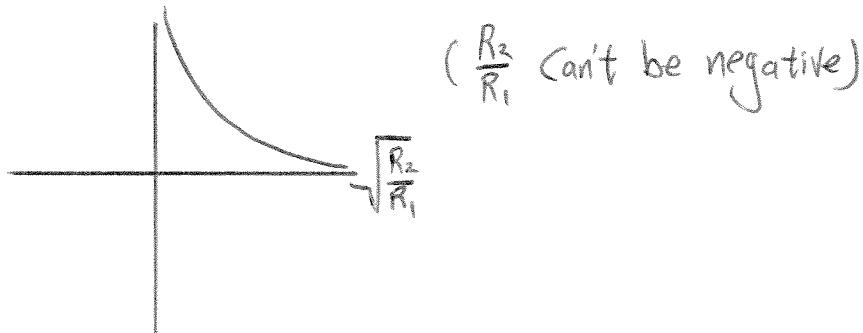


$$\text{Range: } 0 < Q < \infty$$

$$0 < \sqrt{\frac{R_2}{R_1}} < \infty$$

If the transfer function does not want to experience peaking, then $0 < Q \leq \frac{1}{\sqrt{2}} \Rightarrow 3.5356 \leq \sqrt{\frac{R_2}{R_1}} < \infty$

22.

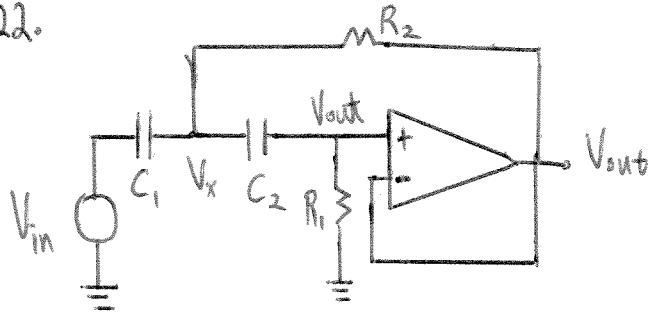

Assuming an ideal
OP amp.

$$1) (V_x - V_{in})C_1s + (V_x - V_{out})(C_2s + \frac{1}{R_2}) = 0, \text{ nodal equation at } V_x.$$

$$2) (V_x - V_{out})C_2s - \frac{V_{out}}{R_1} = 0, \text{ nodal equation at } V_{out}.$$

$$3) \Rightarrow V_x = V_{out} \left[\frac{C_2s + \frac{1}{R_1}}{C_2s} \right] \quad (A)$$

The stuff in the bracket becomes "A"

$$1) \Rightarrow (AV_{out} - V_{in})C_1s + (AV_{out} - V_{out})\left[C_2s + \frac{1}{R_2}\right] = 0$$

$$\Rightarrow AV_{out}C_1s + V_{out}(A-1)\left(C_2s + \frac{1}{R_2}\right) = V_{in}C_1s$$

$$A-1 = \frac{1}{R_1 C_2 s}, \quad A = \frac{C_2 s + \frac{1}{R_1}}{C_2 s}$$

Substitute $(A-1)$ and A into 1) \Rightarrow

$$\left(\frac{C_2 s + \frac{1}{R_1}}{C_2 s} \right) C_1 s V_{out} + \left(C_2 s + \frac{1}{R_2} \right) \frac{1}{R_1 C_2 s} V_{out} = V_{in} C_1 s$$

22.

$$\frac{V_{out}}{V_{in}} = \frac{\frac{C_1 S}{C_2} \left(C_2 S + \frac{1}{R_1} \right) + \frac{1}{R_1 C_2 S} \left(C_2 S + \frac{1}{R_2} \right)}{\frac{C_1}{C_2} \left(C_2 S + \frac{1}{R_1} \right) + \frac{1}{R_1 C_2 S} \left(C_2 S + \frac{1}{R_2} \right)}$$

Rearranging

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{s^2}{s^2 + \left(\frac{C_1 + C_2}{C_2 R_1 C_1} \right) s + \frac{1}{R_2 C_2 R_1 C_1}}$$

$$\omega_n^2 = \frac{1}{R_2 C_2 R_1 C_1}, \quad \frac{\omega_n}{Q} = \frac{C_1 + C_2}{C_2 R_1 C_1}$$

$$\omega_n = \frac{1}{\sqrt{R_2 C_2 R_1 C_1}}, \quad Q = \sqrt{\frac{C_2 C_1 R_1}{R_2}} \left(\frac{1}{C_1 + C_2} \right)$$

23.

$$Q = \frac{1}{C_1 + C_2} \sqrt{\frac{C_2 C_1 R_1}{R_2}} \Rightarrow \frac{1}{Q} = (C_1 + C_2) \sqrt{\frac{R_2}{C_2 C_1 R_1}}$$

$$1) \frac{d\left[\frac{1}{Q}\right]}{dQ} = -\frac{1}{Q^2} \Rightarrow d\left[\frac{1}{Q}\right] = -\frac{1}{Q^2} dQ$$

$$2) \frac{d\left[\frac{1}{Q}\right]}{dR_2} = \frac{1}{2} \frac{C_1 + C_2}{\sqrt{C_2 C_1 R_1 R_2}} \Rightarrow d\left[\frac{1}{Q}\right] = \frac{1}{2} \frac{C_1 + C_2}{\sqrt{C_2 C_1 R_1 R_2}} dR_2$$

Equating 1) and 2) and multiply 2) by $\frac{R_2}{R_2}$

$$-\frac{dQ}{Q^2} = \frac{1}{2} \frac{(C_1 + C_2) R_2}{\sqrt{C_2 C_1 R_1 R_2}} \frac{dR_2}{R_2}$$

$$\frac{dQ}{Q} / \frac{dR_2}{R_2} = -\frac{Q(C_1 + C_2)}{2} \sqrt{\frac{R_2}{C_1 C_2 R_1}}$$

$$S_{R_2}^Q = -\frac{Q(C_1 + C_2)}{2} \sqrt{\frac{R_2}{C_1 C_2 R_1}} = -\frac{1}{2}$$

$$\frac{1}{Q} = (C_1 + C_2) \sqrt{\frac{R_2}{C_2 C_1 R_1}} = C_1 \sqrt{\frac{R_2}{C_2 C_1 R_1}} + C_2 \sqrt{\frac{R_2}{C_2 C_1 R_1}}$$

$$\frac{\partial(\frac{1}{Q})}{\partial C_1} = \frac{1}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} - \frac{C_2}{2C_1} \sqrt{\frac{R_2}{C_2 R_1 C_1}}, \frac{d(\frac{1}{Q})}{dQ} = -\frac{1}{Q^2}$$

$$\text{Rearranging} \Rightarrow -\frac{\partial Q}{Q^2} = \frac{\partial C_1}{C_1} \left(\frac{C_1 - C_2}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

$$\frac{\partial Q}{Q} / \frac{\partial C_1}{C_1} = S_{C_1}^Q = -Q \left(\frac{C_1 - C_2}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

23.

Similarly:

$$S_{C_2}^Q = -Q \left(\frac{C_2 - C_1}{2} - \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

$$S_{R_1}^Q = Q \left(\frac{C_1 + C_2}{2} - \sqrt{\frac{R_2}{C_2 C_1 R_1}} \right) = \frac{1}{2}$$

24.

$$\frac{V_{out}(s)}{V_{in}} = \frac{\alpha s^2}{s^2 + \frac{\omega_n s + \omega_n^2}{Q}}$$


Cross-multiply.

$$V_{out} s^2 + V_{out} \frac{\omega_n s}{Q} + V_{out} \omega_n^2 = V_{in} \alpha s^2$$

Rearranging

$$V_{out} = V_{in} \frac{\alpha s^2}{\omega_n^2} - V_{out} \frac{s^2}{\omega_n^2} - V_{out} \frac{s}{Q \omega_n}$$

Block diagram:

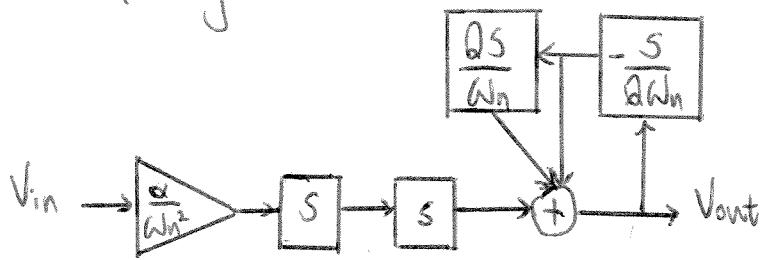

25.

$$Q=2, \omega_n = (2\pi)(2 \times 10^6)$$

$$R_6 = R_3, R_1 = R_2, C_1 = C_2$$

$$10 \text{ pF} < \text{Total } C < 1 \text{ nF}, 1 \text{ k}\Omega < \text{Total } R < 50 \text{ k}\Omega$$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left(\frac{1}{R_1 C_1} \right), \quad \omega_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\text{Since } R_6 = R_3 \Rightarrow \omega_n^2 = \left(\frac{1}{R_1 C_1} \right)^2 = (2\pi \times 2 \times 10^6)^2$$

$$\frac{1}{R_1 C_1} = 2\pi \times 2 \times 10^6 = \omega_n$$

$$Q = \frac{R_4 + R_5}{R_4} = 2 \Rightarrow R_5 = R_4$$

$$\text{Let } C_1 = C_2 = 100 \text{ pF}, \quad R_1 = \frac{1}{(2\pi)(2 \times 10^6)(100 \text{ pF})} = 795.77 \Omega$$

$$\text{So } R_1 = R_2 = 795.77 \Omega, \quad C_1 = C_2 = 100 \text{ pF}.$$

Since R_3, R_4, R_5, R_6 don't affect Q and ω_n ,
let them be 500Ω each.

$$\text{Total } R: (4)(500) + (2)(795.77) = 3.6 \text{ k}\Omega$$

$$\text{Total } C: 100 \text{ pF} + 100 \text{ pF} = 200 \text{ pF}.$$

26.

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \cdot \frac{1}{R_1 C_1}, \quad \omega_n^2 = \frac{R_6}{R_3} \cdot \frac{1}{R_1 R_2 C_1 C_2}$$


$$Q = \omega_n \left(\frac{R_4 + R_5}{R_4} \right) R_1 C_1, \quad \omega_n = \sqrt{\frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right)}$$

$$Q = \sqrt{\frac{R_6}{R_3}} \left(\frac{1}{R_1 R_2 C_1 C_2} \right) \left(\frac{R_4 + R_5}{R_4} \right) R_1 C_1$$

$$Q = \sqrt{\frac{R_6}{R_3}} \sqrt{\frac{R_1 C_1}{R_2 C_2}} \left(\frac{R_4 + R_5}{R_4} \right)$$

If $R_6 = R_3$, Q doesn't depend on R_6 and R_3 ,
hence zero sensitivity.

27.

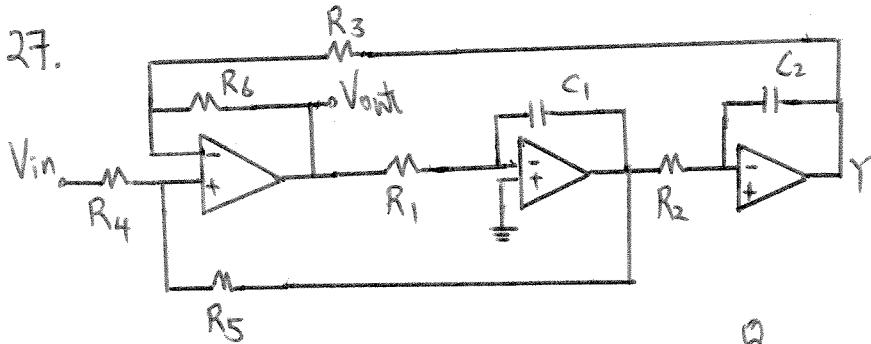

Low Pass, low freq gain of 2. $S_{R_3, R_6}^Q = 0$

$$\frac{V_Y}{V_{in}} = \left(\frac{\alpha s^2}{s^2 + \omega_n s + \omega_n^2} \right) \left(\frac{1}{R_1 R_2 C_1 C_2 s^2} \right) \quad \text{Low pass transfer function}$$

$$\text{Low freq gain: } \frac{\alpha}{\omega_n^2 R_1 R_2 C_1 C_2}, \text{ where } \alpha = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3} \right)$$

$$\text{and } \omega_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\text{Therefore, Low freq gain: } \frac{\alpha}{\frac{R_6}{R_3}} = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3} \right) \left(\frac{R_3}{R_6} \right)$$

$$S_{R_3, R_6}^Q = \frac{Q}{2} \frac{|R_3 - R_6|}{1 + R_5/R_4} \sqrt{\frac{R_2 C_2}{R_3 R_6 R_1 C_1}}$$

To obtain $S_{R_3, R_6}^Q = 0$, $R_3 = R_6$, however this makes the low freq gain: $2 \left(\frac{R_5}{R_4 + R_5} \right) \neq 2$.

Therefore, it's impossible a low freq gain of 2 if $S_{R_3, R_6}^Q = 0$.

28.

Peaking: 1 dB, $R_3 = R_6$

Normalized Peak Value: $\frac{\omega_n}{\sqrt{1-(4Q^2)^{-1}}} = 1.1$

Solving for Q^2 : $0.8570, 0.3880 \leftarrow$ (not possible for peaking)

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4+R_5} \left(\frac{1}{R_1 C_1} \right), \quad \left(\frac{\omega_n}{Q} \right)^2 = \left(\frac{R_4}{R_4+R_5} \right)^2 \left(\frac{1}{R_1 C_1} \right)^2$$

$$\omega_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right) = \frac{1}{R_1 R_2 C_1 C_2} \quad (\text{since } R_6 = R_3)$$

$$\text{Therefore, } Q^2 = \left(\frac{R_1 C_1}{R_2 C_2} \right) \left(\frac{R_4+R_5}{R_4} \right)^2 = 0.8570$$


$$\text{Low pass gain: } 2 \frac{R_5}{R_4+R_5} = \alpha \quad (\text{since } R_6 = R_3)$$

$$\text{So } \frac{\alpha}{2} = \frac{R_5}{R_4+R_5}, \quad \frac{R_4}{R_4+R_5} = 1 - \frac{\alpha}{2} \Rightarrow \frac{R_4+R_5}{R_4} = \left(1 - \frac{\alpha}{2} \right)^{-1}$$

$$\text{So } \left(\frac{R_1 C_1}{R_2 C_2} \right) \left(1 - \frac{\alpha}{2} \right)^2 = 0.8570, \quad \text{if } \alpha = 1 \Rightarrow \frac{R_1 C_1}{R_2 C_2} = 0.214.$$

However, can't go down any further without knowing more information.

29.

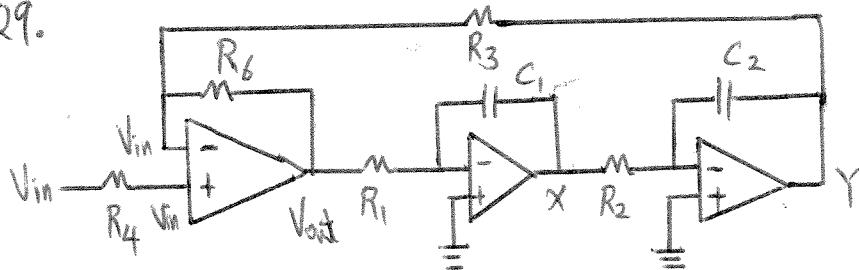

$$V_x = -\frac{V_{out}}{R_1} \left(\frac{1}{C_1 s} \right), \quad V_y = -\frac{V_x}{R_2} \left(\frac{1}{C_2 s} \right), \quad V_{out} = V_{in} - \frac{(V_y - V_{in}) R_6}{R_3}$$

$$\text{Substituting } V_x \text{ into } V_y \Rightarrow V_y = \frac{V_{out}}{R_1} \left(\frac{1}{C_1 s} \right) \left(\frac{1}{R_2 C_2 s} \right)$$

Substituting V_y into V_{out} and rearranging:

$$\frac{V_{out}}{V_{in}} = \frac{(R_1 C_1)(R_2 C_2) s^2 \left(1 + \frac{R_6}{R_3} \right)}{(R_1 C_1)(R_2 C_2) s^2 + \frac{R_6}{R_3}}$$

Simplifying


$$\frac{V_{out}}{V_{in}} = \frac{s^2 \left(1 + \frac{R_6}{R_3} \right)}{s^2 + \frac{R_6}{R_3} \left(\frac{1}{R_1 C_1 R_2 C_2} \right)}$$

$$\omega_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 C_1 R_2 C_2} \right), \quad Q = \infty$$

$$\alpha = \left(1 + \frac{R_6}{R_3} \right)$$

30.

Tow-Thomas Biquad:

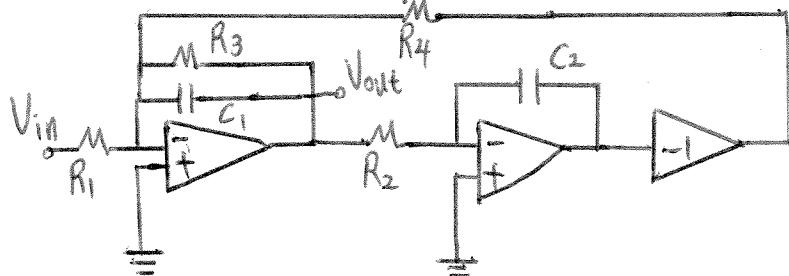

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q^{-1} = \frac{1}{R_3} \sqrt{\frac{R_2 R_4 C_2}{C_1}}$$

$$\frac{\partial \omega_n}{\partial R_2} = -\frac{1}{2} \frac{1}{R_2 \sqrt{R_2 R_4 C_1 C_2}} = -\frac{1}{2} \frac{\omega_n}{R_2}$$

$$\frac{\partial \omega_n}{\omega_n} / \frac{\partial R_2}{R_2} = S_{R_2}^{\omega_n} = -\frac{1}{2}$$

Since R_2, R_4, C_1, C_2 are equivalent in ω_n 's definition,
all of their sensitivities = $-\frac{1}{2}$

Sensitivities of Q :

$$\frac{\partial Q}{\partial R_3} = \sqrt{\frac{C_1}{R_2 R_4 C_2}} \left(\frac{R_3}{R_3} \right) \Rightarrow \frac{\partial Q}{Q} = \frac{\partial R_3}{R_3} \Rightarrow S_{R_3}^Q = 1$$

$$\frac{\partial Q}{\partial C_1} = \frac{1}{2} R_3 \left(\frac{C_1}{R_2 R_4 C_2} \right)^{\frac{1}{2}} \left(\frac{1}{R_2 R_4 C_2} \right) \frac{C_1}{C_1} \Rightarrow \frac{\partial Q}{Q} = \frac{1}{2} \frac{\partial C_1}{C_1} \Rightarrow S_{C_1}^Q = \frac{1}{2}$$

$$\frac{\partial Q}{\partial R_2} = -\frac{1}{2} R_3 \left(\frac{C_1}{R_2 R_4 C_2} \right)^{\frac{1}{2}} \frac{C_1}{R_4 C_2} \left(\frac{1}{R_2^2} \right) \Rightarrow \frac{\partial Q}{Q} = -\frac{1}{2} \frac{\partial R_2}{R_2} \Rightarrow S_{R_2}^Q = -\frac{1}{2}$$

30.

Since R_2 , R_4 and C_2 are equivalent in the expression


$$S_{R_2, R_4, C_2}^Q = -\frac{1}{2}$$

$$\text{so, } S_{R_2, R_4, C_1, C_2}^{W_n} = -\frac{1}{2}, \quad S_{R_1, R_3}^{W_n} = 0$$

$$S_{R_2, R_4, C_2}^Q = -\frac{1}{2}, \quad S_{C_1}^Q = \frac{1}{2}, \quad S_{R_3}^Q = 1$$

$$S_{R_1}^Q = 0$$

31.

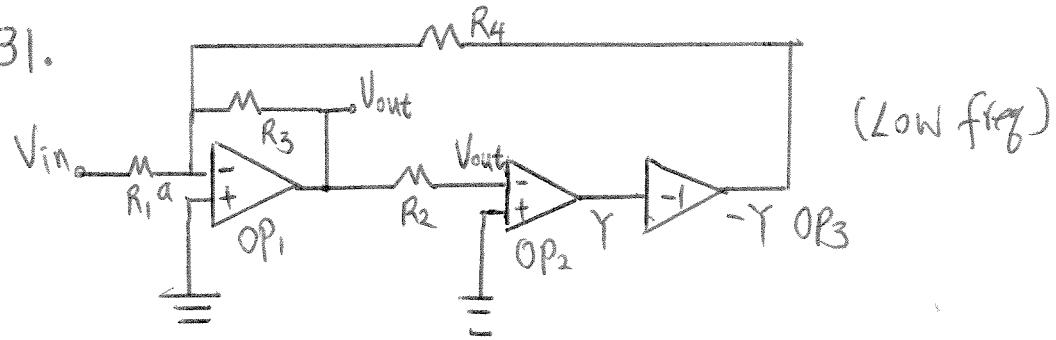

V_{out} equals zero because of OP_2 's negative feedback.

Likewise, V_a equals to zero as well.

So, summing all the currents thru R_3 , we have

$$-\left(\frac{0-V_Y}{R_4} + \frac{V_{in}}{R_1}\right)R_3 = V_{out} = 0$$

$$\Rightarrow \frac{V_{in}}{R_1} = \frac{V_Y}{R_4} \Rightarrow \frac{V_Y}{V_{in}} = \frac{R_4}{R_1}$$

32.

$$\frac{V_Y}{V_{IN}} = \frac{R_3 R_4}{R_1} \left(\frac{1}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$

$$\omega_n = (2\pi)(10 \text{ MHz}), \quad R_3 = 1K, \quad R_2 = R_4, \quad C_1 = C_2$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = \frac{1}{R_3} \sqrt{\frac{R_2 R_4 C_2}{C_1}}$$

Peaking: 1dB

$$\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.1, \quad Q^2 = 0.8570$$

$$\omega_n = \frac{1}{\sqrt{(R_2 C_1)^2}} = (2\pi)(10 \times 10^6) \Rightarrow \frac{1}{R_2 C_1} = (2\pi)(10 \times 10^6)$$


$$\frac{1}{Q} = \frac{1}{1000} \sqrt{R_2^2} = \frac{1}{Q} = \frac{R_2}{1000} \Rightarrow R_2 = 1166.860 \text{ ohm}$$

$$R_2 = 1.2 \text{ k}\Omega$$

Solving for C_1 we have: $C_1 = 13.64 \text{ pF}$.

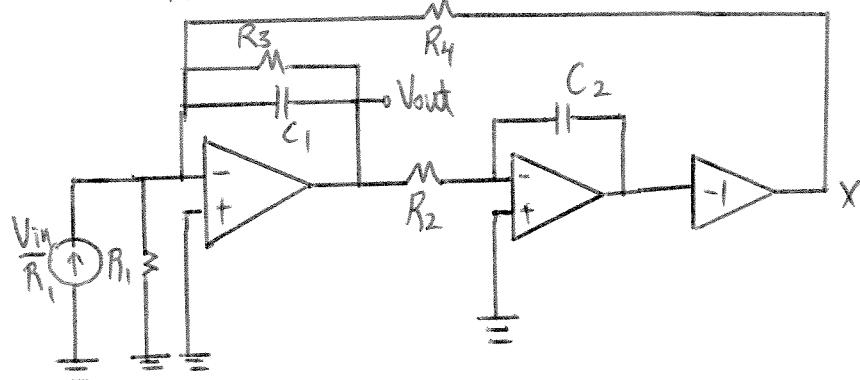33.

$$\frac{V_o}{V_{in}} = \frac{R_3 R_4}{R_1} \left(\frac{1}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$



When R_1 and V_{in} are replaced with its Norton equivalent, we see that the "upper" terminal of R_1 is at virtual ground. Since R_1 's two terminals are at the same potential, no current will flow through it, therefore it can be seen as an open. So R_1 is not in the signal path, and therefore will not affect the frequency response. However, since its magnitude is embedded in the Norton current source, it will affect the DC gain.

34.

$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} \quad (\text{for circuit diagram, please refer to Problem \# 35})$$

For Z_{in} to be inductive, the following combinations will work.

1 2 3

$$Z_5 = R$$

$$Z_4 = R$$

$$Z_3 = R$$

$$Z_2 = C$$

$$Z_1 = R$$

$$Z_5 = R$$

$$Z_4 = C$$

$$Z_3 = R$$

$$Z_2 = C$$

$$Z_1 = C$$

$$Z_5 = R$$

$$Z_4 = C$$


$$Z_3 = R$$

$$Z_2 = R$$

$$Z_1 = R$$

Any other combination will result in DC path blockage at a node. Moreover, in #2 it's assumed that the input can provide a DC bias.

35.

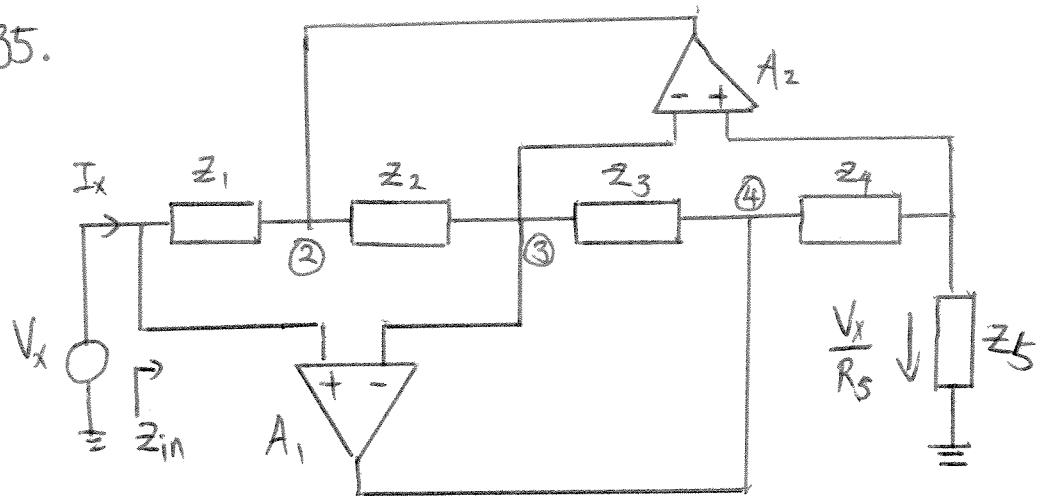

$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

For Z_{in} to be capacitive, the following combinations can be used.

<u>1</u>	<u>2</u>	<u>3</u>	<u>4</u>	<u>5</u>
----------	----------	----------	----------	----------

$Z_5 = C$	$Z_5 = C$	$Z_5 = R$	$Z_5 = R$	$Z_5 = R$
$Z_4 = R$	$Z_4 = R$	$Z_4 = R$	$Z_4 = R$	$Z_4 = C$
$Z_3 = R$	$Z_3 = R$	$Z_3 = R$	$Z_3 = C$	$Z_3 = C$
$Z_2 = R$	$Z_2 = C$	$Z_2 = R$	$Z_2 = R$	$Z_2 = R$
$Z_1 = R$	$Z_1 = C$	$Z_1 = C$	$Z_1 = R$	$Z_1 = C$

Any other combination results in a DC path blockage at a node. Moreover, in # 2, 3, 5, it is assumed that the input node will produce a DC bias.

36.

$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

$$Z_5 = R_x + \frac{1}{CS}, \quad Z_4 = R_x, \quad Z_3 = R_x, \quad Z_2 = R_x,$$

$$Z_1 = \frac{1}{CS}$$

$$Z_{in} = \frac{\frac{R_x}{CS} \left(R_x + \frac{1}{CS} \right)}{R_x^2} = \frac{1}{CS R_x} \left(R_x + \frac{1}{CS} \right)$$

$$Z_{in} = \frac{1}{CS} + \frac{1}{C^2 S^2 R_x}$$

$$V_{out} = \frac{V_{in} [S^2 [C^2 R_x] + CS]}{[S^2 [C^2 R_x] + SC + R_i [S^3 C^3 R_x]]}$$

$$\frac{V_{out}}{V_{in}} = \frac{SCR_x + 1}{S^2 R_i R_x C^2 + SCR_x + 1}$$

37.

$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} \quad (\text{for circuit diagram, please refer to problem # 35})$$

Let Z_5 be a capacitor, Z_2 and Z_4 be large resistors and Z_1 and Z_3 be small resistors compared to Z_2 and Z_4 .

For example, let Z_1 and Z_3 equal 50Ω and Z_2 and Z_4 equal $5\text{ k}\Omega$. Then there's a $(100)^2 = 10000$ multiplication factor onto C_5 .

38.

Butterworth filter: Roll-off of 1dB @ $\omega = 0.9\omega_0$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (0.9)^{2n}}} = 0.9 \Rightarrow 2n = \frac{\log(0.2345679)}{\log(0.9)}$$

$$n = 6.88$$

So we need a 7th order.

39.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (0.9)^{2n}}}$$

$$n=0 \Rightarrow -3 \text{ dB}$$

$$n=1 \Rightarrow -2.577 \text{ dB}$$

$$n=3 \Rightarrow -1.851 \text{ dB}$$

$$n=5 \Rightarrow -1.299 \text{ dB}$$


$$n=7 \Rightarrow -0.895 \text{ dB}$$

$$n=9 \Rightarrow -0.607 \text{ dB}$$

$$n=11 \Rightarrow -0.408 \text{ dB}$$

$$n=13 \Rightarrow -0.272 \text{ dB}$$

$$n=15 \Rightarrow -0.180 \text{ dB}$$

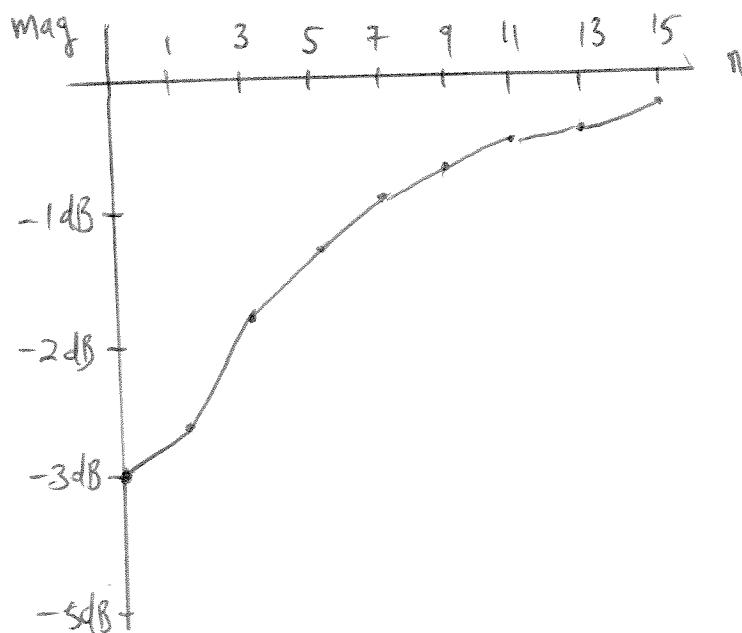

40.

$$1.1\omega_0$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (1.1)^{2n}}} = 0.1 \Rightarrow 2n = \frac{\log(99)}{\log(1.1)}$$

$$\omega = 24.106 \text{ so needs } n=25.$$

$$n=0 \Rightarrow -3 \text{ dB}$$

$$n=1 \Rightarrow -3.4439 \text{ dB}$$

$$n=3 \Rightarrow -4.427 \text{ dB}$$

$$n=5 \Rightarrow -5.555 \text{ dB}$$


$$n=7 \Rightarrow -6.810 \text{ dB}$$


$$n=9 \Rightarrow -8.169 \text{ dB}$$

$$n=11 \Rightarrow -9.61 \text{ dB}$$

$$n=13 \Rightarrow -11.112 \text{ dB}$$

$$n=15 \Rightarrow -12.66 \text{ dB}$$

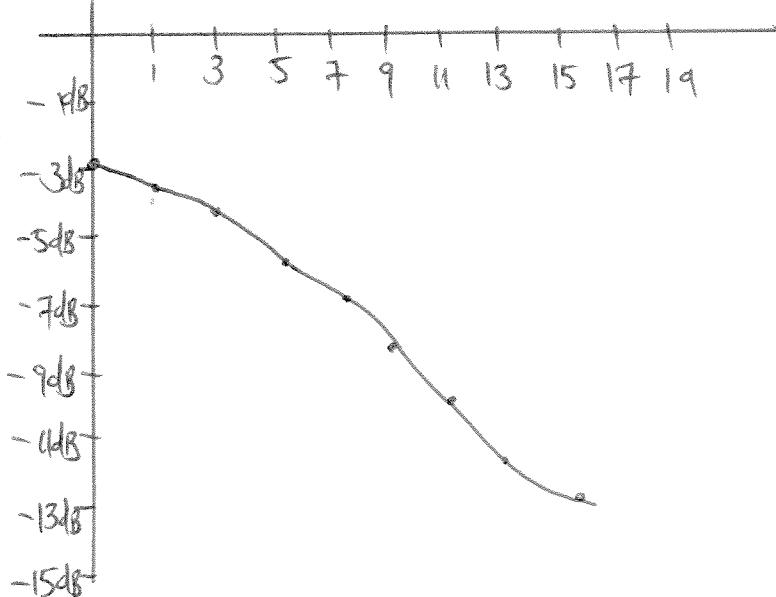

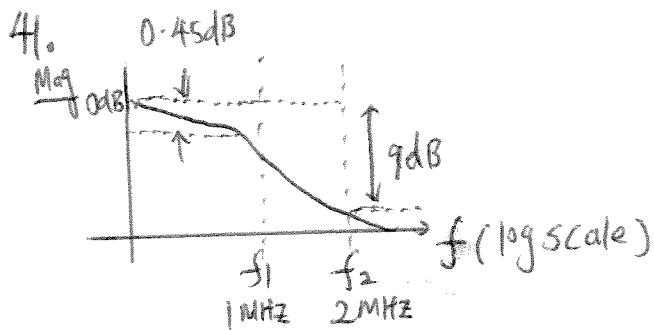

$$|H(f)| = \frac{1}{\left(1 + \left(\frac{2\pi f}{\omega_0}\right)^6\right)^{\frac{1}{2}}}$$

$$|H(5\text{MHz})| = 0.02438$$

$$\text{Suppression: } 20 \log(0.02438) = -32.26 \text{ dB}$$

42.

Low-pass Butterworth: Passband flatness of 0.5 dB

$f_1 = 1 \text{ MHz}$, $f_2 = 2 \text{ MHz}$, Order < 5

$$-0.5 \text{ dB} = 20 \log(x) \Rightarrow x = 0.944$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^{2n}}} = 0.944 \Rightarrow \frac{1}{\left(1 + \left(\frac{1}{f_0}\right)^{2n}\right)} = (0.944)^2$$

$$\Rightarrow 1 + \frac{1}{(f_0)^{2n}} = \frac{1}{(0.944)^2} \Rightarrow f_0 = 10^{\frac{0.9136}{2n}}$$

$$\text{for } n=1, \quad f_0 \approx 2.86 \text{ MHz}$$

$$\text{for } n=5, \quad f_0 \approx 1.234 \text{ MHz}$$

Therefore, for greatest attenuation $n=5$

$$\text{So } H(2 \text{ MHz}) = \frac{1}{\sqrt{1 + \left(\frac{2}{1.234}\right)^{10}}} = 0.089$$


$$20 \log(0.089) = -21.0 \text{ dB at } n=5$$

43.

$$P_k = \omega_0 \exp\left(\frac{j\pi}{2}\right) \exp\left(j\frac{2k-1}{2n}\pi\right), \quad k=1, 2, \dots, n$$

The poles lie on a circle because all of their magnitude, which is the distance from the origin to the poles, are the same (ω_0) with each k ; only the phase, which is the angle the poles make with the positive real axis, differ. Therefore, a circle is formed.

44.

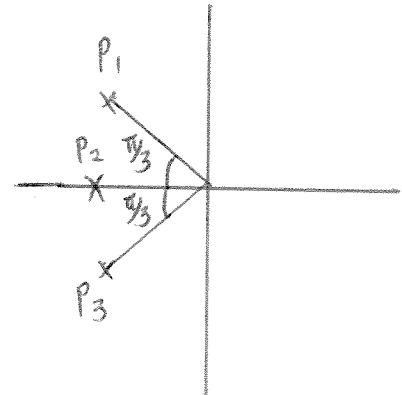

$$P_1 = 2\pi(1.45 \text{ MHz}) \left[\cos\left(\frac{2\pi}{3}\right) + j \sin\left(\frac{2\pi}{3}\right) \right]$$

$$P_2 = (2\pi)(1.45 \text{ MHz})$$

$$P_3 = (2\pi)(1.45 \text{ MHz}) \left[\cos\left(\frac{2\pi}{3}\right) - j \sin\left(\frac{2\pi}{3}\right) \right]$$

$$H(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{\left[2\pi(1.45 \text{ MHz})\right]^2}{s^2 - [4\pi(1.45 \text{ MHz}) \cos(2\pi/3)]s + [2\pi(1.45 \text{ MHz})]^2}$$

KHN Low pass Transfer function:

$$\frac{\alpha s^2}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2} \cdot \frac{1}{R_1 R_2 C_1 C_2 s^2} = \frac{\alpha / (R_1 R_2 C_1 C_2)}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}$$

$$\frac{\alpha}{R_1 R_2 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2, \quad \omega_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right) = [2\pi \times 1.45 \times 10^6]^2$$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left(\frac{1}{R_1 C_1} \right) = -(4\pi \times 1.45 \times 10^6 \times \cos(2\pi/3))$$

$$\frac{\alpha}{R_1 R_2 C_1 C_2} = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3} \right) \left(\frac{1}{R_1 R_2 C_1 C_2} \right)$$

Let $R_6 = R_3$, $R_2 = 4R_1$, $C_1 = C_2$

$$\omega_n^2 = \left(\frac{1}{4R_1 C_1} \right)^2 = (2\pi \times 1.45 \times 10^6)^2 \Rightarrow \frac{1}{2R_1 C_1} = 2\pi \times 1.45 \times 10^6$$

44.

Let $R_1 = 5K \Rightarrow C_1 = 10.98\text{pf}$, $R_2 = 20K$, $C_2 = 10.98\text{pf}$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left(\frac{1}{R_1 C_1} \right) = 9110618.7$$

$$\Rightarrow \frac{R_4}{R_4 + R_5} = \frac{1}{2}$$


$$\frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3} \right) \left(\frac{1}{R_1 R_2 C_1 C_2} \right) = \left(\frac{1}{2} \right) (2) (2\pi \times 1.45 \times 10^6)^2 = (2\pi \times 1.45 \times 10^6)^2$$

let R_5 and R_4 be $1K$ apiece.

so $R_5 = R_4 = R_6 = R_3 = 1K$

$R_1 = 5K$, $R_2 = 20K$

$C_1 = C_2 = 10.98\text{pf}$

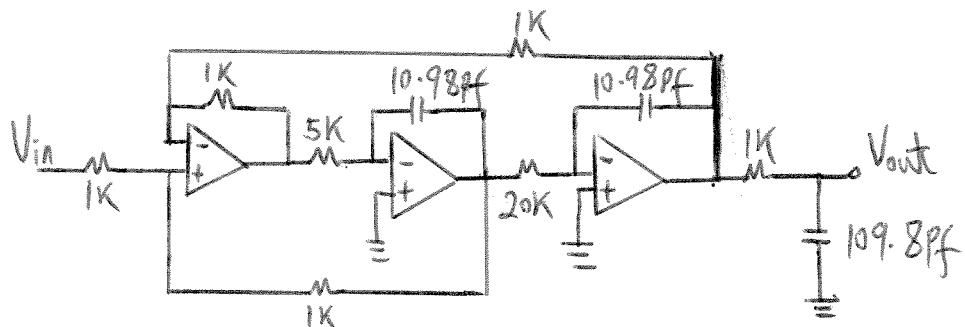

45.

To W-Thomas Biquad

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left(\frac{1}{R_2 R_3 R_4 C_1 C_2 s^2 + R_2 R_4 C_2 s + R_3} \right)$$

$$\frac{V_Y}{V_{in}} = \frac{1 / (R_1 R_2 C_1 C_2)}{s^2 + 1 / (R_3 C_1) s + 1 / (R_2 R_4 C_1 C_2)}$$

$$\frac{V_Y}{V_{in}} = \frac{(2\pi \times 1.45 \times 10^6)^2}{s^2 - (4\pi \times 1.45 \times 10^6 \times \cos(\frac{2\pi}{3}))s + (2\pi \times 1.45 \times 10^6)^2}$$


$$\frac{1}{R_1 R_2 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2, \quad \frac{1}{R_2 R_4 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2$$

$$\frac{1}{R_3 C_1} = 2\pi \times 1.45 \times 10^6$$

$$\text{Let } R_1 = R_2 = R_3 = R_4, \quad C_1 = C_2$$

$$\text{let } R_3 = 5K \Rightarrow C_1 = 21.95 \text{ pF}$$
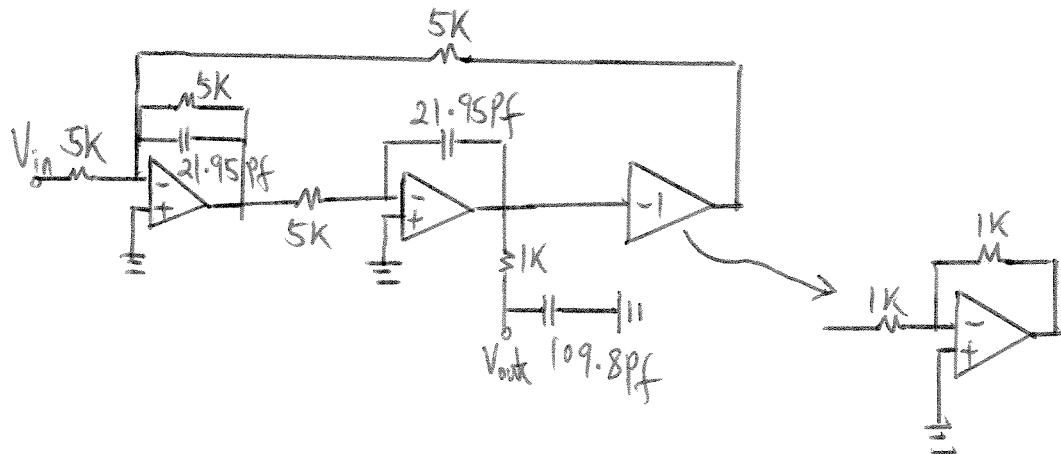
$$\text{so } R_1 = R_2 = R_3 = R_4 = 5K, \text{ and } C_1 = C_2 = 21.95 \text{ pF}$$



46.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2(\frac{\omega}{\omega_0})}} \quad n=4 \quad \epsilon = 0.2$$

$$C_n\left(\frac{\omega}{\omega_0}\right) = \cos\left(n \cos^{-1}\frac{\omega}{\omega_0}\right) = \cos\left(4 \cos^{-1}\frac{\omega}{\omega_0}\right)$$

$$C_n^2\left(\frac{\omega}{\omega_0}\right) = \cos^2\left(n \cos^{-1}\frac{\omega}{\omega_0}\right) = \frac{1}{2} \left(1 + \cos\left(2n \cos^{-1}\frac{\omega}{\omega_0}\right)\right)$$


$$2n \cos^{-1}\frac{\omega}{\omega_0} = \pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.924$$

$$2n \cos^{-1}\frac{\omega}{\omega_0} = 3\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.383$$


$$2n \cos^{-1}\frac{\omega}{\omega_0} = 0, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 1$$

$$2n \cos^{-1}\frac{\omega}{\omega_0} = 2\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.707$$

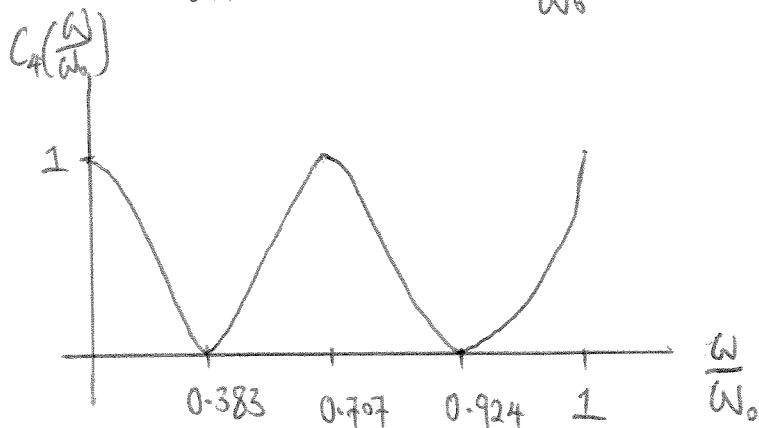
$$2n \cos^{-1}\frac{\omega}{\omega_0} = 4\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0$$



46.

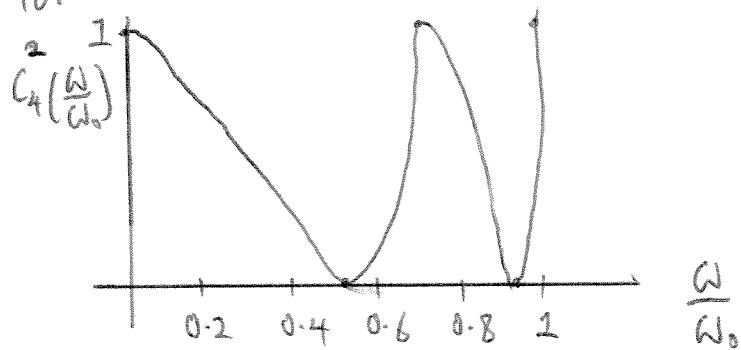
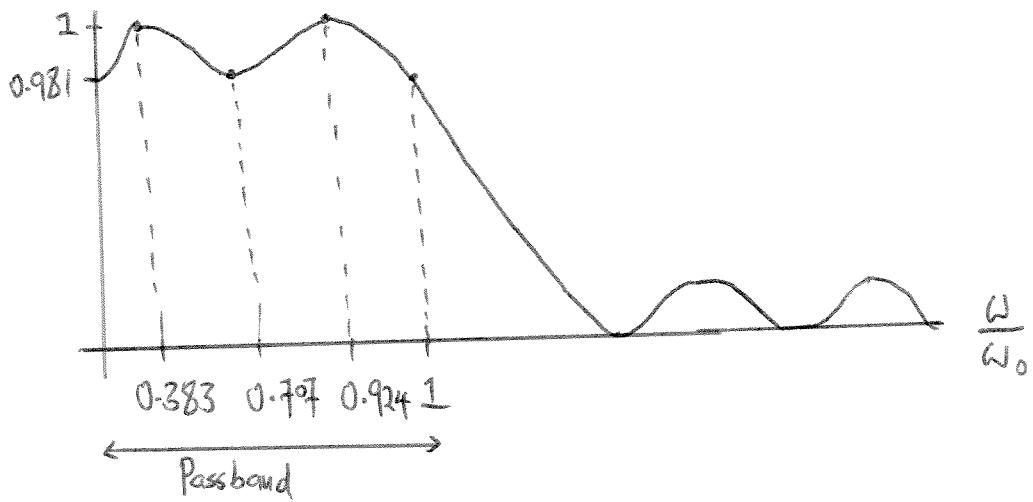
$$H(j\omega) = \frac{1}{\sqrt{1 + (0.2)^2 [C_4^2(\frac{\omega}{\omega_0})]}}$$



47. Chebyshev: 25 dB at 5 MHz.

$$n=5, \quad W_0 = 2 \text{ MHz}, \quad \frac{W}{W_0} = \frac{5}{2}$$

$$\sqrt{\frac{1}{1 + \epsilon^2 \cosh^2(n \cosh^{-1} \frac{5}{2})}} = -25 \text{ dB} = 0.056234$$

$$\Rightarrow \frac{1}{1 + \epsilon^2 (1.5939 \times 10^6)} = 0.003162277$$

$$\Rightarrow \epsilon^2 = 1.9777 \times 10^{-4}$$

\Rightarrow Minimum Ripple

$$\frac{1}{\sqrt{1 + (1.9777 \times 10^{-4})}} = 0.99990 = -8.6 \times 10^{-4} \text{ dB.}$$

$$48. \quad n=6$$

$$\cosh^2 \left(6 \cos^{-1} \left(\frac{5}{2} \right) \right) = 36590401$$

$$\frac{1}{\sqrt{1 + \epsilon^2 (36590401)}} = 0.056234$$

$$\epsilon^2 = 8.615 \times 10^{-6}$$

$$\text{Minimum Ripple} = \frac{1}{\sqrt{1 + 8.615 \times 10^{-6}}} = -3.74 \times 10^{-5} \text{ dB}$$

Smaller than when $n=5$.

$$49. \quad \epsilon = 0.509, \quad n = 4$$

$$P_{1,4} = -0.140\omega_0 \pm 0.983j\omega_0$$

$$P_{2,3} = -0.337\omega_0 \pm 0.407j\omega_0$$

$$H_{1,4}(s) = \frac{0.986\omega_0^2}{s^2 + 0.28\omega_0 s + 0.986\omega_0^2} = \frac{\alpha/(R_1 R_2 C_1 C_2)}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

$$Q = 3.55$$

$$\omega_0 = (2\pi)(4.965 \text{ MHz})$$

$$\omega_0^2 = [(2\pi)(4.965 \times 10^6)]^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\frac{\omega_0}{Q} = (0.28)(5 \text{ MHz})(2\pi) = (1.4 \text{ MHz})(2\pi) = \frac{R_4}{R_4 + R_5} \cdot \left(\frac{1}{R_1 C_1} \right)$$

$$\frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3} \right) \left(\frac{1}{R_1 R_2 C_1 C_2} \right) = \frac{R_6}{R_3} \left(\frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\Rightarrow \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3} \right) = \frac{R_6}{R_3}$$

$$\Rightarrow \frac{R_5}{R_4 + R_5} = \frac{\frac{R_6}{R_3}}{1 + \frac{R_6}{R_3}}$$

$$\Rightarrow 1 - \alpha = \frac{\frac{R_6}{R_3}}{1 + \frac{R_6}{R_3}}, \quad \alpha = \frac{R_4}{R_4 + R_5}$$

$$\Rightarrow \frac{R_6}{R_3} = \frac{1 - \alpha}{\alpha}$$

$$\text{Let } \alpha = 0.5 \Rightarrow \frac{R_6}{R_3} = 1$$

49.

$$\Rightarrow \omega_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 C_1 R_2 C_2} \right) = \frac{1}{R_1 C_1 R_2 C_2} \quad (*)$$

$$\text{Since } \frac{\omega_n}{\alpha} = \alpha \left(\frac{1}{R_1 C_1} \right) = 1.4 \times 10^6 \times 2\pi, \quad \alpha = 0.5$$

$$\Rightarrow \frac{1}{R_1 C_1} = 1.76 \times 10^7 \quad (1)$$

Consider (*)

$$\Rightarrow \frac{1}{R_2 C_2} = \omega_n^2 \cdot R_1 C_2 = 5.53 \times 10^7 \quad (2)$$

$R_6 = R_3 = R_5 = R_4 = 1K$. According to (1), (2), choose

$$R_1 = 5K, \quad C_1 = 11.368 \mu F$$

$$R_2 = 5K, \quad C_2 = 3.62 \mu F$$

$$\text{For } H_{2,3}(s) = \frac{\alpha 279 \omega_0^2}{s^2 + 0.674 \omega_0 s + 0.279 \omega_0^2}$$

$$\omega_n = (2\pi) (2.64 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = (2\pi) (0.674 \times 5 \times 10^6) = (2\pi) (3.37 \times 10^6)$$

$$\text{Let } \alpha = 0.5$$

$$49. \frac{W_n}{Q} = (\alpha) \left(\frac{1}{R_1 C_1} \right)$$

$$\Rightarrow \frac{1}{R_1 C_1} = \frac{W_n}{Q} \cdot \frac{1}{\alpha} = 4.23 \times 10^7 \quad (3)$$


$$\frac{R_6}{R_3} = 1, \quad W_n^2 = \frac{R_6}{R_3} \left(\frac{1}{R_1 C_1 R_2 C_2} \right) = \frac{1}{R_1 C_1 R_2 C_2}$$

$$\Rightarrow \frac{1}{R_2 C_2} = W_n^2 \cdot R_1 C_1 = 6.50 \times 10^6 \quad (4)$$

Consider (3) (4), choose

$$R_1 = 5k, \quad C_1 = 4.72pF; \quad R_2 = 5k, \quad C_2 = 30.78pF$$

$$R_6 = R_3 = R_5 = R_4 = 1k.$$

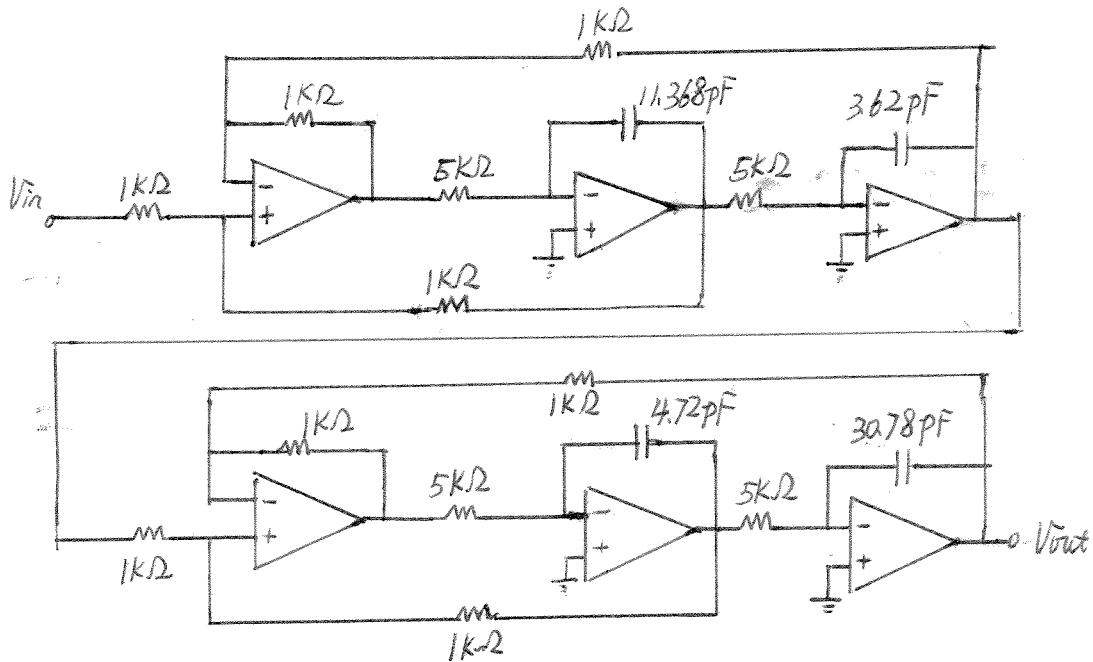

50. Tow Thomas

Low Pass Transfer Function

$$P_{1,4} = \frac{V_4}{V_{in}} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{S^2 + \frac{1}{R_3 C_1} S + \frac{1}{R_2 R_4 C_1 C_2}} = \frac{0.986 w_0^2}{S^2 + 0.28 w_0 S + 0.986 w_0^2}$$

$$\frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{R_2 R_4 C_1 C_2} = [(2\pi)(4.965 \times 10^6)]^2 \quad \textcircled{*}$$

$$\frac{1}{R_3 C_1} = 2\pi \times 1.4 \times 10^6$$

$$\text{Let } R_3 = 5K, \quad C_1 = 22.736 \mu F$$

$$\text{Let } C_1 = C_2, \quad C_2 = 22.736 \mu F$$

$$R_1 = R_2 \stackrel{+}{\Rightarrow} R_1 = R_2 = R_4 = 1.4K \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{for } P_{1,4}$$

$$R_3 = 5K, \quad C_1 = C_2 = 22.736 \mu F$$

$$P_{2,3} = \frac{0.279 w_0^2}{S^2 + 0.674 w_0 S + 0.279 w_0^2} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{S^2 + \frac{1}{R_3 C_1} S + \frac{1}{R_2 R_4 C_1 C_2}}$$


$$\frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{R_2 R_4 C_1 C_2} = [(2\pi)(2.64 \times 10^6)]^2 \quad \textcircled{**}$$

$$\frac{1}{R_3 C_1} = (2\pi)(3.37 \times 10^6)$$

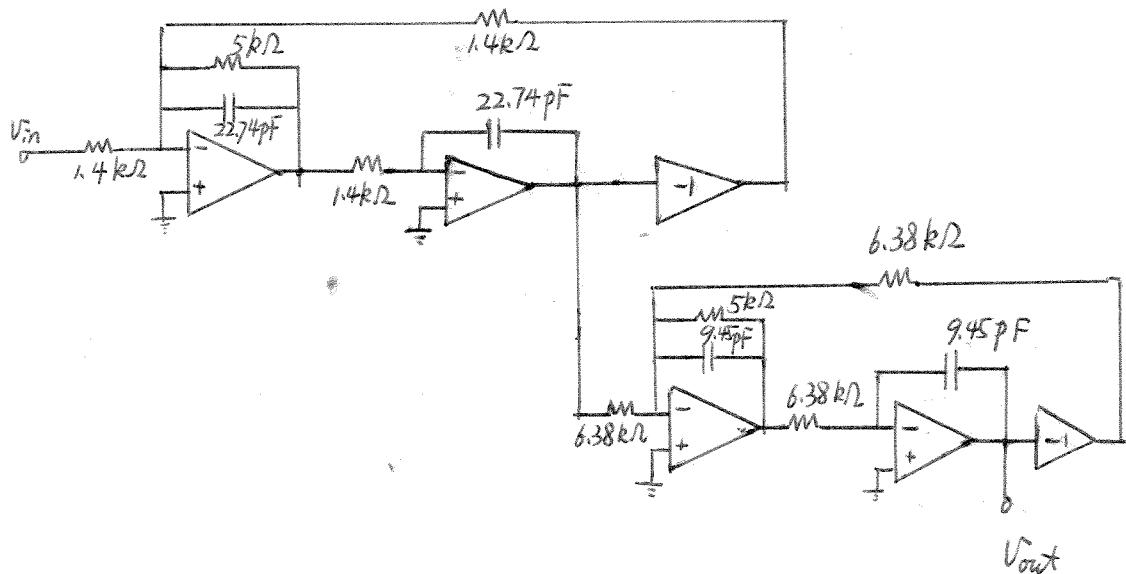
50. Let $R_3 = 5K$, $C = 9.45 pF$

Let $C_1 = C_2 = 9.45 pF$, $R_1 = R_2 \xrightarrow{*} R_1 = R_2 = R_4 = 6.38 K$.

For $P_{1,4}$. $\left\{ \begin{array}{l} R_1 = R_2 = R_4 = 6.38 K, R_3 = 5K \\ C_1 = C_2 = 9.45 pF \end{array} \right.$




51.

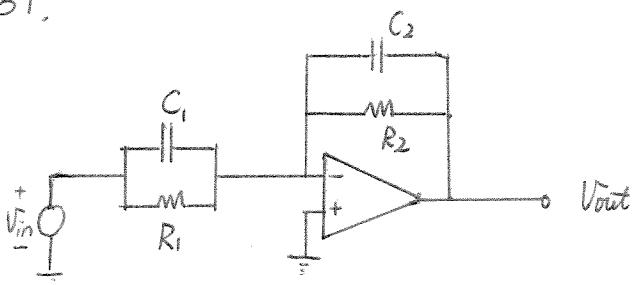

High pass, 1 MHz \Rightarrow 10 dB attenuation

$f > 5 \text{ MHz}$, gain = 1

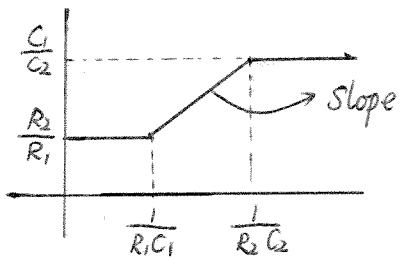

$$\frac{1}{R_2 C_2} = (5 \text{ MHz})(2\pi).$$

$$\text{Let } \frac{G}{C_2} = 1, \quad \frac{R_2}{R_1} = -10 \text{ dB} = 0.316$$


$$\text{So } \frac{1}{0.316} = 3.1623, \quad \frac{5 \text{ MHz}}{3.1623} = 1.58 \text{ MHz}$$

$$\Rightarrow \frac{1}{R_1 C_1} = (1.58 \text{ MHz})(2\pi)$$

$$\text{Choose } C_2 = 31.83 \text{ pF} \Rightarrow R_2 = 1 \text{ k}\Omega$$

$$C_1 = 31.83 \text{ pF} \Rightarrow R_1 = 3.16 \text{ k}\Omega$$

52.

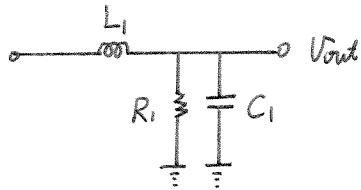

Peaking : 1 dB

bandwidth: 100 MHz

$$L_1 < 100 \text{nH}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{L_1 C_1}}{s^2 + \frac{1}{R_1 C_1} s + \frac{1}{L_1 C_1}} = \frac{r}{s^2 + \frac{w_h}{\alpha} s + w_h^2} \Big|_{s=jw} = \frac{r}{(jw)^2 + \frac{w_h}{\alpha} (jw) + w_h^2}$$

$$H(jw) = \frac{r}{(w_h^2 - w^2) + \frac{w_h}{\alpha} w j}$$

$$|H(jw)| = \frac{r}{\sqrt{(w_h^2 - w^2)^2 + (\frac{w_h}{\alpha} w)^2}}$$

$$\text{At } w_1, |H(jw_1)| = \frac{r}{\sqrt{(w_h^2 - w_1^2)^2 + (\frac{w_h}{\alpha} w_1)^2}} = \frac{r}{w_h \sqrt{2}}$$

$$\Rightarrow \sqrt{\frac{(w_h^2 - w_1^2)^2 + (\frac{w_h}{\alpha} w_1)^2}{w_h^4}} = \sqrt{2}.$$

$$\Rightarrow (w_h^2 - w_1^2)^2 + (\frac{w_h}{\alpha} w_1)^2 = 2w_h^4 \quad \textcircled{*}$$

$$\frac{\alpha}{\sqrt{1 - (4\alpha^2)^{-1}}} = 1.1 \Rightarrow \alpha = 0.9258, 0.5941 (< \frac{1}{\sqrt{2}}, \text{ can't produce peaking})$$

$$\text{So } \alpha = 0.9258.$$

$$\text{Solve } \textcircled{*} \text{ gives } w = \sqrt{1.5} w_h.$$

$$w = \sqrt{1.5} \frac{1}{\sqrt{L_1 C_1}} = (2\pi) (100 \times 10^6) \quad \textcircled{1}$$


52.

$$\frac{W_0}{Q} = \frac{1}{R_1 C_1} \Rightarrow Q = R_1 C_1 \frac{1}{\sqrt{4G}} = \underline{R_1 \sqrt{\frac{G}{L_1}}} = 0.9258 \quad (2)$$

$$\text{Let } L_1 = 90 \text{nH} \stackrel{(1)}{\Rightarrow} C_1 = 42.22 \text{pF} \stackrel{(2)}{\Rightarrow} R_1 = 42.74 \Omega.$$

53. $W_h = (2\pi)(50 \text{ MHz})$, $Q = 1.5$, Low frequency gain = 2.

$C = 10 \text{ pF}$ to 100 pF .

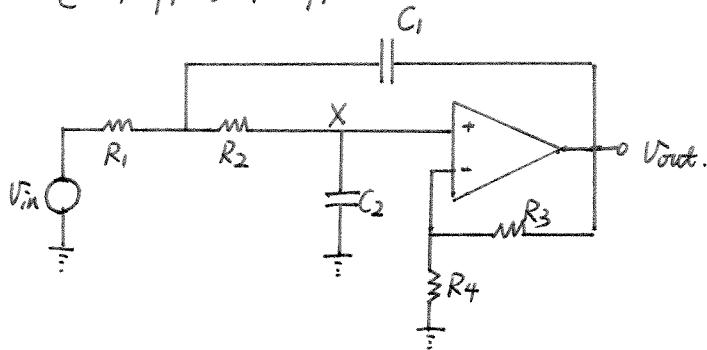

$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{R_3}{R_4}}{R_1 R_2 C_1 C_2 S^2 + (R_1 C_2 + R_2 C_2 - R_1 \frac{R_3}{R_4} C_1)S + 1}$$

$$= \frac{(1 + \frac{R_3}{R_4}) / (R_1 R_2 C_1 C_2)}{S^2 + (R_1 C_2 + R_2 C_2 - \frac{R_1 R_3}{R_4} C_1)S + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$W_h = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \frac{W_h}{Q} = \frac{R_1 C_2 + R_2 C_2 - R_1 \frac{R_3}{R_4} C_1}{R_1 R_2 C_1 C_2}$$

Low frequency gain $(1 + \frac{R_3}{R_4}) = 2$, Let $\frac{R_3}{R_4} = 1$.

$$\frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = W_h = (2\pi)(50 \times 10^6) \quad ①$$

$$R_1 C_2 + R_2 C_2 - R_1 C_1 = \frac{W_h}{Q} (R_1 R_2 C_1 C_2) = \frac{1}{(1.5)(2\pi)(50 \times 10^6)} \quad ②$$

Let $C_1 = C_2 = 10 \text{ pF}$

$$② \Rightarrow R_2 = \frac{1}{(1.5)(2\pi)(50 \times 10^6)} \cdot \frac{1}{C_2} = 212.2 \Omega$$

$$① \Rightarrow R_1 = \frac{1}{[(2\pi)^2 (50 \times 10^6)^2 \cdot R_2 C_1 C_2]} = 477.5 \Omega$$

Let $R_3 = R_4 = 1 \text{ k}\Omega$.

54. $W_{3dB} = (30 \times 10^6) / (2\zeta)$, gain = 2, sensitivities no greater than 1.

$$H(s) = \frac{K w_n^2}{s^2 + \frac{w_n}{\zeta} s + w_n^2}, \quad s = j\omega \Rightarrow$$

$$H(j\omega) = \frac{K w_n^2}{w_n^2 - \omega^2 + \frac{w_n}{\zeta} \omega j}$$

$$|H(j\omega)| = \frac{K w_n^2}{\sqrt{(w_n^2 - \omega^2)^2 + (\frac{w_n}{\zeta} \omega)^2}}$$

$$|H(j\omega)| = \frac{K}{\sqrt{2}} \Rightarrow \frac{w_n^2}{\sqrt{(w_n^2 - \omega^2)^2 + (\frac{w_n}{\zeta} \omega)^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow (w_n^2 - \omega^2)^2 + (\frac{w_n}{\zeta} \omega)^2 = 2w_n^4$$

$$\Rightarrow w_n^4 (1 - \frac{\omega^2}{w_n^2})^2 + w_n^4 \left[\left(\frac{1}{\zeta} \right)^2 \cdot \left(\frac{\omega}{w_n} \right)^2 \right] = 2w_n^4$$

$$\Rightarrow \left[1 - \left(\frac{\omega}{w_n} \right)^2 \right]^2 + \left(\frac{1}{\zeta} \right)^2 \left(\frac{\omega}{w_n} \right)^2 = 2$$

$$\Rightarrow \left(\frac{\omega}{w_n} \right)^4 + \left[\left(\frac{1}{\zeta} \right)^2 - 2 \right] \left(\frac{\omega}{w_n} \right)^2 - 1 = 0$$

$$S_{R_2, C_1, C_2, R_1}^{w_n} = -\frac{1}{2} \quad (\text{sensitivities of } w_n \text{ all } < 1)$$

$$S_{R_1}^Q = -S_{R_2}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}}$$

$$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q \left(\sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_1}{R_1 C_2}} \right) = \frac{1}{2} + Q \sqrt{\frac{R_1 C_2}{R_2 C_1}}$$

$$S_K^Q = Q K \sqrt{\frac{R_1 C_1}{R_2 C_2}} = 2 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

Let $\sqrt{\frac{R_1 C_1}{R_2 C_2}} = 1$, and $\alpha = \frac{1}{2}$,

$$S_K^\alpha = 2 \cdot \left(\frac{1}{2}\right) = 1, \quad S_G^\alpha = \frac{1}{2} + \frac{1}{2} = 1$$


$$S_{C_2}^\alpha = -1, \quad S_{R_1}^\alpha = -\frac{1}{2} + \frac{1}{2} = 0, \quad S_{R_2}^\alpha = 0$$

Since $\alpha = \frac{1}{2}$,

$$\left(\frac{w}{w_n}\right)^4 + 2 \left(\frac{w}{w_n}\right)^2 - 1 = 0$$

$$\Rightarrow \left(\frac{w}{w_n}\right)^2 = 0.4142$$

$$\Rightarrow w = \sqrt{0.4142} w_n.$$

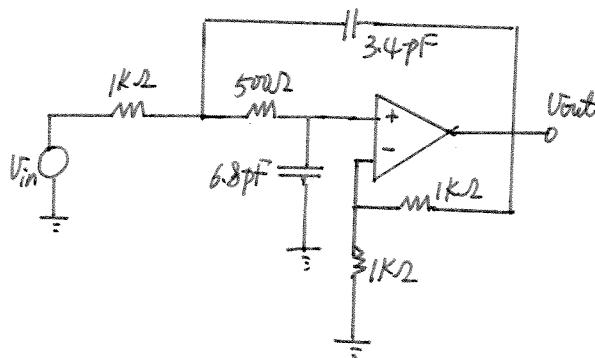

Since $R_1 C_1 = R_2 C_2$,

$$w_n = \frac{1}{\sqrt{(R_1 C_1)^2}} = \frac{1}{R_1 C_1}$$

$$\Rightarrow \sqrt{0.4142} w_n = \frac{\sqrt{0.4142}}{R_1 C_1} = (2\pi)(30 \times 10^6) \text{ rad/s}$$

$$\text{Also } \frac{1}{\alpha w_n} = R_1 C_2 + R_2 C_2 - R_1 C_1 = R_1 C_2 \quad \text{②}$$

$$\Rightarrow \frac{R_1 C_1}{R_1 C_2} = \frac{\frac{1}{w_n}}{\frac{1}{\alpha w_n}} = \alpha = \frac{1}{2}.$$

$$\Rightarrow \frac{C_1}{C_2} = \frac{1}{2}.$$

$$\text{Let } R_1 = 1k\Omega \stackrel{\text{①}}{\Rightarrow} C_1 = \frac{\sqrt{0.4142}}{(2\pi)(30 \times 10^6) \cdot R_1} = 3.4\text{pF}.$$


$$\Rightarrow C_2 = 2C_1 = 6.8\text{pF}.$$

$$\Rightarrow R_2 = R_1 \frac{C_1}{C_2} = 500\Omega.$$

And as before, $R_3 = R_4 = 1k\Omega$.

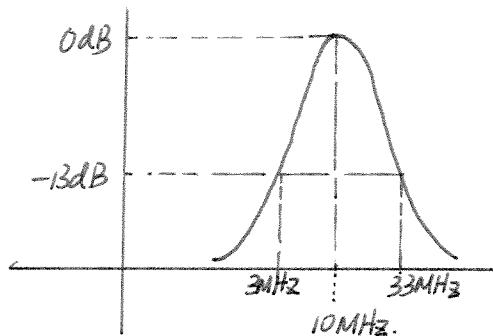55. 10 MHz, Gain = 1 (peak), $R_6 = R_3$, -13 dB @ 3 MHz, 33 MHz.

$$\frac{V_x}{V_{in}} = \frac{\alpha s^2}{s^2 + \frac{W_n}{Q} s + W_n^2} \cdot \frac{-1}{R_1 C_1 s}$$



$$1 = \left(\frac{\alpha}{R_1 C_1}\right) \cdot \frac{Q}{W_n}, \quad \alpha = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3}\right), \quad \frac{W_n}{Q} = \frac{R_4}{R_4 + R_5} \cdot \frac{1}{R_1 C_1}.$$

$$\text{since } R_6 = R_3, \quad \alpha = 2 \frac{R_5}{R_4 + R_5} \Rightarrow \frac{\alpha}{2} = \frac{R_5}{R_4 + R_5}$$

$$\Rightarrow \frac{R_4}{R_4 + R_5} = 1 - \frac{\alpha}{2} \Rightarrow \frac{Q}{W_n} = \frac{R_1 C_1}{1 - \frac{\alpha}{2}}$$

$$\Rightarrow \left(\frac{\alpha}{R_1 C_1}\right) \cdot \left(\frac{R_1 C_1}{1 - \frac{\alpha}{2}}\right) = 1 \Rightarrow \alpha = 1 - \frac{\alpha}{2}.$$

$$\Rightarrow \alpha = \frac{2}{3}, \quad \frac{R_5}{R_4 + R_5} = \frac{1}{3}$$

$$\Rightarrow R_5 = \frac{1}{2} R_4.$$

$$\left. \begin{aligned} \frac{W_n}{Q} &= \left(\frac{2}{3}\right) \left(\frac{1}{R_1 C_1}\right) \\ W_n &= \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \end{aligned} \right\} \Rightarrow \frac{3}{2} \frac{R_1 C_1}{\sqrt{R_1 R_2 C_1 C_2}} = Q$$

$$\Rightarrow \frac{3}{2} \frac{\sqrt{R_1 C_1}}{R_2 C_2} = Q$$

$$\text{Let } R_1 C_1 = R_2 C_2 \Rightarrow Q = \frac{3}{2}, \quad W_n = \frac{1}{R_1 C_1}.$$

$$H(j\omega) = \frac{\frac{2}{3}w^2}{\frac{w}{w_n} \sqrt{(w_n^2 - w^2)^2 + (\frac{2}{3}whw)^2}} = \frac{\frac{2}{3}w^2}{\frac{w}{w_n} \sqrt{w_n^4 - \frac{14}{9}(w_n w)^2 + w^4}}$$

$$H(j\omega) = 1$$

$$\Rightarrow \frac{4}{9}w^2 = w_n^2 - \frac{14}{9}w^2 + \frac{w^4}{w_n^2}$$

$$\Rightarrow w_n^4 - 2w^2w_n^2 + w^4 = 0$$

$$\Rightarrow w_n^2 = w^2 = [(2\pi)(10\text{MHz})]^2$$


As derived, $w_n = \frac{1}{R_1 C_1}$

Let $R_1 = 5\text{k}\Omega \Rightarrow C_1 = 3.183\text{ pF}$.


Let $R_2 = R_1 = 5\text{k}\Omega \Rightarrow C_2 = C_1 = 3.183\text{ pF}$

Let $R_4 = 5\text{k}\Omega \Rightarrow R_5 = \frac{1}{2}R_4 = 2.5\text{k}\Omega$.

Let $R_3 = R_6 = 1\text{k}\Omega$.

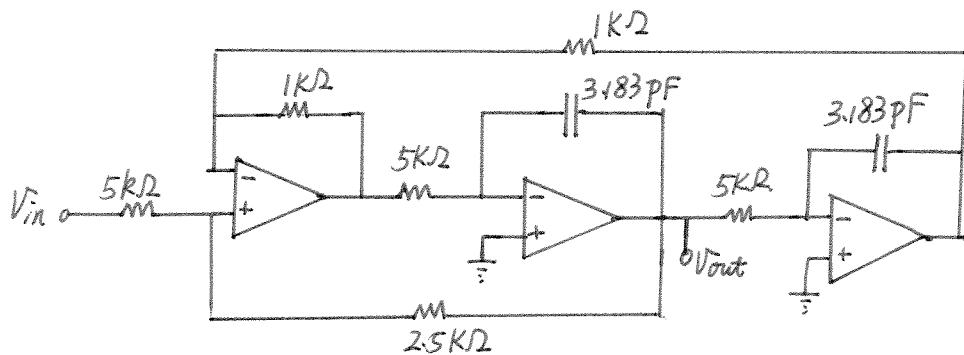

56.

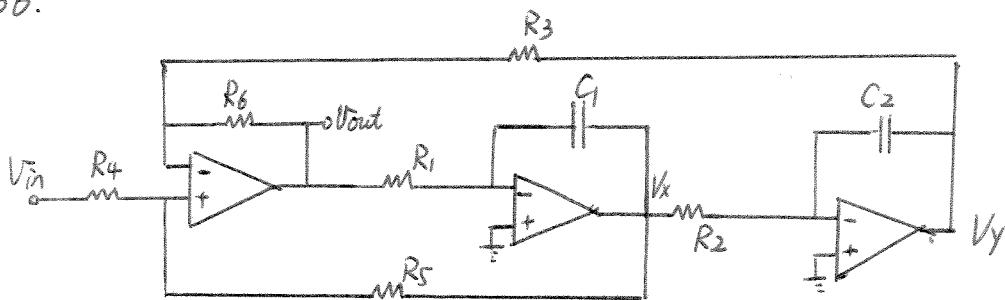

$$\text{Low pass, } \frac{V_y}{V_{in}} = \frac{\alpha s^2}{s^2 + \frac{w_h}{\alpha} s + w_h^2} \cdot \frac{1}{R_1 R_2 C_1 C_2 s^2}$$

$$= \frac{\alpha}{(s^2 + \frac{w_h}{\alpha} s + w_h^2)(R_1 R_2 C_1 C_2)}$$

$$H(s) = \frac{\alpha / (R_1 R_2 C_1 C_2)}{s^2 + \frac{w_h}{\alpha} s + w_h^2}$$

$$H(j\omega) = \frac{\alpha / (R_1 R_2 C_1 C_2)}{(w_h^2 - \omega^2) + j \frac{w_h}{\alpha} \omega}$$

$$|H(j\omega)| = \frac{\alpha / (R_1 R_2 C_1 C_2)}{\sqrt{(w_h^2 - \omega^2)^2 + (\frac{w_h \omega}{\alpha})^2}}$$

$$|H(j\omega_{3dB})| = \frac{\alpha / (R_1 R_2 C_1 C_2)}{\sqrt{(w_h^2 - \omega_{3dB}^2)^2 + (\frac{w_h \omega_{3dB}}{\alpha})^2}} = \frac{\alpha}{w_h^2 (R_1 R_2 C_1 C_2) \sqrt{2}}$$

$$\Rightarrow \frac{\sqrt{(w_h^2 - \omega_{3dB}^2)^2 + (\frac{w_h \omega_{3dB}}{\alpha})^2}}{w_h^2} = \sqrt{2}$$

$$\Rightarrow 1 - 2 \left(\frac{\omega_{3dB}}{w_h} \right)^2 + \left(\frac{\omega_{3dB}}{w_h} \right)^4 + \frac{1}{\alpha^2} \left(\frac{\omega_{3dB}}{w_h} \right)^2 = 2$$

$$\Rightarrow \left(\frac{W_{3dB}}{W_h}\right)^4 + \left(\frac{1}{Q^2} - 2\right) \left(\frac{W_{3dB}}{W_h}\right)^2 - 1 = 0$$

$$Q = 1.5 \Rightarrow \left(\frac{W_{3dB}}{W_h}\right)^4 - 1.556 \left(\frac{W_{3dB}}{W_h}\right)^2 - 1 = 0$$

$$\Rightarrow \left(\frac{W_{3dB}}{W_h}\right)^2 = 2.0446, \quad -0.4891 \text{ (impossible)}$$

$$\Rightarrow W_{3dB} = 1.43 W_h$$

$$\Rightarrow \text{Low pass corner} = 14.3 \text{ MHz.}$$

High pass:

$$\frac{V_{out}}{V_{in}}(s) = \frac{\alpha s^2}{s^2 + \frac{W_h}{Q}s + W_h^2}$$

$$|H(jw)| = \frac{\alpha w^2}{\sqrt{(W_h^2 - w^2)^2 + \left(\frac{W_h w}{Q}\right)^2}}$$

$$|H(jW_{3dB})| = \frac{\alpha W_{3dB}^2}{\sqrt{(W_h^2 - W_{3dB}^2)^2 + \left(\frac{W_{3dB} W_h}{Q}\right)^2}} = \frac{\alpha}{\sqrt{2}}$$


$$\Rightarrow \left(\frac{W_h}{W_{3dB}}\right)^4 + \left(\frac{1}{Q^2} - 2\right) \left(\frac{W_h}{W_{3dB}}\right)^2 - 1 = 0$$

$$\text{Since } Q = 1.5$$

$$\Rightarrow \left(\frac{W_h}{W_{3dB}}\right)^2 = 2.0446 \Rightarrow W_{3dB} = \frac{W_h}{1.43}$$

$$\Rightarrow W_{3dB} = 7 \text{ MHz. (high pass corner)}$$

57.

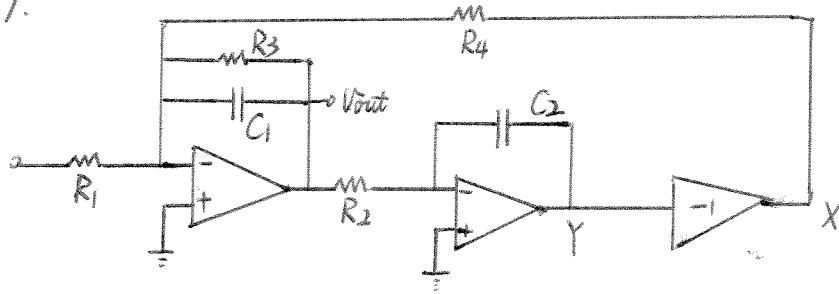

$$\omega_n = 10 \text{ MHz},$$

$$-13 \text{ dB} = 3 \text{ MHz},$$

$$33 \text{ MHz}.$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_2 R_3 R_4}{R_1} \left(\frac{C_2 s}{R_2 R_3 R_4 C_1 C_2 s^2 + R_2 R_4 C_2 s + R_3} \right)$$

$$\text{Same as in } \#55, \quad Q = \frac{10}{6.684} = 1.5.$$

$$\frac{V_{out}}{V_{in}} = - \frac{\frac{1}{R_3 C_1} s}{s^2 + \frac{1}{R_3 C_1} s + \frac{1}{R_2 R_4 C_1 C_2}}$$

$$\frac{\omega_n}{Q} = \frac{1}{R_3 C_1}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}.$$

$$Q = \frac{R_3 C_1}{\sqrt{R_2 R_4 C_1 C_2}} = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta s}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2},$$

$$\text{At } \omega = \omega_n \Rightarrow |H(j\omega_n)| = 1 = \frac{\beta Q}{\omega_n}$$

$$\frac{\beta Q}{\omega_n} = \left(\frac{1}{R_3 C_1}\right) (R_3 C_1) = \frac{R_3}{R_1} = 1$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}} = 1.5, \quad W_A = \frac{1}{\sqrt{R_2 R_4 C_2 C_1}} = (10 \times 10^6)(2\pi) = (10 \times 10^6)(2\pi)$$

Let $R_2 = R_4 = 1k\Omega$.

$$\frac{1}{\sqrt{10^6 \times C_1 C_2}} = (10 \times 10^6)(2\pi) \Rightarrow C_1 C_2 = 2.533 \times 10^{-22}$$

Let $C_1 = C_2 = 15.9 \text{ pF}$

$$R_3 \sqrt{\frac{1}{1000 \times 1000}} = 1.5$$

$$\Rightarrow R_3 = 1.5 k\Omega = R_1$$


So : $R_1 = 1.5 k\Omega, R_2 = 1k\Omega, R_3 = 1.5 k\Omega, R_4 = 1k\Omega$.

$$C_1 = C_2 = 15.9 \text{ pF}.$$

58. Peaking : 1 dB @ 7 MHz.

Couner : 3.69 MHz

-13.6 dB @ 2 MHz.

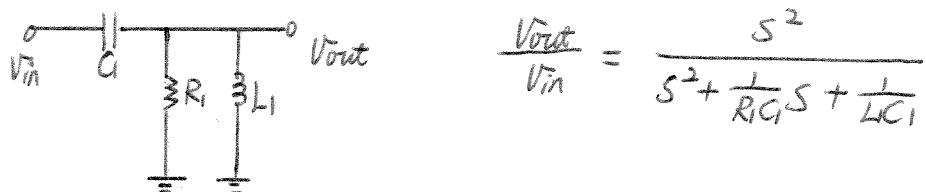

$$\frac{V_{out}}{V_{in}} = \frac{s^2}{s^2 + \frac{1}{R_1 C_1} s + \frac{1}{L_1 C_1}}$$

Peaking 1 dB $\Rightarrow \alpha = 0.926$.

$$\frac{W_h}{\sqrt{1 - 1/\alpha^2}} = (2\pi)(7 \text{ MHz}) \Rightarrow W_h = (2\pi)(14.52 \text{ MHz}).$$

$$\frac{W_h}{\alpha} = \frac{(2\pi)(14.52 \text{ MHz})}{0.926} = (2\pi)(14.88 \text{ MHz}) = \frac{1}{R_1 C_1}.$$

$$W_h^2 = [(2\pi)(14.52 \text{ MHz})]^2 = \frac{1}{L C_1}$$

Let $C_1 = 100 \text{ pF}$, $L_1 = 12.4 \text{ uH}$, $R_1 = 326.1 \Omega$.

With simulated inductor


$$Z_{in} = \left(\frac{Z_1 Z_3}{Z_2 Z_4} \right) Z_5 = R_Y R_X C_S$$

Let $Z_1 = Z_3 = Z_4 = R_Y$, $Z_5 = R_X$, $Z_2 = C_S^{-1}$

Let $R_Y = 1 \text{ k}\Omega$, $R_X = 5 \text{ k}\Omega$.

$$12.4 \times 10^{-6} = (1000)(5000) C$$

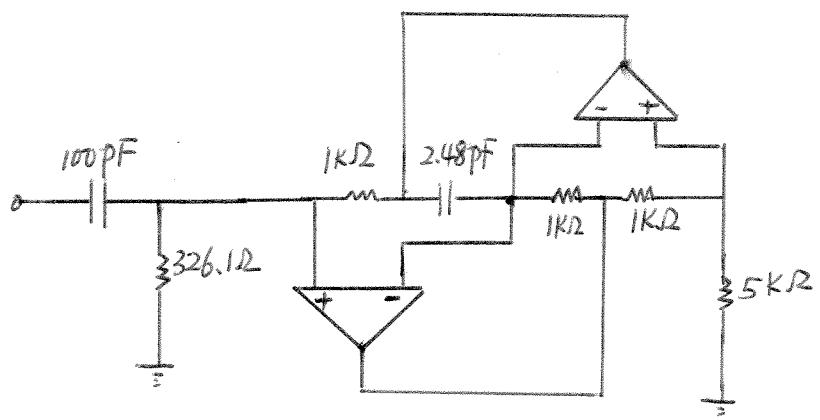$\Rightarrow C = 2.48 \text{ pF}$ to simulate an L of 12.4 uH .



59. Corner @ 16.38 MHz, peaking 0.5 dB @ 8 MHz.

5.9 dB \approx 6 dB attenuation @ 20 MHz.

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{R_1 R_X C^2 S^2 + R_1 C S + 1} = \frac{1/(R_1 R_X C^2)}{S^2 + \frac{S}{R_X C} + \frac{1}{R_1 R_X C^2}}$$

0.5 dB $\Leftrightarrow 1.05292$.

$$\frac{\Omega}{\sqrt{1 - \frac{1}{4Q^2}}} = 1.05292 \Rightarrow Q = 0.8636$$


$$W_n \sqrt{1 - \frac{1}{2Q^2}} = (2\pi)(18 \times 10^6)$$

$$\Rightarrow W_n = (2\pi)(13.934 \times 10^6).$$

$$\frac{1}{R_1 R_X C^2} = W_n^2, \quad \frac{1}{R_X C} = \frac{W_n}{Q} = (2\pi)(16.134 \times 10^6).$$

$$\Rightarrow \frac{1}{R_1 C} = 7.56 \times 10^7$$

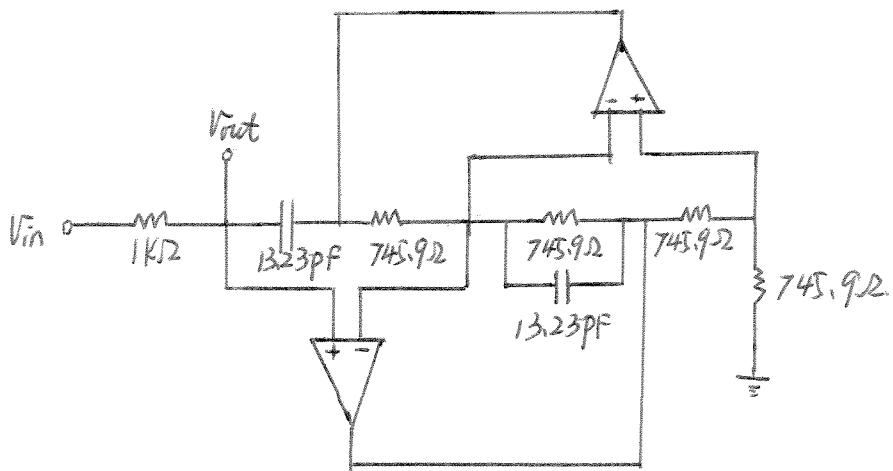Let $R_1 = 1 k\Omega$, $C = 13.23 \mu F$, $R_X = 745.9 \Omega$.



60. Butterworth

a) Passband $0.5 \text{ dB} @ 1 \text{ MHz}$, $-0.5 \text{ dB} \Leftrightarrow 0.944$

Attenuation $12 \text{ dB} @ 2.5 \text{ MHz}$, $-12 \text{ dB} \Leftrightarrow 0.2512$.

$$|H(j\omega)|_{1 \text{ MHz}}^2 = \frac{1}{1 + \left(\frac{(2\pi)(10^6)}{\omega_0}\right)^{2n}} = 0.944^2 \quad (1)$$

$$|H(j\omega)|_{2.5 \text{ MHz}}^2 = \frac{1}{1 + \left(\frac{(2\pi \times 2.5 \times 10^6)}{\omega_0}\right)^{2n}} = 0.2512^2 \quad (2)$$

$$\begin{aligned} (1) \Rightarrow 1 &= (0.944)^2 \left[\left(\frac{2\pi \times 10^6}{\omega_0} \right)^{2n} + 1 \right] \\ \Rightarrow \omega_0^{2n} &= 8.186 \times (2\pi \times 10^6)^{2n} \end{aligned} \quad (3)$$

$$(2) \Rightarrow 1 = (0.2512)^2 \left[\frac{(2\pi \times 2.5 \times 10^6)^{2n}}{8.186 \times (2\pi \times 10^6)^{2n}} + 1 \right]$$

$$\Rightarrow n = 2.62$$

$$\text{So choose } n = 3. \quad (3) \Rightarrow \omega_0 = 2\pi \times 142 \text{ MHz}.$$

$$|H(j\omega)| = \sqrt{\frac{1}{1 + \left(\frac{\omega}{2\pi \times 142 \times 10^6}\right)^6}}$$

b). Passband: 0.1 dB @ 1 MHz

$$\frac{1}{1 + \left(\frac{2\pi \times 10^6}{W_0}\right)^{2n}} = (0.98855)^2 \quad (1)$$

Stopband attenuation: 12 dB @ 2.5 MHz

$$\frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{W_0}\right)^{2n}} = (0.2512)^2 \quad (2)$$

$$(1) \Rightarrow W_0^{2n} = 42.931 \times (2\pi \times 10^6)^{2n}$$

$$(2) \Rightarrow n = 3.52$$

choose $n = 4 \xrightarrow{(3)} W_0 = 2\pi \times 1.6 \text{ MHz}$.

$$|H(jw)| = \frac{1}{\sqrt{1 + \left(\frac{w}{2\pi \times 1.6 \times 10^6}\right)^8}}$$

$$(3) \text{ Passband } 1 \text{ dB @ } 1 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 10^6}{W_0}\right)^{2n}} = (0.90)^2 \quad (4)$$

$$\text{Attenuation } 18 \text{ dB @ } 2.5 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{W_0}\right)^{2n}} = (0.259)^2 \quad (5)$$

$$(4) \Rightarrow W_0^{2n} = 4.263 \times (2\pi \times 10^6)^{2n} \quad (6)$$

$$(5) \Rightarrow n = 3.0$$

choose $n = 3 \xrightarrow{(6)} W_0 = 2\pi \times 1.27 \text{ MHz}$

$$|H(jw)| = \frac{1}{\sqrt{1 + \left(\frac{w}{2\pi \times 1.27 \times 10^6}\right)^6}}$$

$$d) \text{ Passband: } 0.5 \text{ dB @ } 1 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 10^6}{W_0}\right)^{2n}} = 0.944^2 \quad ①$$

$$\text{Attenuation: } 18 \text{ dB @ } 2.5 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{W_0}\right)^{2n}} = 0.1259^2 \quad ②$$

$$① \Rightarrow W_0^{2n} = 8.186 \times (2\pi \times 10^6)^{2n} \quad ③$$

$$② \Rightarrow n = 3.4$$

$$\text{Choose } n = 4 \xrightarrow{③} W_0 = 2\pi \times 1.3 \text{ MHz}$$

$$|H(jw)| = \frac{1}{\sqrt{1 + \left(\frac{w}{2\pi \times 1.3 \times 10^6}\right)^8}}$$

Chebyshev

$$a) \text{ Passband } 0.5 \text{ dB @ } 1 \text{ MHz} \Rightarrow \alpha_s = 20 \log(\sqrt{1+\epsilon^2})$$

$$\Rightarrow \epsilon = 0.3493, W_0 = 1 \text{ MHz}.$$

$$\text{Attenuation } 12 \text{ dB @ } 2.5 \text{ MHz}$$

$$\Rightarrow \frac{1}{\sqrt{1 + \epsilon^2 \cosh^2[n \cosh^{-1}(\frac{w}{W_0})]}} = 0.2512, \text{ when } w = 2.5 \times 10^6 \times 2\pi.$$

Since W, W_0, ϵ , known

$$\Rightarrow n = 1.9733$$

$$\text{Choose } n=2, |H(jw)| = \frac{1}{\sqrt{1 + 0.3493^2 (C_2^2 \frac{w}{W_0})}}, W_0 = 2\pi \times 1 \text{ MHz}$$

b). Passband 0.1 dB @ 1 MHz, $\omega_0 = 1 \text{ MHz}$

$$\Rightarrow 0.1 = 20 \log (\sqrt{1+\epsilon^2}) \Rightarrow \epsilon = 0.1526.$$

Attenuation 12 dB @ 2.5 MHz

$$\Rightarrow \frac{1}{1 + 0.1526^2 \cosh^2[n \cosh^{-1}(2.5)]} = 0.2512^2$$

$$\Rightarrow n = 2.5$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.1526^2 C_3^2(\frac{\omega}{\omega_0})}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

c). Passband 1 dB @ 1 MHz, $\omega_0 = 1 \text{ MHz}$

$$\Rightarrow 1 = 20 \log \sqrt{1+\epsilon^2} \Rightarrow \epsilon = 0.5089.$$

Attenuation 18 dB @ 2.5 MHz

$$\Rightarrow \frac{1}{1 + 0.5089^2 \cosh^2[n \cosh^{-1}(2.5)]} = 0.1259^2 \Rightarrow n = 2.19$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.5089^2 C_3^2(\frac{\omega}{\omega_0})}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

d). Passband 0.5 dB @ 1 MHz $\Rightarrow \epsilon = 0.3493$

Attenuation 18 dB @ 2.5 MHz

$$\Rightarrow \frac{1}{1 + 0.3493^2 \cosh^2[n \cosh^{-1}(2.5)]} = 0.1259^2 \Rightarrow n = 2.43$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.3493^2 C_3^2(\frac{\omega}{\omega_0})}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

61. a) Butterworth in Sallen and Key

$$n=3, \omega_0 = (2\pi)(1.42 \text{ MHz})$$

$$P_k = \omega_0 \cdot \exp\left(\frac{j\pi}{2}\right) \exp\left(j\frac{2k-1}{2n}\pi\right), \quad k=1, 2, 3.$$

$$P_1 = \omega_0 \exp\left(j\frac{2\pi}{3}\right) = (2\pi)(1.42 \text{ MHz}) \times \left(\cos\frac{2\pi}{3} + j\sin\frac{2\pi}{3}\right).$$

$$P_2 = \omega_0 \exp(j\pi) = -(2\pi)(1.42 \text{ MHz})$$

$$P_3 = \omega_0 \exp\left(j\frac{4\pi}{3}\right) = (2\pi)(1.42 \text{ MHz}) \times \left(\cos\frac{2\pi}{3} - j\sin\frac{2\pi}{3}\right)$$

$$\begin{aligned} H_{P_{1,3}}(s) &= \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} \\ &= \frac{\left[2\pi \times (1.42 \text{ MHz})\right]^2}{s^2 - \left[4\pi \times (1.42 \text{ MHz}) \cos\frac{2\pi}{3}\right]s + \left[2\pi \times (1.42 \text{ MHz})\right]^2} \end{aligned}$$

$$W_n = 2\pi \times 1.42 \text{ MHz} \left(= \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}\right)$$

$$\frac{W_n}{Q} = 2\pi \times 1.42 \text{ MHz} \cdot \cos\left(\frac{2\pi}{3}\right) \Rightarrow Q = \frac{-1}{2\cos\left(\frac{2\pi}{3}\right)} \left(= \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}\right)$$


Let $C_1 = 4C_2$, $R_1 = R_2$, so that it satisfies $Q = \frac{-1}{2\cos\left(\frac{2\pi}{3}\right)} = 1$

$$\text{Also } \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 2\pi \times 1.42 \text{ MHz}$$

$$\text{Let } R_1 = R_2 = 1 \text{ k}\Omega \Rightarrow C_1 = 224 \text{ pF}, \quad C_2 = 56 \text{ pF}$$

$$P_2 = -\omega_0, \quad \frac{1}{R_3 C_3} = (2\pi)(142 \text{ MHz})$$

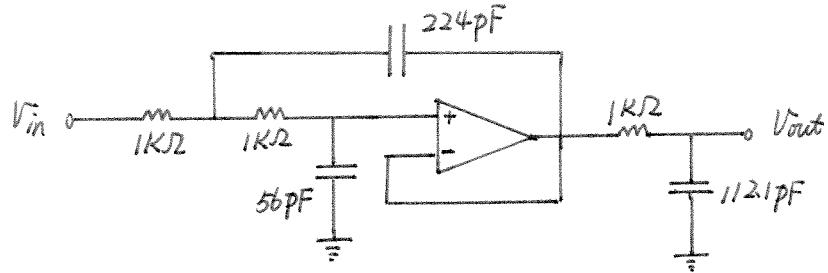Let $R_3 = 1k\Omega \Rightarrow C_3 = 1/2.1 \text{ pF}$



Chebyshev in Sallen and Key

$$P_k = -\omega_0 \sin \frac{(2k-1)\pi}{2n} \sinh \left(\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right) + j\omega_0 \cos \frac{(2k-1)\pi}{2n} \cosh \left(\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right)$$

$$n=2, \quad \omega_0 = (2\pi)(1 \text{ MHz}), \quad \epsilon = 0.3493, \quad k=1, 2.$$

$$\omega_{1,2} = -0.7128\omega_0 \pm j1.0041\omega_0$$

$$H_{SK}(s) = \frac{(-P_1)(-P_2)}{(s-P_1)(s-P_2)} = \frac{(1.2314)^2 \omega_0^2}{s^2 + 1.4256\omega_0 s + (1.2314)^2 \omega_0^2}$$

$$\omega_n = 1.2314\omega_0 = (2\pi)(1.2314 \text{ MHz})$$


$$\frac{\omega_n}{Q} = 1.4256\omega_0 \Rightarrow Q = \frac{1.2314}{1.4256} = 0.8638.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2, \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 2.9844$$

$$\frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \omega_n = 2\pi(1.2314 \text{ MHz}), \Rightarrow \frac{1}{R_1 C_2 \sqrt{2.9844}} = 2\pi(1.2314 \text{ MHz})$$
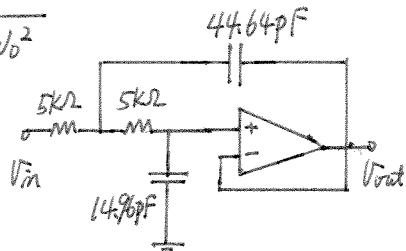
$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 14.96 \text{ pF}, \quad Q = 44.64 \text{ pF}$$



b). Butterworth with SK

$$n=4, \omega_0 = (2\pi)(1.6 \text{ MHz})$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1, 2, 3, 4.$$

$$P_1 = \omega_0 \exp(j\frac{5\pi}{8}), \quad P_2 = \omega_0 \exp(j\frac{\pi}{8}), \quad P_3 = \omega_0 \exp(-j\frac{5\pi}{8}), \quad P_4 = \omega_0 \exp(j\frac{7\pi}{8})$$

$$H_{SK1,4}(s) = \frac{(-P_1)(-P_4)}{(s-P_1)(s-P_4)} = \frac{[(2\pi)(1.6 \times 10^6)]^2}{s^2 - [4\pi \times (1.6 \times 10^6) \cos(\frac{5\pi}{8})]s + [2\pi \times (1.6 \times 10^6)]^2}$$

$$\omega_n = 2\pi \times 1.6 \times 10^6$$

$$\frac{\omega_n}{Q} = (4\pi)(1.6 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = 1.31.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}.$$


$$\text{Let } R_1 = R_2, \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{Q}{C_2} = 4Q^2 = 6.83.$$

$$\omega_n = \frac{1}{\sqrt{6.83 R_1 C_2}} = 2\pi \times 1.6 \times 10^6$$

$$\text{Let } R_1 = R_2 = 5\text{ k}\Omega \Rightarrow C_2 = 7.61\text{ pF}, \quad C_1 = 52\text{ pF}.$$

Similarly, $H_{SK2,3}(s) = \frac{(-P_2)(-P_3)}{(s-P_2)(s-P_3)}$, it can be derived for $H_{SK2,3}$.
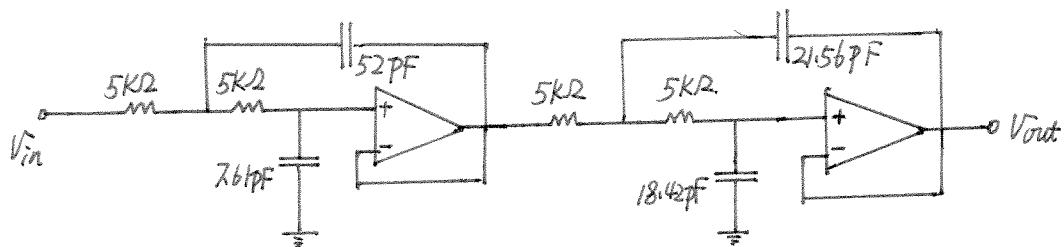
$$R_1 = R_2 = 5\text{ k}\Omega, \quad C_2 = 18.42\text{ pF}, \quad C_1 = 21.55\text{ pF}.$$



b) Chebyshev in SK.

$$n=3, \quad w_0 = (2\pi)(1 \times 10^6), \quad \epsilon = 0.1526$$

$$P_1 = -w_0(0.9694) \sin\left(\frac{1}{6}\pi\right) + jw_0(1.3927) \cos\left(\frac{\pi}{6}\right) = -0.4847w_0 + j1.206/w_0$$

$$P_2 = -w_0(0.9694) \sin\left(\frac{3}{6}\pi\right) + jw_0(1.3927) \cos\left(\frac{3\pi}{6}\right) = -0.9496w_0$$

$$P_3 = -w_0(0.9694) \sin\left(\frac{5}{6}\pi\right) + jw_0(1.3927) \cos\left(\frac{5\pi}{6}\right) = -0.4847w_0 - j1.206/w_0$$

$$H_{SK}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{1.3^2 w_0^2}{s^2 + 0.9694w_0 s + (1.3)^2 w_0^2}$$

$$W_n = 1.3 w_0$$

$$\frac{W_n}{\alpha} = 0.9694 w_0 \Rightarrow \alpha = 1.3410.$$

$$W_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \alpha = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2 \Rightarrow \alpha = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = (2\alpha)^2 = 7.1931.$$


$$W_n = \frac{1}{\sqrt{7.1931} \cdot R_1 C_2} = (1.3)(2\pi)(1 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_1 = 9.13 \text{ pF} \Rightarrow C_1 = 65.67 \text{ pF}$$

$$P_2 = (2\pi)(0.9694 \times 10^6), \text{ and}$$

$$\frac{1}{R_3 C_3} = P_2$$
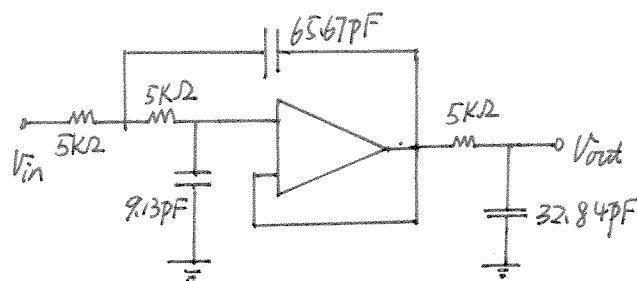
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 32.84 \text{ pF}$$



C). Butterworth in SK.

$$n=3, \omega_0 = (2\pi)(1.27 \times 10^6)$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1, 2, 3.$$

$$H_{P_{1,3}}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{[(2\pi)(1.27 \times 10^6)]^2}{s^2 - [4\pi \times (1.27 \times 10^6) \omega s(\frac{2\pi}{3})]s + [2\pi(1.27 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(1.27 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = (4\pi)(1.27 \times 10^6) \omega s(\frac{2\pi}{3}) \Rightarrow Q = 1.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$


$$\text{Let } C_1 = 4C_2, R_1 = R_2$$

$$\omega_n = \frac{1}{2R_1 C_2} = (2\pi)(1.27 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 12.53 \text{ pF}, \quad C_1 = 50.13 \text{ pF.}$$

$$P_2 = -\omega_0 = (2\pi)(1.27 \times 10^6) = \frac{1}{R_3 C_3}$$
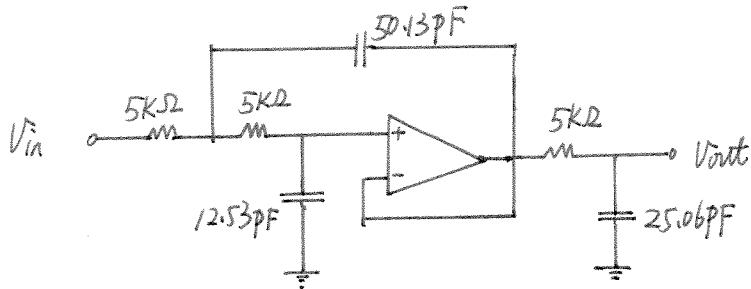
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 25.06 \text{ pF}$$



C). Chebyshev in SK.

$$n=3, \quad G = 0.5089, \quad \omega_0 = (2\pi)(10^6).$$

$$P_1 = -0.2470\omega_0 + j0.9660\omega_0$$

$$P_2 = -0.4941\omega_0$$

$$P_3 = -0.2470\omega_0 - j0.9660\omega_0$$

$$H_{P_{13}}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{[(2\pi)(0.9971 \times 10^6)]^2}{s^2 + (0.4940)(2\pi)(10^6)s + (2\pi \times 0.9971 \times 10^6)^2}$$

$$\omega_n = (2\pi)(0.9971 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.4940)(2\pi \times 10^6) \Rightarrow Q = 2.02.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 G C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{G}{C_2}}.$$

$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{G}{C_2}} \Rightarrow \frac{G}{C_2} = 4Q^2 = 16.296.$$


$$\omega_n = \frac{1}{\sqrt{16.296} R_1 C_2} = (2\pi)(0.9971 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5\text{ k}\Omega \Rightarrow C_2 = 7.91\text{ pF} \Rightarrow G = 128.87\text{ pF}$$

$$P_2 = 2\pi \times 0.4941 \times 10^6 = \frac{1}{R_3 C_3}$$

$$\text{Let } R_3 = 5\text{ k}\Omega$$

$$\Rightarrow C_3 = 64.42\text{ pF}$$

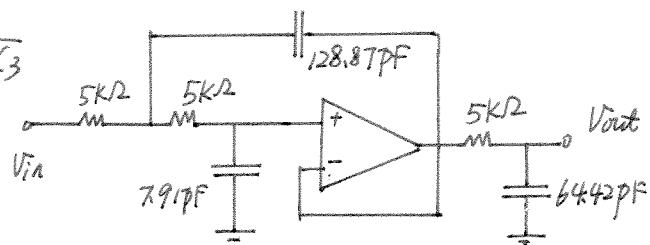

d). Butterworth in SK.

$$n=4, \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$P_k = \omega_0 \exp(j \frac{\pi}{2}) \exp(j \frac{2k-1}{2n} \pi), \quad k=1,2,3,4.$$

$$H_{SK_{1,4}}(s) = \frac{(-P_1)(-P_4)}{(s-P_1)(s-P_4)} = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = 4\pi(1.3 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = 1.3$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$


$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 6.828$$

$$\omega_n = \frac{1}{\sqrt{6.828 R_1 C_2}} = (2\pi)(1.3 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 9.37 \text{ pF} \Rightarrow C_1 = 63.98 \text{ pF}$$

Similarly, $H_{SK_{2,3}}(s) = \frac{(-P_2)(-P_3)}{(s-P_2)(s-P_3)}$. It can be derived that
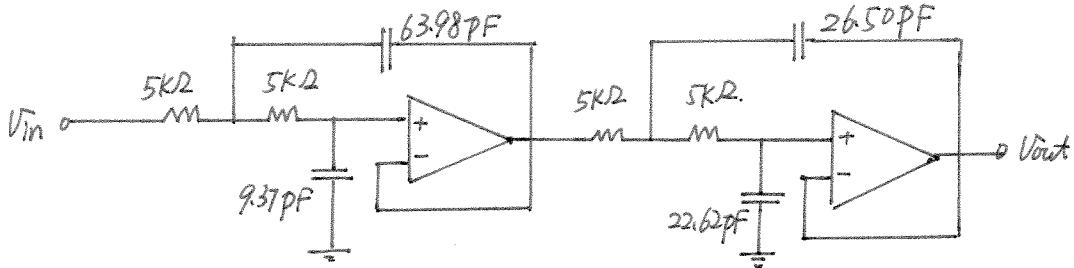
$$R_1 = R_2 = 5k\Omega, \quad C_2 = 22.62 \text{ pF}, \quad G = 26.50 \text{ pF}$$



d). Chebychev in SK.

$$n=3, \quad E=0.3493, \quad w_0 = (2\pi)(1 \times 10^6)$$

$$P_1 = -w_0 0.6265 \sin\left(\frac{1}{6}\pi\right) + jw_0(1.1800) \cos\left(\frac{1}{6}\pi\right)$$

$$P_2 = -w_0 0.6265$$

$$P_3 = -w_0 0.6265 \sin\left(\frac{5}{6}\pi\right) + jw_0(1.1800) \cos\left(\frac{5}{6}\pi\right).$$

$$H_{P,3} = \frac{(-P_1)(-P_3)}{(S-P_1)(S-P_3)} = \frac{[2\pi \times 1.069 \times 10^6]^2}{S^2 + (0.6265)(2\pi \times 10^6)S + (2\pi \times 1.069 \times 10^6)^2}$$

$$w_n = (2\pi)(1.069 \times 10^6)$$

$$\frac{w_n}{\alpha} = (0.6265)(2\pi \times 10^6) \Rightarrow \alpha = 1.7063$$


$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{R_1 R_2 C_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} = \frac{1}{2} \sqrt{\frac{Q}{C_2}} \Rightarrow \frac{Q}{C_2} = 4Q^2 = 11.6459.$$

$$w_n = \frac{1}{\sqrt{R_1 R_2 Q C_2}} = \frac{1}{\sqrt{11.6459} R_1 C_2} = (2\pi)(1.069 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 8.73 \text{ pF} \Rightarrow C_1 = 101.62 \text{ pF}.$$

$$-P_2 = (0.6265)(2\pi \times 10^6) = \frac{1}{R_3 C_3}$$
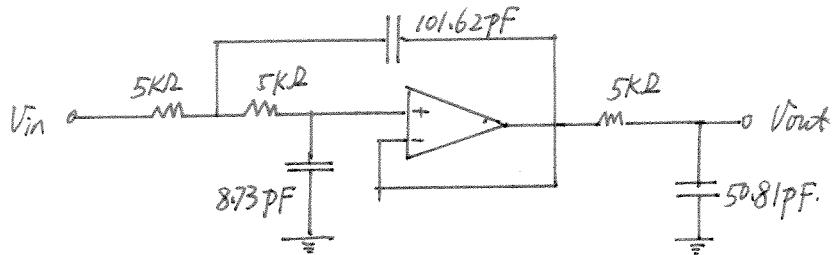
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 50.81 \text{ pF}.$$



62) a). Butterworth TT

$$n=3, \omega_0 = (2\pi)(1.42 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{2\pi}{3}), P_2 = -\omega_0, P_3 = \omega_0 \exp(-j\frac{2\pi}{3}).$$

$$H_{P_{1,3}} = \frac{[2\pi \times (1.42 \times 10^6)]^2}{s^2 - [4\pi \times (1.42 \times 10^6) \cos(\frac{2\pi}{3})]s + [2\pi \times 1.42 \times 10^6]^2}$$

$$\omega_n = (2\pi)(1.42 \times 10^6).$$


$$Q = \frac{-1}{2 \cos(\frac{2\pi}{3})} = 1$$

$$\omega_h = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, Q = R_3 \sqrt{\frac{C_1}{C_2 R_2 R_4}}.$$

$$\text{Let } R_2 = R_4 = R_3 = 5\text{ k}\Omega, C_1 = C_2 = 22.42 \text{ pF}$$

$$-P_2 = -(2\pi)(1.42 \times 10^6) = \frac{1}{R_3 C_3}.$$
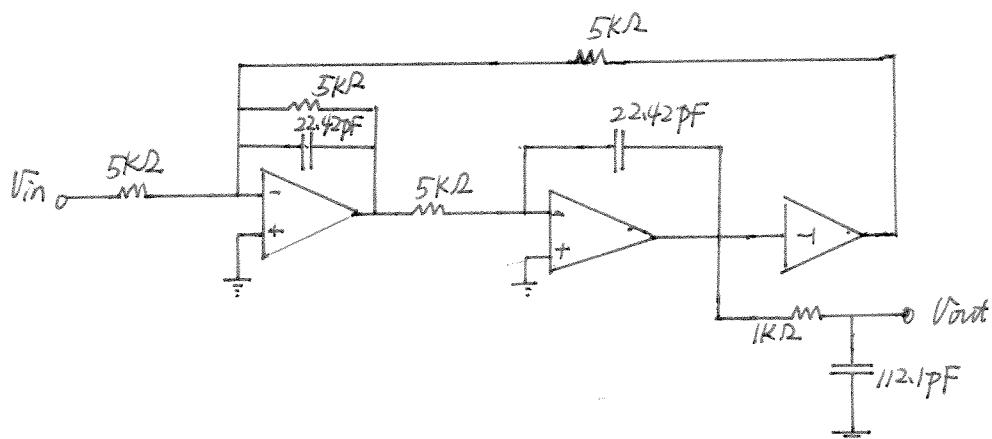
$$\text{Let } R_3 = 1\text{ k}\Omega \Rightarrow C_3 = 112.1 \text{ pF}$$



$R_1 = R_2 = R_4$ to match low frequency gain requirement.

a) Chebyshev TT

$$n=2, \omega_0 = (2\pi)(1\text{MHz}), \epsilon = 0.3493$$

$$H_{P_{02}} = \frac{(1.2314)^2 \omega_0^2}{s^2 + 1.4256 \omega_0 s + (1.2314)^2 \omega_0^2}$$

$$\omega_0 = (2\pi)(1.2314 \times 10^6)$$

$$Q = \frac{1.2314}{1.4256} = 0.8638$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_h = \frac{1}{\sqrt{R_2 R_4 G C_2}}$$


$$\text{Let } C_1 = C_2, R_2 = R_4$$

$$\omega_h = \frac{1}{R_2 C_1} = (2\pi)(1.2314 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5\text{k}\Omega, \quad C_1 = C_2 = 25.85\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{k}\Omega$, to match low frequency gain of unity.
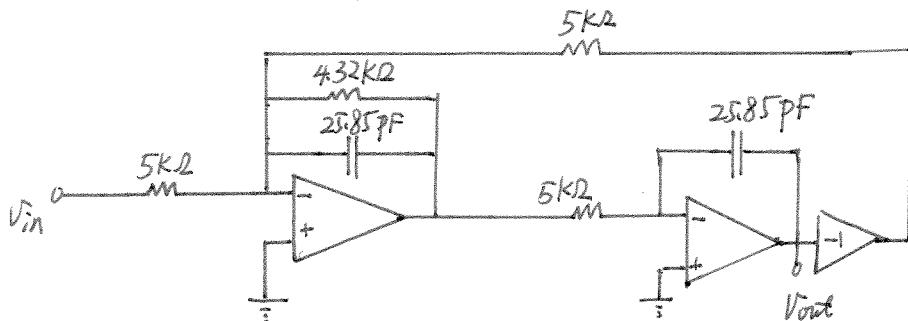
$$Q = \frac{R_3}{R_2} \Rightarrow R_3 = 4.32\text{k}\Omega.$$



b). Butterworth with TT

$$n=4, \omega_0 = (2\pi)(1.6 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{5\pi}{8}), \quad P_4 = \omega_0 \exp(-j\frac{5\pi}{8})$$

$$P_2 = \omega_0 \exp(j\frac{\pi}{8}), \quad P_3 = \omega_0 \exp(-j\frac{7\pi}{8}).$$

$$H_{P44} = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_h = \omega_0 = (2\pi)(1.6 \times 10^6)$$

$$\frac{\omega_h}{\alpha} = (4\pi)(1.6 \times 10^6) \omega_0 (\frac{5\pi}{8}) \Rightarrow \alpha = 1.31$$

$$\omega_h = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad \alpha = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2 \Rightarrow \omega_h = \frac{1}{R_2 C} = (2\pi)(1.6 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5\text{ k}\Omega \Rightarrow C_1 = C_2 = 19.89 \text{ pF.}$$

$R_1 = R_2 = R_4 = 5\text{ k}\Omega$, to obtain a low-frequency gain of unity.

$$\alpha = \frac{R_3}{R_2} = 1.31 \Rightarrow R_3 = 1.31 R_2 = 6.55 \text{ k}\Omega.$$

Similarly for $H_{P2,3}$, it can be derived that $R_1 = R_2 = R_4 = 5\text{ k}\Omega, R_3 = 2.7 \text{ k}\Omega$

$$C_1 = C_2 = 19.89 \text{ pF.}$$

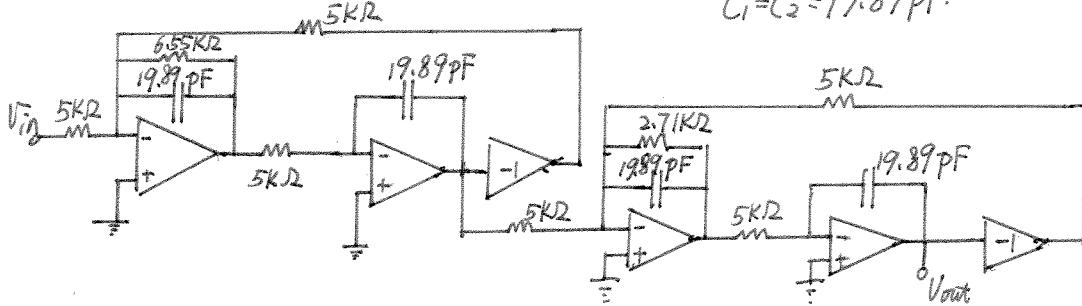

b). Chebyshev with TT

$$n=3, \epsilon = 0.1526, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = 0.4847\omega_0 \pm j1.206/\omega_0$$

$$P_2 = -0.9694\omega_0$$

$$H_{P_{1,3}}(s) = \frac{(1.3)^2 \omega_0^2}{s^2 + 0.9694\omega_0 s + (1.3)^2 \omega_0^2}$$

$$\omega_n = 1.3\omega_0, \frac{\omega_n}{\alpha} = 0.9694\omega_0$$

$$\alpha = \frac{1.3}{0.9694} = 1.3410$$

$$\alpha = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } R_2 = R_4, C_1 = C_2, \frac{1}{R_2 C_1} = (1.3)(2\pi)(10^6)$$

$$\text{Let } R_2 = R_4 = 5k\Omega, \Rightarrow C_1 = C_2 = 24.49\text{ pF}$$

$R_1 = R_2 = R_4 = 5k\Omega$, to obtain low-frequency gain of unity.

$$R_3 = \alpha R_2 = 6.705k\Omega$$
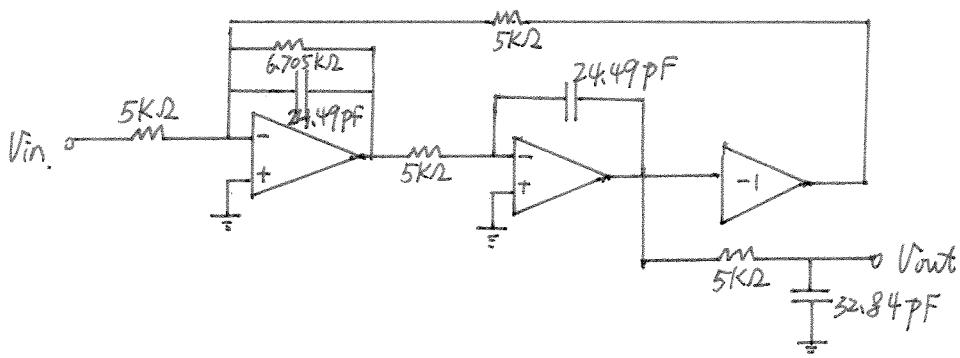
$$-P_2 = (2\pi)(0.9694 \times 10^6) = \frac{1}{R_5 C_5}, \text{ Let } R_5 = 5k\Omega \Rightarrow C_5 = 32.84\text{ pF}$$



c) Butterworth with T-T

$$n=3, \omega_0 = (2\pi)(1.27 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{2\pi}{3}), \quad P_3 = \omega_0 \exp(-j\frac{2\pi}{3}), \quad P_2 = -\omega_0.$$

$$H_{P_{1,3}}(s) = \frac{[(2\pi)(1.27 \times 10^6)]^2}{s^2 - [(4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3})]s + [(2\pi)(1.27 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(1.27 \times 10^6), \quad \frac{\omega_n}{Q} = (4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3})$$

$$Q = -\frac{1}{2\cos(\frac{2\pi}{3})} = 1.$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2, \quad \frac{1}{R_2 C_1} = (2\pi)(1.27 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5\text{ k}\Omega \Rightarrow C_1 = C_2 = 25.06 \text{ pF.}$$

$R_1 = R_2 = R_4 = 5\text{ k}\Omega$, to obtain Low-frequency gain of unity.

$$R_3 = Q R_2 = 5\text{ k}\Omega.$$

$$-P_2 = \omega_0 \Rightarrow \frac{1}{R_5 C_5} = (2\pi)(1.27 \times 10^6)$$
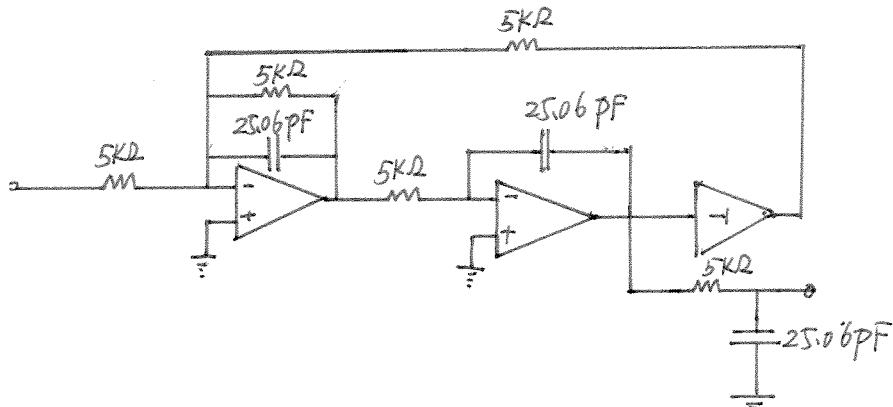
$$\text{Let } R_5 = 5\text{ k}\Omega \Rightarrow C_5 = 25.06 \text{ pF}$$



c) Chebyshev TT

$$n=3, \epsilon = 0.5089, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = -0.2470\omega_0 \pm j0.9660\omega_0, P_2 = -0.4941\omega_0$$

$$H_{P_{1,3}}(s) = \frac{[(2\pi)(0.9971 \times 10^6)]^2}{s^2 + (0.4940)(2\pi \times 10^6)s + [(2\pi \times 0.9971 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(0.9971 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.4940)(2\pi \times 10^6) \Rightarrow Q = 2.02$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } R_2 = R_4, C_1 = C_2 \Rightarrow \frac{1}{R_2 C_1} = (2\pi)(0.9971 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5k\Omega \Rightarrow C_1 = C_2 = 31.92 \text{ pF}$$

$R_1 = R_2 = R_4 = 5k\Omega$, to obtain Low-frequency gain of unity.

$$R_3 = Q R_2 = 10.1 k\Omega.$$
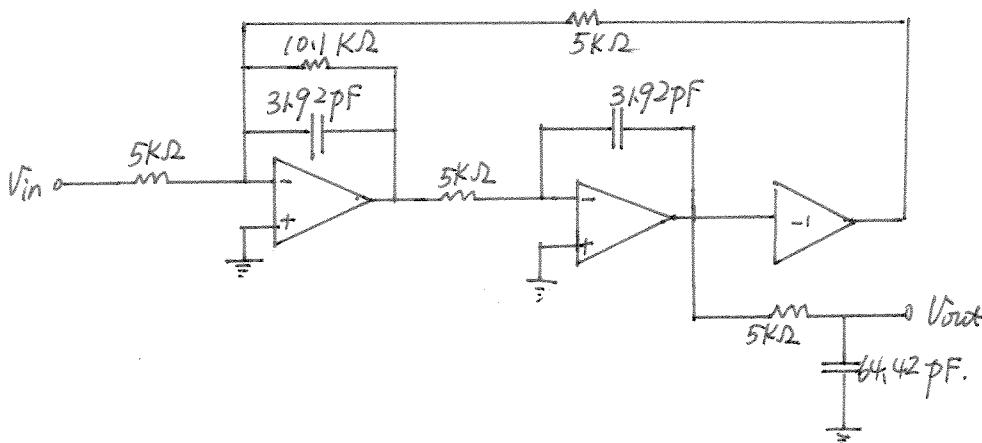
$$-P_2 = (2\pi)(0.4941 \times 10^6) = \frac{1}{R_5 C_5}. \quad \text{Let } R_5 = 5k\Omega \Rightarrow C_5 = 64.42 \text{ pF.}$$



d). Butterworth in TT

$$n=4, \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$P_{1,4} = \omega_0 \exp(\pm j \frac{5\pi}{8}), \quad P_{2,3} = \omega_0 \exp(\pm j \frac{7\pi}{8})$$

$$H_{P_{1,4}}(s) = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = (2\pi)(1.3 \times 10^6)$$

$$\frac{\omega_n}{Q} = (4\pi)(1.3 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = -\frac{1}{2\cos(\frac{5\pi}{8})} = 1.31.$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2, \quad \omega_n = \frac{1}{\sqrt{R_2^2 C_1^2}} = \frac{1}{R_2 C_1} = (2\pi)(1.3 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5\text{ k}\Omega \Rightarrow C_1 = C_2 = 24.49\text{ pF}.$$

$R_1 = R_2 = R_4 = 5\text{ k}\Omega$, to obtain a low-frequency gain of unity.

$$R_3 = Q R_2 = 6.55\text{ k}\Omega.$$

$$\text{Similarly, } H_{P_{2,3}}(s) = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{7\pi}{8})]s + \omega_0^2}$$

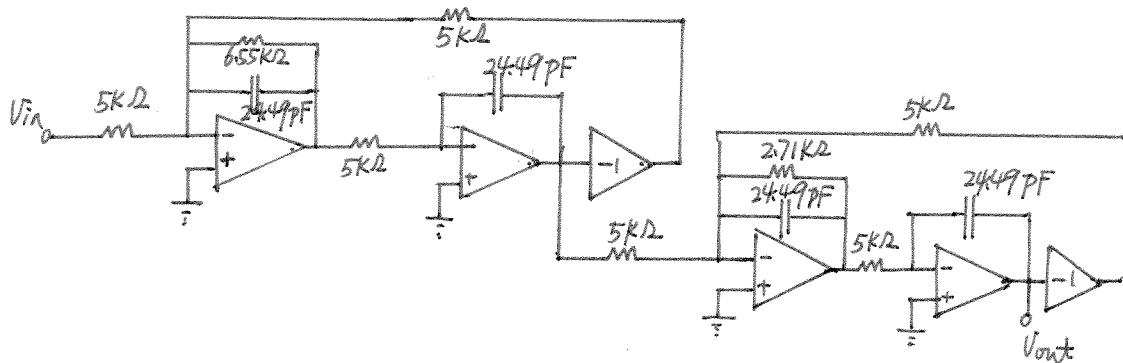It can be obtained that $R_1 = R_2 = R_4 = 5\text{ k}\Omega$, $R_3 = 2.71\text{ k}\Omega$, $C_1 = C_2 = 24.49\text{ pF}$.



d). Chebyshev TT

$$n=3, \quad \epsilon = 0.3493, \quad w_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = -0.3133 w_0 \pm j1.022 w_0, \quad P_2 = -0.6265 w_0.$$

$$H_{P_{1,3}} = \frac{[2\pi \times 1.069 \times 10^6]^2}{s^2 + (0.6265)(2\pi \times 10^6)s + (2\pi \times 1.069 \times 10^6)^2}$$

$$w_n = (2\pi)(1.069 \times 10^6)$$

$$\frac{w_n}{Q} = (0.6265)(2\pi \times 10^6) \Rightarrow Q = \frac{1.069}{0.6265} = 1.7063$$

$$w_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$


$$\text{Let } R_2 = R_4, \quad C_1 = C_2, \quad \frac{1}{R_2 C_1} = (2\pi)(1.069 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5k\Omega \Rightarrow C_1 = C_2 = 29.78 \text{ pF.}$$


$R_1 = R_2 = R_4 = 5k\Omega$, to obtain a low-frequency gain of unity.

$$R_3 = Q R_2 = 8.53 k\Omega.$$
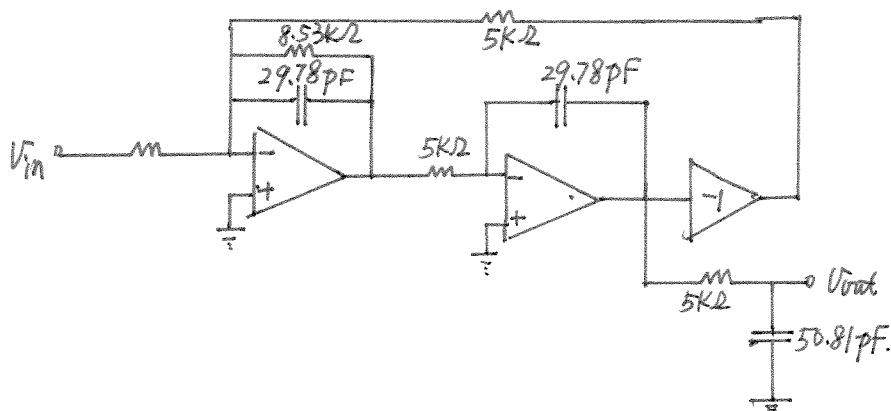
$$-P_2 = 0.6265 \times (2\pi \times 10^6) = \frac{1}{R_5 C_5}, \quad \text{Let } R_5 = 5k\Omega \Rightarrow C_5 = 50.81 \text{ pF}$$



1.

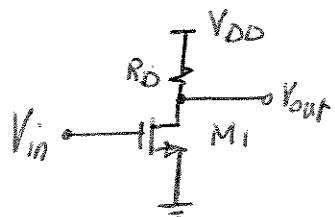

M_1 operates in the triode region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2]$$

$$R_D = 10K$$

$$V_{out} = V_{DD} - R_D I_D$$

$$\left(\frac{W}{L} \right)_1 = 3/0.18$$

$$V_{out, min} = ? \text{ when } V_{in} = V_{DD}$$

$$V_{out, min} = V_{DD} - R_D I_{D, max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2] \times R_D$$


If the second term in the square brackets is neglected, then

$$V_{out, min} \approx \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH}) \times R_D}$$

$$= \frac{1.8}{1 + 100 \times 10^{-6} \times \frac{3}{0.18} \times (1.8 - 0.4) \times 10^5}$$

$V_{out, min} \approx 74 mV$

2.

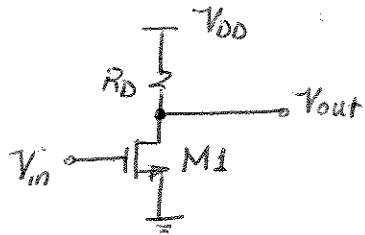

$$V_{out,min} \leq 100 \text{ mV}$$

$$R_D = 5 \text{ k}\Omega$$

$$\left(\frac{W}{L}\right)_{I,min} = ?$$

Output low level establishes for $V_{in} = V_{DD}$, driving M_1 into the triode region.

$$I_{D,max} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_I \left[2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2 \right]$$

$$V_{out,min} = V_{DD} - R_D \times I_{D,max}$$


$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_I \left[2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2 \right] \times R_D$$

$$\left(\frac{W}{L}\right)_I = \frac{V_{DD} - V_{out,min}}{\frac{1}{2} \mu_n C_{ox} \left[2(V_{DD} - V_{TH}) V_{out,min} - V_{out,min}^2 \right] \times R_D}$$

$$\left(\frac{W}{L}\right)_{I,min} = \frac{1.8 - 100 \times 10^{-3}}{\frac{1}{2} \times 100 \times 10^{-6} \left[2(1.8 - 0.4) / 100 \times 10^{-3} - (100 \times 10^{-3})^2 \right] \times 5 \times 10^3}$$

$$\left(\frac{W}{L}\right)_{I,min} = 25$$

3.

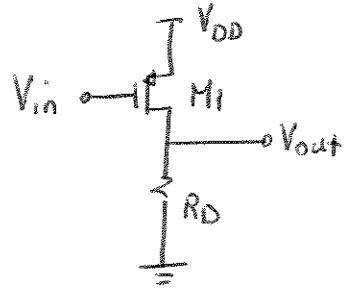

$$\left(\frac{W}{L}\right)_1 = 20/0.18, \quad R_D = 5K$$

$$V_{o_L}, V_{o_H} = ?$$

(1) $V_{in} = V_{DD} \rightarrow M_1 \text{ off} \rightarrow I_D = 0 \rightarrow V_{out} = V_{o_L} = 0$

(2) $V_{in} = 0 \rightarrow M_1 \text{ operates in the triode region}$

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{SG} - |V_{mp}|) V_{SD} - V_{SD}^2 \right]$$

$$I_{D,\max} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - |V_{mp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

$$I_{D,\max} = \frac{V_{out}}{R_D} \quad (2)$$

Equating (1) and (2) and neglecting the second order term in the brackets


$$\frac{V_{out}}{R_D} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \times 2(V_{DD} - |V_{mp}|)(-V_{out} + V_{DD})$$

$$V_{out} \left[\frac{1}{R_D} + \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{mp}|) \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{mp}|) \times \frac{V_{DD}}{R_D}$$

$$V_{out} = \frac{\frac{R_D}{R_D + \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{mp}|)}}}{V_{DD}}$$

$$V_{out} = \frac{5000}{5000 + \frac{1}{50 \times 10^{-6} \times \left(\frac{20}{0.18}\right) \times (1.8 - 0.5)}} \times 1.8$$
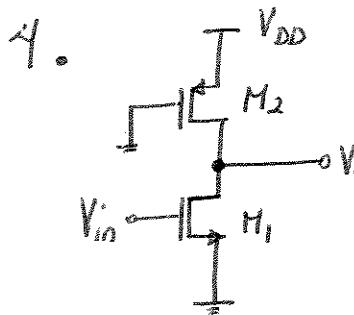
$$\boxed{V_{out} = V_{oh} = 1.75 \text{ V}}$$



$$\left(\frac{W}{L}\right)_1 = 3/0.18 \quad \left(\frac{W}{L}\right)_2 = 2/0.18$$

(a) if $V_{in} = V_{DD}$, M₂ saturated $\rightarrow V_{OL} = ?$

(b) if $V_{in}^o = V_{out} \rightarrow V_{in} = ?$

$$(a) I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left(V_{SG} - |V_{THP}|\right)^2$$

$$I_{D2} = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{2}{0.18}\right) \left(1.8 - 0.5\right)^2, \text{ Note that } V_{SG} = V_{DD}$$

$$I_{D2} = 4.7 \times 10^{-4} A$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{GS} - V_{THN})V_{DS} - V_{DS}^2\right]$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{THN})V_{OL} - V_{OL}^2\right]$$

However $I_{D1} = I_{D2}$

$$4.7 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \left[2(1.8 - 0.4)V_{OL} - V_{OL}^2\right]$$

Neglecting the second-order term yields:

$V_{OL} = 0.2 V$

$$\text{As } (V_{in}^o - V_{THN}) = (V_{DD} - V_{THN}) = (1.8 - 0.4) = 1.4 > V_{DS1} = V_{OL} = 0.2 V$$

The assumption of M₁ being in Triode region is correct

We define, $V_x = V_{in} - V_{TH,N} \rightarrow V_{in} = V_x + V_{TH,N}$

$$\frac{\frac{1}{2}M_nC_{ox}\left(\frac{W}{L}\right)_1}{\frac{1}{2}M_pC_{ox}\left(\frac{W}{L}\right)_2} V_x^2 = 2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{TH,N} - V_x) - (V_{DD} - V_{TH,N} - V_x)^2$$

$$\frac{100}{50} \times \frac{\frac{3}{0.18}}{\frac{2}{0.18}} V_x^2 = 2(1.8 - 0.5)(1.8 - 0.4 - V_x) - (1.8 - 0.4 - V_x)^2$$

$$3V_x^2 = 2.6(1.4 - V_x) - (1.4 - V_x)^2$$

$$3V_x^2 = 3.64 - 2.6V_x - 1.96 + 2.8V_x - V_x^2$$

$$4V_x^2 - 0.2V_x - 1.68 = 0$$

$$V_x = \frac{0.2 \pm \sqrt{0.2^2 + 4 \times 4 \times 1.68}}{8} \rightarrow V_x = 0.67 \text{ V}$$

$$V_{in} = V_x + V_{TH,N} = 0.67 + 0.4 \rightarrow V_{in} = V_{out} = 1 \text{ V}$$

This value of V_{out} guarantees that M_2 operates in the triode region.

Now, let's investigate the region of operation of M₂

$$V_{SD2} = V_{DD} - V_{out}$$

$$= 1.8 - 0.2$$

$$V_{SD2} = 1.6 \text{ V}$$

$$V_{SG2} - |V_{THP}| = V_{DD} - |V_{THP}|$$

$$= 1.8 - 0.5$$

$$V_{SG2} - |V_{THP}| = 1.3$$


As $V_{SD2} > V_{SG2} - |V_{THP}|$, M₂ operates in the saturation region and the initial assumption is valid.

(b) As $V_{in} = V_{out} \rightarrow M_1 \text{ is saturated}$.

We assume that M₂ is in the triode region and check the validity of this assumption

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 [2(V_{DD} - |V_{THP}|) \times \\ (V_{DD} - V_{in}) - (V_{DD} - V_{in})^2]$$

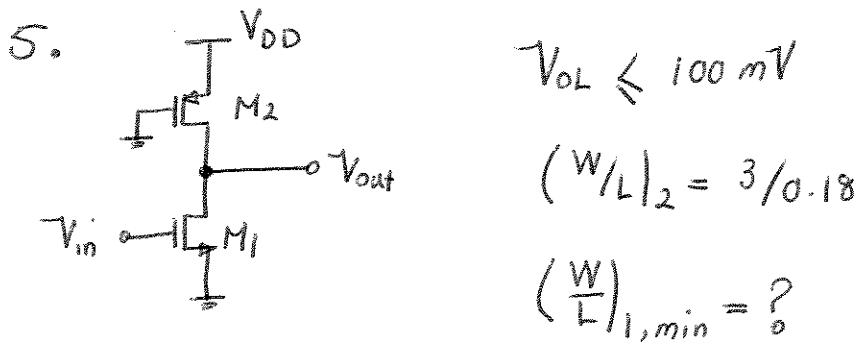

$V_{in} = V_{DD} \rightarrow M_1$ operates in the triode region and M_2 in the saturation.

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{SG} - V_{TH,p})^2$$

$$= \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{3}{0.18} \right) \times (1.8 - 0.5)^2$$


$$I_{D2} = 7.041 \times 10^{-4} \text{ A}$$

$$I_{D1} = I_{D2} = 7.041 \times 10^{-4}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [2(V_{GS} - V_{TH,N}) V_{DS} - V_{DS}^2]$$

$$7.041 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L} \right)_1 [2(1.8 - 0.4) 0.1 - (0.1)^2]$$
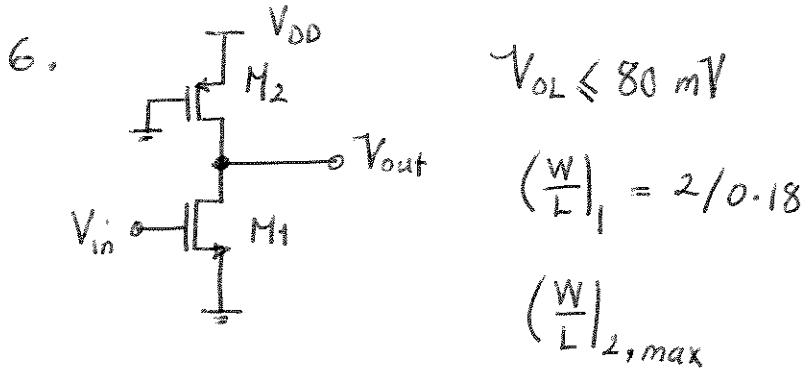
$$\boxed{\left(\frac{W}{L} \right)_{1,\min} = 52.16}$$



$V_{in} = V_{DD} \rightarrow M_1$ operates in the triode region and M_2 in the saturation

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{GS} - V_{TH,N})V_{DS} - V_{DS}^2 \right]$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) \times \left[2(1.8 - 0.4)/0.08 - 0.08^2 \right]$$

$$I_{D1} = 1.2 \times 10^{-4} \text{ A}$$


$$I_{D2} = I_{D1} = 1.2 \times 10^{-4} \text{ A}$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left(V_{SG} - |V_{TH,P}| \right)^2$$

$$1.2 \times 10^{-4} = \frac{1}{2} \times 50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)^2$$

$$\boxed{\left(\frac{W}{L}\right)_{2,\max} = 2.86}$$

7.

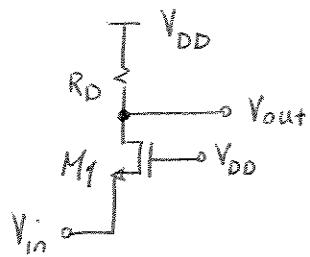

(a) If $V_{in} = 0$, V_{DD} , $V_{out} = ?$

If $V_{in} = 0 \rightarrow M_1$ operates in the triode region.


$$R_{on1} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH,N})}$$


$$V_{out} \approx \frac{R_{on1}}{R_{on1} + R_D} \times V_{DD} \rightarrow V_{out} \approx \frac{1}{1 + \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH,N}) R_D} \times V_{DD}$$

If $V_{in} = V_{DD} \rightarrow V_{out} = V_{DD}$

No, this circuit does not invert.

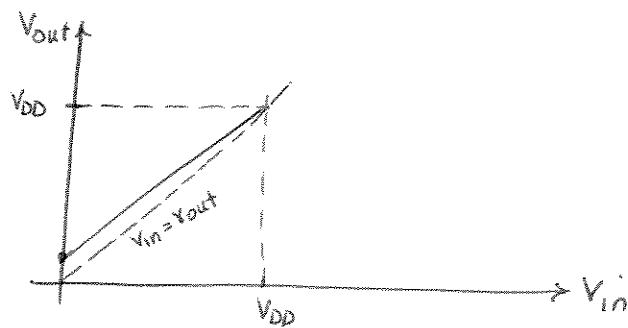(b) A trip point cannot be found for this circuit because $V_{out} = V_{in}$ line does not intersect the transfer characteristic of this buffer.



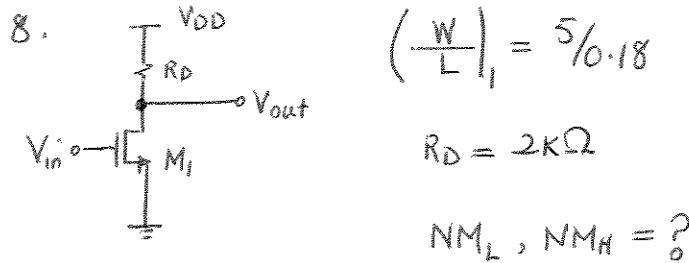

Small signal gain of the circuit is equal to $-g_m R_D$

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1, \quad V_{GS} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH} = \frac{1}{100 \times 10 \times \frac{5}{0.18} \times 2000} + 0.4$$

$$\boxed{V_{IL} = 0.58 \text{ V}}$$

To determine NM_H , we note that V_{in} drives M_1 into the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH,N}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH,N}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D$$

$$+ 2V_{out}$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \text{ @ } V_{IH}$$

$$-1 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[-2(V_{in} - V_{TH,N}) + 2V_{out} \right] R_D$$

$$I = \mu_n C_{ox} \left(\frac{W}{L}\right) \left[-V_{in} + V_{THN} + 2V_{out} \right] R_D$$

$$\frac{I}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} = -(V_{in} - V_{THN}) + 2V_{out}$$

$$V_{out} = \frac{1}{2\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + \frac{V_{in} - V_{THN}}{2} \rightarrow V_{out} = 0.5V_{in} - 0.11$$


Substituting this in (1) yields:

$$0.5V_{in} - 0.11 = 1.8 - \frac{1}{2} \times 100 \times 10 \times \frac{5}{0.18} \times 2000 \left[2(V_{in} - 0.4)(0.5V_{in} - 0.11) - (0.5V_{in} - 0.11)^2 \right]$$

$$0.75V_{in}^2 - 0.33V_{in} - 0.6117 = 0$$

$$V_{in} = V_{IH} = 1.15$$
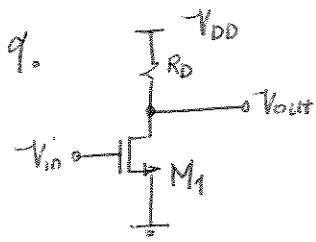
$$NM_H = V_{DD} - V_{IH} = 1.8 - 1.15 \rightarrow NM_H = 0.65V$$



Small signal gain of the inverter is equal to $-g_m R_D$

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{GS} - V_{TH,N} \right)$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{GS} - V_{TH,N} \right) R_D = 1, \quad V_{GS} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{IL} - V_{TH,N} \right) R_D = 1 \rightarrow V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right) R_D} + V_{TH,N}$$

If we double the value of $\left(\frac{W}{L} \right)$ or R_D

$$V_{IL} = \frac{1}{100 \times 10 \times \frac{5}{0.18} \times 2000 \times 2} + 0.4 \rightarrow V_{IL} = 0.19$$

To determine NM_H , we note that V_{in} drives M_1 into the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D. \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[2V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right]$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \quad \textcircled{a} \quad V_{TH}$$

$$V_{out} = \frac{1}{2 \mu_n C_{ox} \left(\frac{W}{L} \right) R_D} + \frac{V_{in} - V_{TH,N}}{2}$$

Doubling ($\frac{w}{L}$), or RD leads to

$$V_{out} = 0.5V_{in} - 0.155$$


Substituting in (1) yields:

$$0.5V_{in} - 0.155 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \times 2 \left[2(V_{in} - 0.4)(0.5V_{in} - 0.155) - (0.5V_{in} - 0.155)^2 \right]$$

$$0.75V_{in}^2 - 0.465V_{in} - 0.251925 = 0$$

$$V_{in} = 0.967V \rightarrow NM_H = 1.8 - 0.967$$

$$NM_H = 0.833V$$

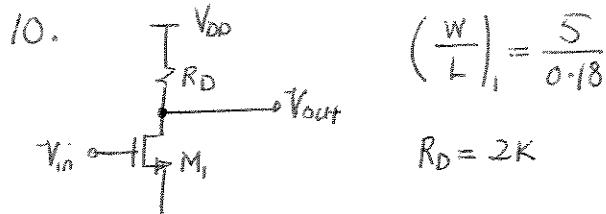

$$\left(\frac{W}{L}\right)_1 = \frac{5}{0.18}$$

$$R_D = 2K$$

NM_L and $NM_H = ?$ if $\frac{\partial V_{out}}{\partial V_{in}} = -0.5$ instead of -1

Small signal gain of the inverter is equal to " $-g_m R_D$ "

and $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 0.5$$

$$V_{IL} = \frac{1}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N} = \frac{1}{2 \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000} + 0.4$$

$V_{IL} = 0.49$

which is less than 0.58 obtained in problem 8.

To determine NM_H , note that M_1 operates in the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = 0.5 \text{ @ } V_{IH}$$

$$-0.5 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[-(V_{in} - V_{TH,N}) + 3V_{out} \right] R_D$$

$$V_{out} = \frac{1}{3\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{THN}}{3} \longrightarrow V_{out} = -73.33 \times 10^{-3} + 0.333 V_{in}$$

$$\text{or } V_{\text{out}} = -\frac{0.22}{3} + \frac{V_{\text{in}}}{3}$$

Substituting in (1) yields:

$$-\frac{0.22}{3} + \frac{V_{\text{in}}}{3} = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[2(V_{\text{in}} - 0.14) \left(-\frac{0.22}{3} + \frac{V_{\text{in}}}{3} \right) - \left(-\frac{0.22}{3} + \frac{V_{\text{in}}}{3} \right)^2 \right]$$

$$5V_{\text{in}}^2 - 2.2V_{\text{in}} - 5.59 = 0$$


$$V_{\text{in}} = V_{\text{IH}} = 1.3$$

$$NM_{\text{H}} = 1.8 - 1.3$$

$$NM_{\text{H}} = 0.5 \text{ V}$$

less than 0.65 V obtained in problem 8 because

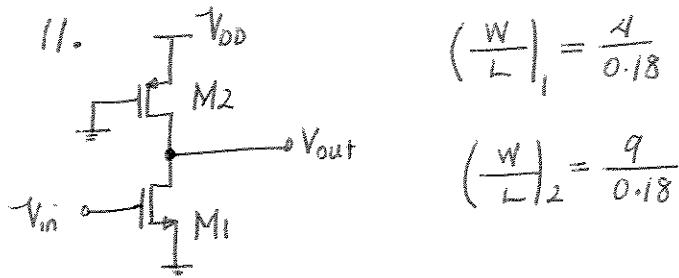V_{IH} is now further pushed up toward V_{dd} .



To calculate V_{IL} , we assume that M_1 and M_2 operate in saturation and triode region respectively.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH,N})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{THN}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{TH,P}|) \left(-\frac{\partial V_{out}}{\partial V_{in}} \right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}} \right) \right]$$

By substituting $\frac{\partial V_{out}}{\partial V_{in}}$ with "-1" in the above relationship:

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{THN}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{TH,P}|) - 2(V_{DD} - V_{out}) \right]$$

$$-V_{out} = \frac{\mu_n C_{ox} \left(\frac{W}{L} \right)_1}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2} (V_{in} - V_{THN}) + |V_{THP}| = \frac{100 \times 10 \times 4 / 0.18}{50 \times 10^{-6} \times 9 / 0.18} (V_{in} - 0.4) + 0.5$$

$$V_{out} = 0.144 + 0.88 V_{in} \quad \text{or} \quad \boxed{V_{out} = \frac{8}{9} V_{in} + \frac{1.3}{9}}$$

Substituting V_{out} in (1) by the derivation versus V_{in} gives :

$$136 V_{in}^2 - 108.8 V_{in} - 115.13 = 0$$

$$\boxed{V_{in} = V_{IL} = NM_L = 1.4 V}$$

To calculate V_{IH} , we assume that M₁ and M₂ operate in the triode and saturation region respectively.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{THN}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left(V_{DD} - |V_{MPL}| \right)^2 \quad (2)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 0$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = 0$$

$$-V_{out} = \frac{V_{in} - V_{THN}}{2} \quad \text{Substituted in (2) yields:}$$

$$V_{in} = \sqrt{\frac{3}{2}} (V_{DD} - |V_{MPL}|) + V_{THN}$$

$V_{in} = 2 \rightarrow V_{out} = 0.8$ This value of V_{out} puts M₂ into the triode region so our initial assumption is not correct

Now we assume that both M₁ and M₂ operate in the triode region.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{THN}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{MPL}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (3)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times$$

$$\left[2(V_{DD} - |V_{MP}|) \left(-\frac{\partial V_{out}}{\partial V_{in}} \right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}} \right) \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times$$

$$\left[2(V_{DD} - |V_{MP}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = - \frac{\frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN}) - |V_{MP}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}}{2 \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} - 1}$$

$$V_{out} = \frac{8}{7} V_{in} - 1.1$$

After substituting in (3) it leads to :


$$2 \cdot 1769 V_{in}^2 - 4 \cdot 19 V_{in} + 0.576 = 0$$

$$V_{in} = 1.77 V$$

$$V_{out} = 0.93 V \rightarrow \text{The assumption is correct}$$

$$V_{IH} = 1.77 V \rightarrow NM_H = 1.8 - 1.77$$

$$NM_H = 0.03 V$$

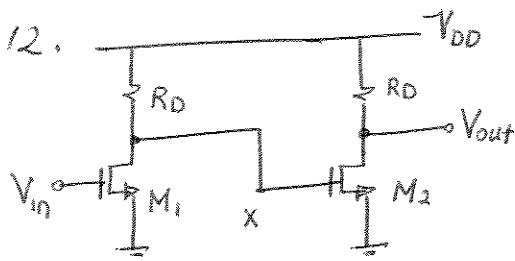

The small signal gain of the circuit is equal to $-g_m R_D$ and since

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{THN})$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{IL} - V_{THN}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_D} + V_{THN} = \frac{2}{S} + 0.4 \quad ; \quad \left(\frac{W}{L} \right)_{1,2} = S$$

Now we calculate the output of M₁ for $V_{in} = V_{DD}$:

$$V_{DD} - R_D I_D = V_{out}$$

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{THN}) V_{out} - V_{out}^2 \right] R_D = V_{out} \quad ; \quad \left(\frac{W}{L} \right)_{1,2} = S$$

$$1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times S \left[2(1.8 - 0.4) \left(\frac{2}{S} + 0.4 \right) - \left(\frac{2}{S} + 0.4 \right)^2 \right] \times 5000 = \left(\frac{2}{S} + 0.4 \right)$$

$$1.8 - 0.25 \times \left[2.8 \left(2 + 0.4S \right) - S \left(\frac{2}{S} + 0.4 \right)^2 \right] = \frac{2}{S} + 0.4$$






$$1.8S - 0.25 \times \left[2.8 \left(2S + 0.4S^2 \right) - S \left(\frac{2}{S} + 0.4 \right)^2 \right] = 2 + 0.4S$$


$$1.8S - 0.25 \times \left[5.6S + 1.12S^2 - 4 - 1.6S - 0.16S^2 \right] = 2 + 0.4S$$

$$0.24S^2 - 0.4S + 1 = 0$$

$$\Delta < 0!$$

13.

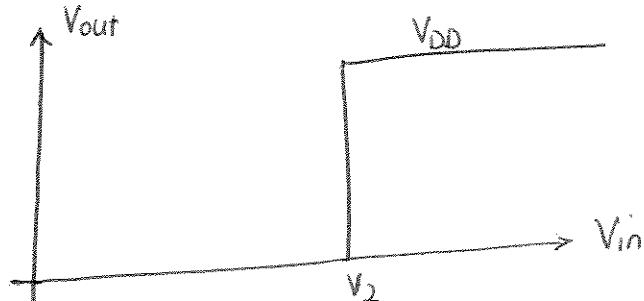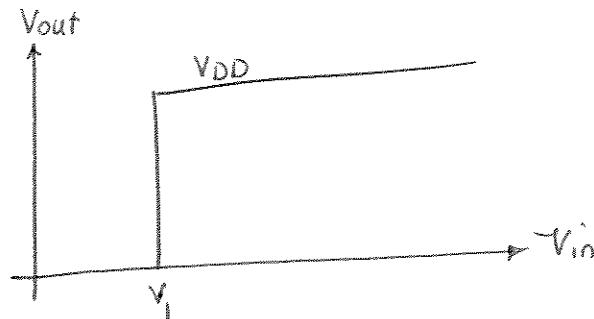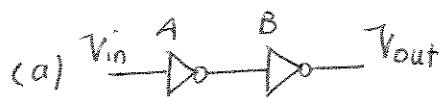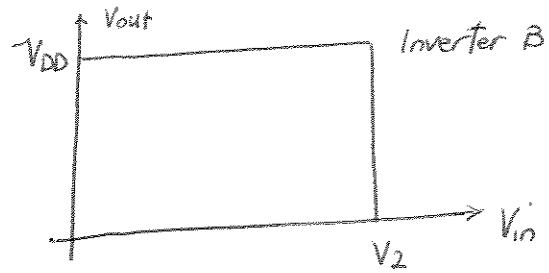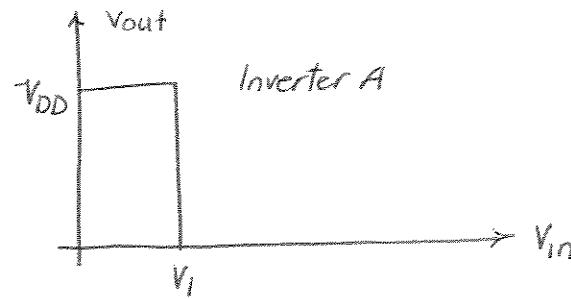

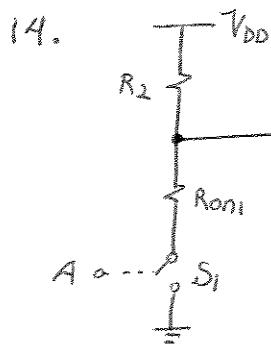

$$R_{on1} \ll R_2 \rightarrow V_{out, min} \approx 0$$

$$(a) V_{out}(t) = V_{out}(\bar{0}) + [V_{DD} - V_{out}(\bar{0})] \left(1 - \exp \frac{-t}{R_2 C_L} \right) t > 0$$

Note that $V_{out}(\bar{0}) = 0$, $V_{out}(\infty) = V_{DD}$

$$V_{out}(t) = V_{DD} \times \left(1 - \exp \frac{-t}{R_2 C_L} \right) t > 0$$

$$0.95 V_{DD} = V_{DD} \times \left(1 - \exp \frac{-T_{95\%}}{R_2 C_L} \right)$$

$T_{95\%} = 3 R_2 C_L$

$$(b) V_{out}(t) = V_{out}(\bar{0}) + [V_{out}(\infty) - V_{out}(\bar{0})] \times \left(1 - \exp \frac{-t}{R_2 C_L} \right)$$

$$V_{out}(t) = V_{DD} + [0 - V_{DD}] \times \left(1 - \exp \frac{-t}{R_2 C_L} \right)$$


$$V_{out}(t) = V_{DD} \exp \frac{-t}{R_2 C_L}$$

$$0.05 V_{DD} = V_{DD} \exp \frac{-T_{0.05}}{R_2 C_L}$$

$T_{0.05} = 3 R_2 C_L$

If $R_{on1} \ll R_2$, inverter exhibits equal rise and fall time (or low-to-high and high-to-low delay) at the output.

15.

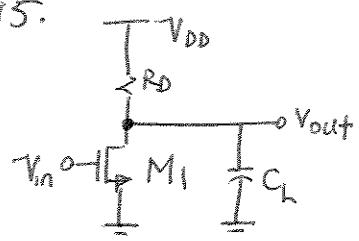

$$C_L = 50 \text{ fF}$$

$$T_R = 100 \text{ pS}$$


$$T_R = 3 Z_{out}$$

$$R_{D,max} = ?$$

$$T_R = 3 R_D C_L = 100 \text{ pS}$$

$$R_D \leq \frac{100 \text{ pS}}{3 \times 50 \text{ fF}}$$

$$R_D \leq 666.67 \Omega$$

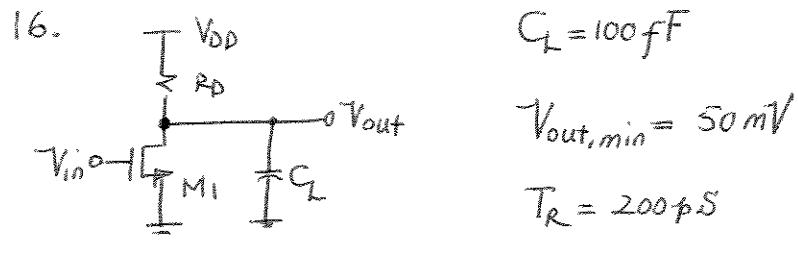

$$C_L = 100 \text{ fF}$$

$$V_{out, min} = 50 \text{ mV}$$

$$T_R = 200 \text{ pS}$$

$$R_D, \left(\frac{W}{L}\right)_1 = ?$$

$$T_R = 3C_{out}$$

$$T_R = 3R_D C_L$$

$$200 \times 10^{-12} = 3 \times R_D \times 100 \times 10^{-15}$$

$$R_D = 666.667 \Omega$$

$V_{in} = V_{DD}$ places M1 in the triode region

$$V_{out, min} = V_{DD} - R_D I_{D, max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_D \left[2(V_{DD} - V_{THN}) V_{out, min} - V_{out, min}^2 \right]$$


Neglecting the 2nd-order term in the square brackets yields:

$$V_{out, min} = \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L} \right)_1 R_D (V_{DD} - V_{TH})}$$

$$50 \times 10^{-3} = \frac{1.8}{1 + 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 \times 666.7 \times (1.8 - 0.4)}$$

$$\left(\frac{W}{L} \right)_1 = 375$$

17.

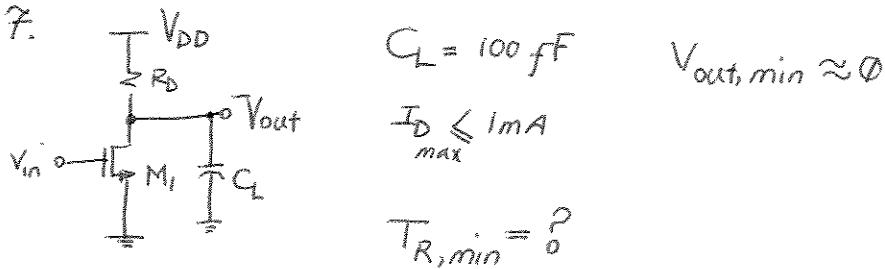

$$I_{D, max} = \frac{V_{DD} - V_{out, min}}{R_D}$$

$$\frac{-3}{10} = \frac{1.8 - 0}{R_D}$$

$$R_D = 1.8 \text{ k}\Omega$$

$$V_{out}(t) = V_{out}(0) + [V_{out}(\infty) - V_{out}(0)] \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) t > 0$$

$$V_{out}(t) = V_{out, min} + [V_{DD} - V_{out, min}] \times \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) t > 0$$


$$V_{out}(t) = V_{DD} \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) t > 0$$

$$0.1 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{10\%}}{R_D C_L}\right)\right) \rightarrow T_{10\%} = 0.105 R_D C_L$$

$$0.9 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{90\%}}{R_D C_L}\right)\right) \rightarrow T_{90\%} = 2.3 R_D C_L$$

$$T_R = T_{90\%} - T_{10\%} = 2.197 \times 1.8 \times 10 \times 100 \times 10^{-15}$$

$$T_R = 395.5 \text{ ps}$$

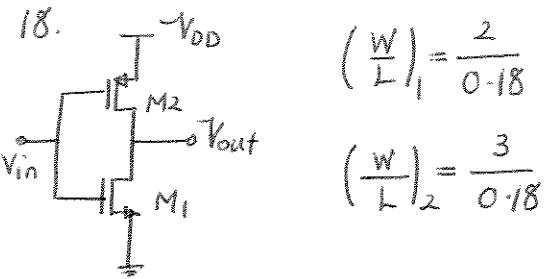

$$\left(\frac{W}{L}\right)_1 = \frac{2}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{3}{0.18}$$

$$I_{D1} = I_{D2}$$

At the trip point $V_{in} = V_{out}$; therefore, both M_1 and M_2 operate in the Saturation region.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(V_{in}^o - V_{THN}\right)^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left(V_{DD} - V_{in}^o - |V_{THP}|\right)^2$$

$$V_{in}^o = \frac{-V_{DD} - |V_{THP}| + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2} \times V_{THN}}}{1 + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}}}$$


$$V_{in}^o = \frac{1.8 - 0.5 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2} \times 0.4}{1 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2}}$$

$$V_{in} = V_{out} = 0.82 \text{ V}$$


$$I_{D1} = I_{D2} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) \left(0.82 - 0.4\right)^2$$

$$I_{D1} = I_{D2} = 97 \text{ } \mu\text{A}$$

19.

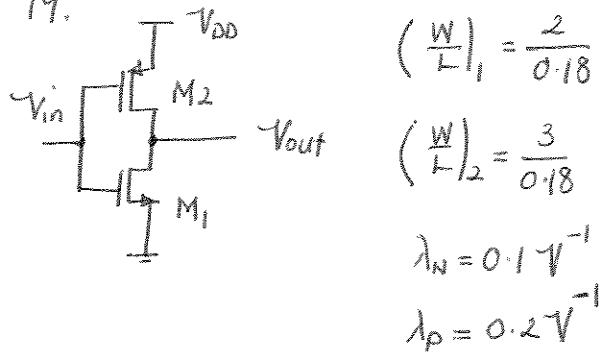

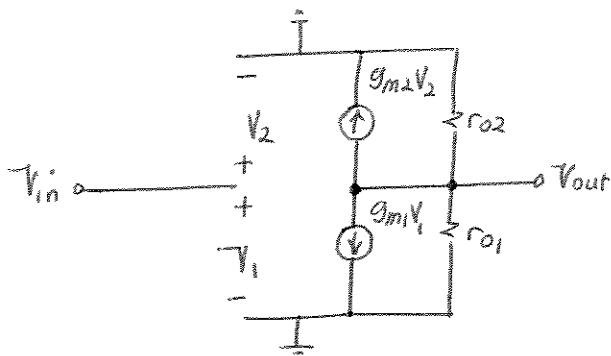Replacing M₁ and M₂ with their small-signal model in the saturation region yields:



$$V_{out} = (-g_{m1}V_1 - g_{m2}V_2) / (r_{o1} \parallel r_{o2})$$

$$V_1 = V_2 = V_{in}$$

$$V_{out} = - (g_{m1} + g_{m2}) (r_{o1} \parallel r_{o2}) V_{in}$$

$$\frac{V_{out}}{V_{in}} = - (g_{m1} + g_{m2}) (r_{o1} \parallel r_{o2})$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{THN})^2$$

$$g_{m1} = \frac{\partial I_{D1}}{\partial V_{in}} = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{THN}) = \frac{2 I_{D1}}{V_{in} - V_{THN}}$$

$$g_{m1} = \frac{2 \times 9.7 \times 10^{-5}}{(0.817 - 0.4)} \rightarrow \boxed{g_{m1} = 4.641 \times 10^{-4} V^{-1}}$$

$$g_{m2} = \frac{2I_{D2}}{(V_{SG} - |V_{TH}|)} = \frac{2 \times 9.7 \times 10^{-5}}{(1.8 - 0.817 - 0.5)} \rightarrow g_{m2} = 4.02 \times 10^{-4} \text{ A}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})^2 \lambda \simeq \lambda I_D$$

$$r_o \simeq \frac{1}{\lambda I_D}$$

$$r_{ON} \simeq \frac{1}{0.1 \times 9.7 \times 10^{-5}} = 103.17 \text{ k}\Omega$$

$$r_{OP} \simeq \frac{1}{0.2 \times 9.7 \times 10^{-5}} = 51.58 \text{ k}\Omega$$

$$\text{Gain} = \frac{-V_{out}}{-V_{in}} = -(4.641 \times 10^{-4} + 4.02 \times 10^{-4}) (51.58 \text{ k} \parallel 103.17 \text{ k})$$


$$\boxed{\text{Gain} = -29.8}$$

20.

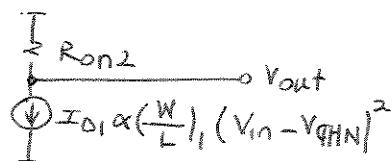(a) Length of M_1 is increased

Let's assume that $V_{in} < V_{TH1}$, as a result M_1 is off and M_2 is on operating in the triode region. As V_{in} increases beyond V_{TH1} , M_1 starts pulling current (conducting) in the saturation region while M_2 is still in the triode region, operating as a resistor; therefore,

CMOS inverter can be modelled as follows:




By increasing L_1 , I_{D1} is weakened due to the inverse proportionality; as a result, an excess V_{in} is required to drop V_{out} to the point where $V_{out} = V_{in} + |V_{TH2}|$ and M_2 is placed at the edge of saturation.

Therefore characteristic is shifted to the right and it will be steeper at the gain region where both M_1 and M_2 are in saturation region.

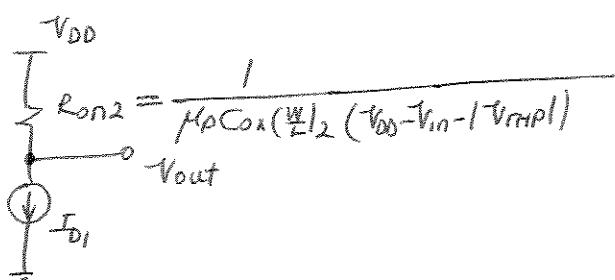
(b) Length of M_2 is increased

Again if we assume that $V_{in} < V_{TH1}$, M_1 is off and M_2 is operating in the triode region with no current. By increasing

V_{in} above V_{TH1} , M_1 conducts in the saturation region while M_2 is operating in the triode region. Using the same models as used in part (a) yields:



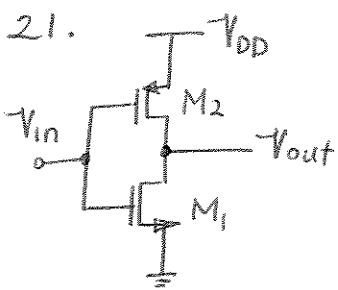
By increasing L_2 , R_{on2} becomes larger; as a result, lower value of I_{D1} causes comparable voltage drop at the output. This will drive M_2 into the saturation with lower current (I_{D2}) and, hence, lower value of V_{in} . Therefore, characteristic is shifted to the left and small signal gain will be higher.



$$\left(\frac{W}{L}\right)_1 = \frac{3}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{7}{0.18}$$

VTC looks like the following figure

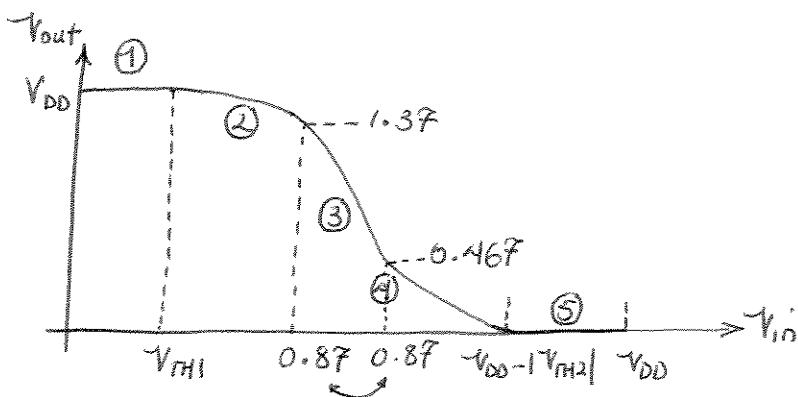

① M₁ off, M₂ in triode region

$$I_{D1} = \emptyset$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|) V_{SD} - V_{SD}^2 \right] = \emptyset$$

$$V_{SD} = 0 \rightarrow V_{out} = V_{DD} \quad (1)$$

② M₁ in saturation, M₂ in triode region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (V_{in} - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times \left[2(1.8 - V_{in} - 0.5) \times (1.8 - V_{out}) - (1.8 - V_{out})^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7 \left[2(1.3 - V_{in})(1.8 - V_{out}) - (1.8 - V_{out})^2 \right] \quad (2)$$

If V_{out} falls significantly, M_2 enters saturation. That is $V_{out} = V_{in} + |V_{TH2}|$, then M_2 is about to exit the triode region.

Replacing V_{out} by $V_{in} + |V_{TH2}|$ in (2) leads to:

$$6(V_{in} - 0.4)^2 = 7 \left[2(1.3 - V_{in})(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7(1.3 - V_{in})^2 \rightarrow \sqrt{\frac{6}{7}} (V_{in} - 0.4) = (1.3 - V_{in})$$

$$V_{in} = 0.867V, V_{out} = 1.37$$

$$(3) \quad \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_1 V_{out}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 \times [1 + \lambda_2 (V_{DD} - V_{out})]$$

$$V_{out} = \frac{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 - \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}{\lambda_2 \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 + \lambda_1 \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}$$

$$V_{out} = \frac{\frac{7}{7}(1.3 - V_{in})^2 - 6(V_{in} - 0.4)^2}{7\lambda_2 (1.3 - V_{in})^2 + 6\lambda_1 (V_{in} - 0.4)^2} \quad (3)$$

in region (3) M_1 and M_2 are both in saturation.

④ M₁ in triode region, M₂ in saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \times \\ (V_{DD} - V_{in} - |V_{TH2}|)^2 \quad (4)$$

$$6 \left[2(V_{in} - 0.4) V_{out} - V_{out}^2 \right] = 7 (1.3 - V_{in})^2$$

If V_{out} falls sufficiently, M₁ enters the triode region. That is, if
 $V_{in} = V_{out} + V_{TH1}$. Then M₁ is about to enter the triode region.

By substituting V_{in} with V_{out} + 0.4 in (4), we have:

$$6 \left[2V_{out}^2 - V_{out}^2 \right] = 7 (0.9 - V_{out})^2$$

$$V_{out} = 0.467, V_{in} = 0.867$$

As channel length modulation has been neglected in this calculation the value of input voltage that makes CMOS inverter transition from region ② to ③ is the same as that which makes inverter transition from region ③ to ④.

The slope in region ③ is infinit; however, we assume a finite slope in that region to emphasize the behavior of inverter as to producing a high gain.


⑤ M₁ in triode region, M₂ off

$$I_{D2} = 0, I_{D1} = 0$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] = 0 \rightarrow V_{out} = 0$$

22.

$$V_{in} = V_{out} = 0.5 \text{ V}$$

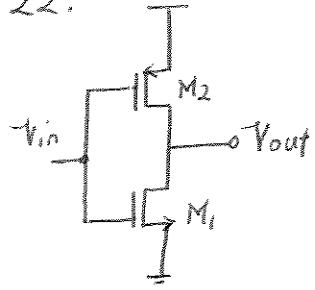

M_1 and M_2 are both in saturation region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 (0.5 - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L} \right)_2 (1.8 - 0.5 - 0.5)^2$$

$$\left(\frac{W}{L} \right)_1 / \left(\frac{W}{L} \right)_2 = 32$$

23. The value of the trip point has to be larger than the threshold voltage of NMOS transistor, 0.4 V . Therefore, 0.3 V cannot be the trip point of such an inverter.


24.

- (a) If the inverter exhibits a very high voltage gain around the trip point, the range of input voltage values which guarantees that M₁ and M₂ are in saturation region is very narrow. Therefore this range can be fairly approximated with only one value of input voltage.

(b) $(W/L)_1 = 3/0.18$ and $(W/L)_2 = 7/0.18$

To calculate the minimum input voltage at which both transistors operate in saturation we assume

M₁ saturation
M₂ triode

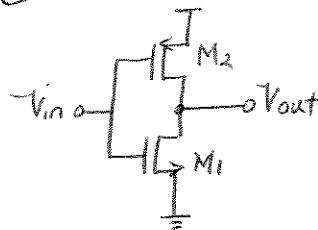

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 [2(V_{DD} - V_{in} - |V_{TH2}|)(V_{out} - V_{DD}) - V_{out} + |V_{TH2}|] \text{ places M}_2 \text{ at the edge of saturation } (V_{out} - V_{DD})^2$$

$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times [2(1.8 - V_{in} - 0.5)(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)]^2$$

$V_{in} = 0.867$
min

To calculate $V_{in,max}$. we assume that M₁ and M₂ are in triode and Saturation region respectively

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [2(V_{in} - V_{TH1})(V_{out} - V_{DD})^2] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

When M_1 is just going to leave the saturation and enters the triode region

$$V_{in} = V_{out} + 0.4^{(V_{M1})}$$

$$\frac{1}{2} \times 100 \times 10 \times \frac{-6}{0.18} \times \left[2(V_{out} + V_{M1} - V_{M1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \times 50 \times 10 \times \frac{-6}{0.18} \times (V_{DD} - V_{in} - |V_{M2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (V_{DD} - V_{out} - V_{M1} - |V_{M2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (0.4 - V_{out})^2$$

$$V_{out} = 0.467 \text{ V}, \boxed{V_{in} = 0.867 \text{ max}}$$

To find the trip point, M_1 and M_2 are assumed to be in saturation.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{in} - V_{M1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{M2}|)^2$$


$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times (1.8 - V_{in} - 0.5)^2$$

$$\boxed{V_{in}^o = 0.867 \text{ (a) trip point}}$$




$$V_{in, trip} - V_{in, min} = 0$$

$$V_{in, max} - V_{in, trip} = 0$$

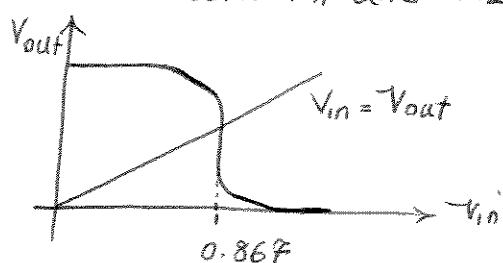
This result is not surprising because VTC of inverter has infinite slope at the region where both M_1 and M_2 are in saturation region



25.

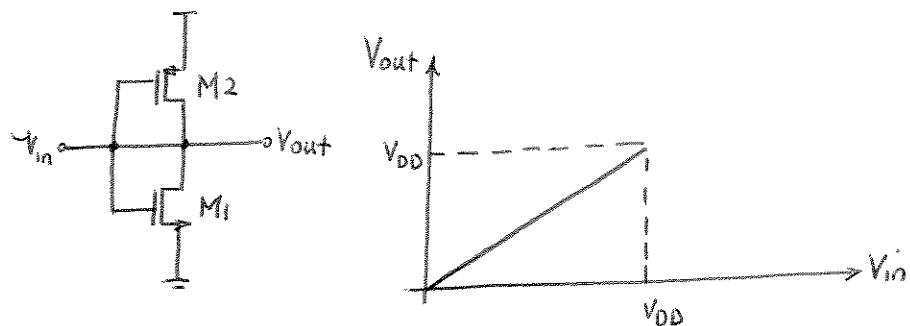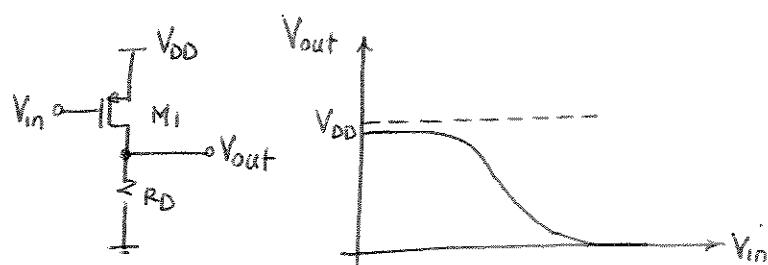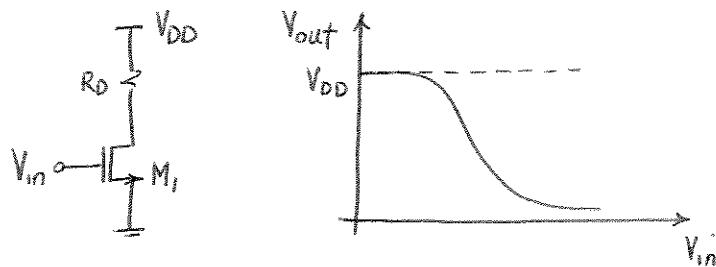

26.

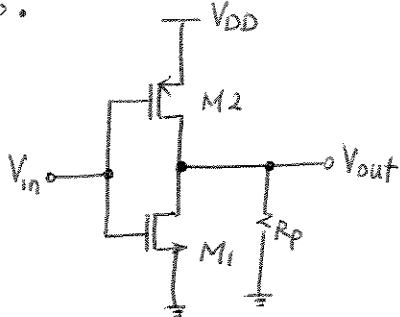


$$R_P = 2K$$

$$V_{OL}, V_{OH}, V_{in, trip} = ?$$

$$(W/L)_1 = 3/0.18$$

$$(W/L)_2 = 5/0.18$$

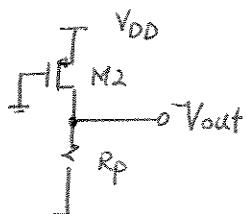To calculate V_{OH} , V_{in} is assumed to be 0V



$$I_{D2} = \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$I_{D2} = \frac{V_{out}}{R_P}$$

$$\frac{V_{out}}{R_P} = \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$V_{out}^2 - 0.28V_{out} - 1.44 = 0$$

$$V_{out} = V_{OH} = 1.348V$$

$$V_{OL} = 0 \quad \text{because } M_2 \text{ is off for } V_{in} = V_{DD}$$


(a) trip point $V_{in} = V_{out}$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_P}$$

$$\frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L}\right)_2 \left(V_{DD} - V_{in} - |V_{TH2}| \right)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(V_{in} - V_{TH1} \right)^2 + \frac{V_{out}}{2000}$$

$$0.05V_{out}^2 + 0.59V_{out} - 0.3745 = 0 \rightarrow V_{in} = V_{out} = 0.6V$$

27.

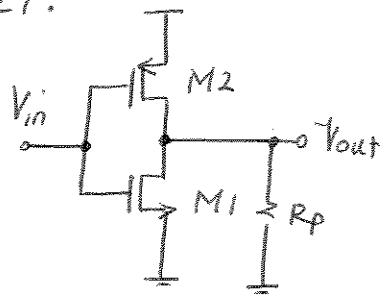

$$R_p = 2k\Omega$$

$$(W/L)_1 = 3/0.18$$

$$(W/L)_2 = 5/0.18$$

$$V_{in}^0 = V_{out} = 0.6 \text{ V} \quad \textcircled{a} \text{ trip point}$$

With R_p

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05 V_{out}^2 + 0.59 V_{out} - 0.3745 = 0$$

$$V_{in} = V_{out} = 0.6 \text{ V}$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (0.6 - 0.4)^2$$

$$I_{D1} = 3.33 \times 10^{-5} \text{ A}$$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} = 3.33 \times 10^{-5} + \frac{0.6}{2000}$$

$$I_{D2} = 3.35 \times 10^{-4} \text{ A}$$

$$g_{m1} = \frac{2I_{D1}}{V_{eff1}} = \frac{2 \times 3.33 \times 10^{-5}}{(0.6 - 0.4)} \rightarrow g_{m1} = 3.3 \times 10^{-3} \text{ A/V}$$

$$g_{m2} = \frac{2I_{D2}}{V_{eff2}} = \frac{2 \times 3.35 \times 10^{-4}}{(1.8 - 0.6 - 0.5)} \rightarrow g_{m2} = 9.4 \times 10^{-3} \text{ A/V}$$


$$A_V = -(g_{m1} + g_{m2}) \times R_p$$

$$A_V = - (3.3 \times 10^{-3} + 9.4 \times 10^{-3}) \times 2000$$

$$A_V = -25.4$$

Without R_p

$$A_V \Rightarrow -\infty$$

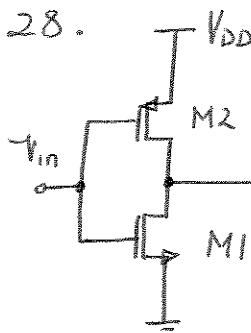

$$\left(\frac{W}{L}\right)_1 = 5/0.18$$

$$\left(\frac{W}{L}\right)_2 = 11/0.18$$

$$NM_L \text{ and } NM_H = ?$$

To calculate NM_L , M_1 and M_2 are assumed to operate in the saturation and triode region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 [2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2] \quad (1)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 [-2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \times \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}}]$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 [2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD}] \quad (2)$$

Obtaining V_{OH} from (2) and substituting in (1) yields:

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100}{50} \times \frac{5}{11} = \frac{10}{11}$$

$$V_{IL} = \frac{2\sqrt{10/11}(1.8 - 0.4 - 0.5)}{(10/11 - 1)\sqrt{10/11 + 3}} - \frac{1.8 - (10/11) \times 0.4 - 0.5}{10/11 - 1}$$

$V_{IL} = 0.7516 \text{ V}$

To determine NM_H , M_1 and M_2 are assumed to operate in the triode and saturation region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}| - V_{in})^2 \quad (3)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = -\mu_p C_{ox} \left(\frac{W}{L} \right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \text{ yields}$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[V_{out} - V_{in} + V_{TH1} + V_{out} \right] = -\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)$$

$$100 \times 5 \times \left[2V_{out} - (V_{in} - 0.4) \right] = -50 \times 11 \times (1.8 - 0.5 - V_{in})$$

$$V_{out} = 1.05V_{in} - 0.915 \quad (4)$$

Substituting (4) in (3) yields an equation versus V_{in} as follows:

$$10 \left[2(V_{in} - 0.4)(1.05V_{in} - 0.915) - (1.05V_{in} - 0.915)^2 \right] = 11(1.3 - V_{in})^2$$

$$1.025V_{in}^2 - 21.115V_{in} + 19.64225 = 0$$

$$V_{in} = V_{IH} = 0.9765 \text{ V}$$

$$NM_H = V_{DD} - V_{IH}$$

$NM_H = 0.823 \text{ V}$

$$29. \quad NM_L = 0.6 \text{ V}$$

$$(W/L)_1 / (W/L)_2 = ?$$

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$$

$$0.6 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - a0.4 - 0.5}{a-1}$$

$$a = 3\sqrt{\frac{a}{a+3}} - \frac{1.3 - 0.4a}{0.6} + 1$$

$$a = \frac{a+3}{9} \times \left[a-1 + \frac{1.3 - 0.4a}{0.6} \right]^2$$

$$\boxed{a=1}$$

$$(W/L)_1 / (W/L)_2 = \frac{\mu_p C_{ox}}{\mu_n C_{ox}} = \frac{1}{2}$$


$$\boxed{(W/L)_1 / (W/L)_2 = \frac{1}{2}}$$

$$30. V_{IL} = \frac{2\sqrt{a}(V_{DD} - |V_{TH1}| - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - a|V_{TH1}| - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$

$$a \rightarrow 0 \quad V_{IL} = V_{DD} - |V_{TH2}|$$

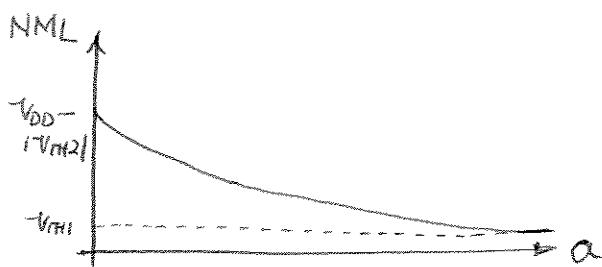
$$a \rightarrow \infty \quad V_{IL} = V_{TH1}$$




If $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$, it implies that PMOS transistor is

extremely stronger than NMOS. Therefore, as V_{in} increases from 0V, the output of inverter stays at V_{DD} until input reaches $V_{DD} - |V_{TH2}|$.

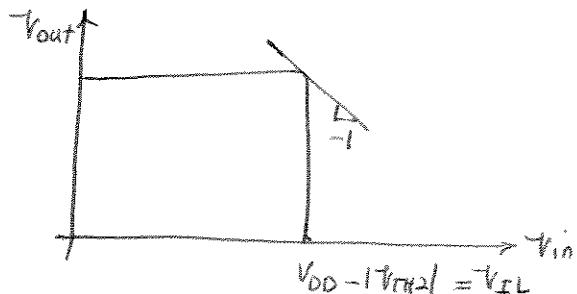At that point, PMOS is cut off and V_{out} sharply drops to 0V.



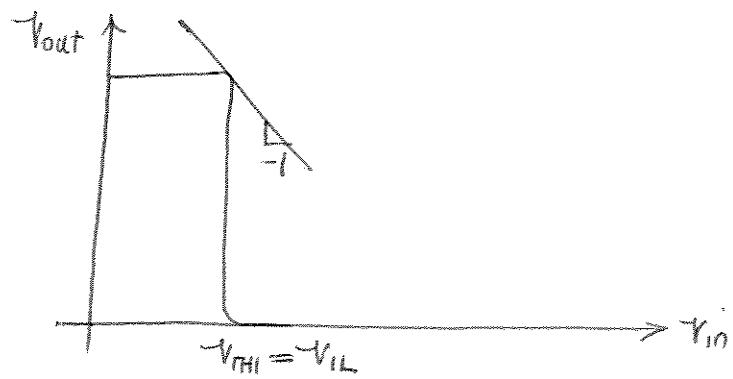When $a \rightarrow \infty$, NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to 0V.




31.

$$NM_H = V_{DD} - \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} + \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n(\frac{W}{L})_1}{\mu_p(\frac{W}{L})_2}$$


$$a \rightarrow 0 \quad NM_H = |V_{TH2}|, \quad V_{IH} = V_{DD} - |V_{TH2}|$$
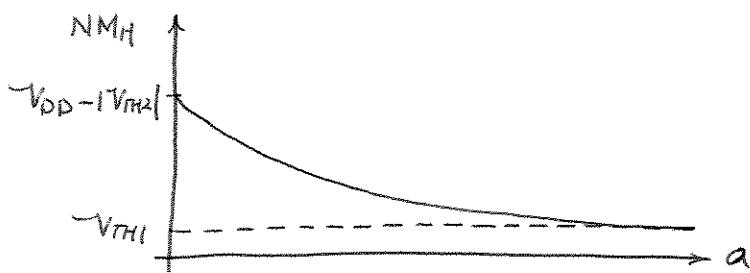
$$a \rightarrow \infty \quad NM_H = V_{DD} - V_{TH1}, \quad V_{IH} = V_{TH1}$$




If $a = \frac{\mu_n}{\mu_p} \times \frac{(\frac{W}{L})_1}{(\frac{W}{L})_2} \rightarrow 0$, it implies that PMOS transistor is much stronger than NMOS. Therefore, as V_{in} increases from 0V, the output of inverter remains at V_{DD} until input reaches $V_{DD} - |V_{TH2}|$.

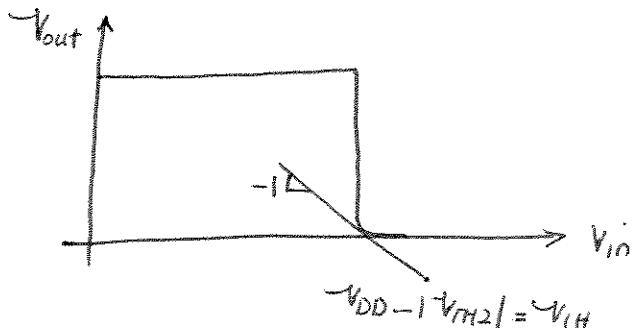At that point, PMOS is cut off and V_{out} sharply drops to 0V.




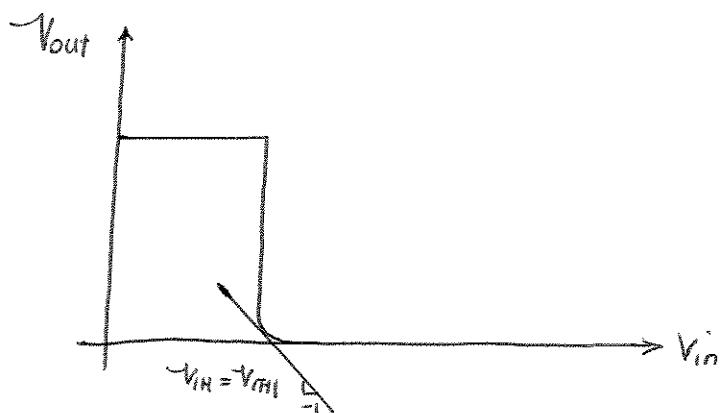When "a" approaches infinity, NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to 0V.



Note that the separation between V_{IH} and V_{IL} depends on the slope of VTC in the transition region. If "a" approaches either "0" or infinity, VTC exhibits infinite gain in its transition region. Therefore V_{IL} and V_{IH} coincide.

32.

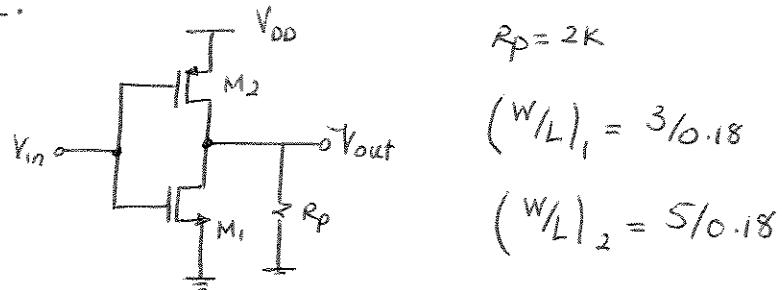

$$R_P = 2k$$

$$NML, NMH = ?$$

$$(W/L)_1 = 3/0.18$$

$$(W/L)_2 = 5/0.18$$

To calculate NML, M₁ and M₂ are assumed to be in the saturation and triode region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_P} \quad (V_{in} = V_{IL})$$

$$\frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{R_P} \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L} \right)_2 \left[-2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right] =$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1}) + \frac{1}{R_P} \frac{\partial V_{out}}{\partial V_{in}}$$

$$\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{IL} - V_{TH1}) - \frac{1}{R_P} = \mu_P C_{ox} \left(\frac{W}{L} \right)_2 \left[2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

$$V_{OH} = 1.01 V_{IL} + 0.73$$

Replacing V_{out} in (1) with its equivalent versus V_{IL} obtained from (2) yields:

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - V_{IL} - |V_{TH2}|)(V_{DD} - 1.1V_{IL} - 0.73) - (V_{DD} - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{IL} - V_{TH1})^2 + \frac{1.1V_{IL} + 0.73}{R_P}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \left[2(1.8 - V_{IL} - 0.5)(1.8 - 1.1V_{IL} - 0.73) - (1.8 - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} (V_{IL} - 0.4)^2 + \frac{1.1V_{IL} + 0.73}{2000}$$

$$-52.5 \times 10^{-3} V_{IL} - 0.6195 V_{IL} + 0.229875 = 0$$

$$V_{IL} = NM_L = 0.36V \quad < V_{TH1} \quad \text{Not Acceptable !}$$

This is less than threshold voltage of M_1 ; therefore, this answer is not acceptable. It means that M_1 is off and should be left out in this calculation.

$$I_{D1} = 0, \quad I_{D2} = \frac{V_{out}}{R_P}$$

$$\mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] = -\frac{1}{R_P}$$

$$50 \times 10^{-6} \times \frac{5}{0.18} \times \left[2V_{OH} - V_{IL} - 0.5 - 1.8 \right] = -\frac{1}{2000}$$

$$V_{OH} = V_{out} = 0.5V_{IL} + 0.97 \quad (3)$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \times \left[2(1.8 - V_{IL} - 0.5)(1.8 - 0.5V_{IL} - 0.97) - (1.8 - 0.5V_{IL} - 0.97)^2 \right] =$$

$$\frac{0.5V_{IL} + 0.97}{2000}$$

$$0.1875 V_{IL} - 0.6225 V_{IL} + 0.192675 = 0$$

$$V_{IL} = NM_L = 0.345V$$

To determine NM_H , M_1 and M_2 are assumed to operate in the triode and saturation region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IH})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [2(V_{in} - V_{TH1}) V_{out} - V_{out}^2] +$$

$$\frac{V_{out}}{R_p} \quad (4)$$

$$-\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}}] + \frac{\partial V_{out}}{\partial V_{in}} \frac{1}{R_p}$$

$$-\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 [V_{out} - V_{in} + V_{TH1} + V_{out}] - \frac{1}{R_p}$$

$$-50 \times 10^{-6} \times \frac{5}{0.18} \times (1.8 - V_{in} - 0.5) = 100 \times 10^{-6} \times \frac{3}{0.18} \times (2V_{out} - V_{in} + 0.4) - \frac{1}{2000}$$

$$\boxed{V_{out} = \frac{0.1V_{in} + 0.59}{1.2}} \quad (5)$$


Combining eqns (4) and (5) yields:

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} (1.8 - V_{in} - 0.5)^2 = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \left[2(V_{in} - 0.4) \frac{0.1V_{in} + 0.59}{1.2} - \frac{(0.1V_{in} + 0.59)^2}{1.2^2} \right] + \frac{0.1V_{in} + 0.59}{1.2 \times 2000}$$

$$-0.291 V_{in}^2 + 1.3182 V_{in} - 0.75531 = 0$$

$$V_{in} = V_{IH} = 0.673 V \rightarrow \boxed{NM_H = V_{DD} - V_{II} = 1.127 V}$$

33.

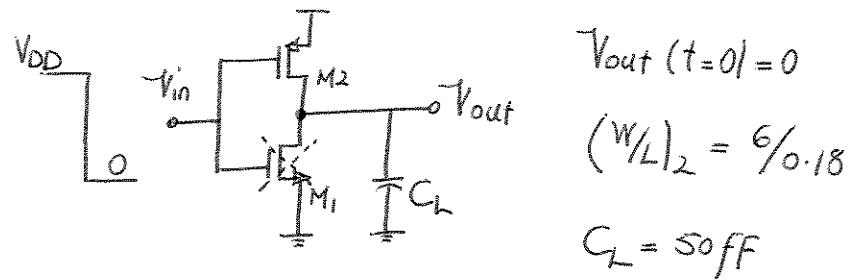

$$V_{out}(t=0) = 0$$

$$(W/L)_2 = 6/0.18$$

$$C_L = 50 \text{ fF}$$

$0 < V_{out} < |V_{TH2}|$; M₂ in the saturation

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{6}{0.18} (1.8 - 0.5)^2 = 1.4 \times 10^{-3} \text{ A}$$

$$V_{out}(t) = \frac{I_{D2}}{C_L} \times t$$

$$|V_{TH2}| = \frac{I_{D2}}{C_L} \cdot T_1 \rightarrow T_1 = \frac{C_L \times |V_{TH2}|}{I_{D2}} = 50 \times 10^{-15} \times (1.4 \times 10^{-3})^{-1} \times 0.5$$

$$T_1 = 17.75 \text{ p.s}$$

$|V_{TH2}| < V_{out} < V_{DD}/2$, M₂ in triode

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{out} + V_{DD}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{\frac{dV_{out}}{dt}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox} \left(\frac{W}{L} \right)_2}{C_L} dt$$

$$\frac{1}{(V_{DD} - V_{out}) \left[2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out}) \right]} = \frac{1}{2(V_{DD} - |V_{TH2}|)} \left[$$

$$\frac{1}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{1}{V_{DD} - V_{out}} \right]$$

$$\frac{1}{2(V_{DD} - |V_{TH2}|)} \left[\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{dV_{out}}{V_{DD} - V_{out}} \right] = \frac{L}{C_L} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 dt$$

$$\ln \frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t + C$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = K \cdot \exp \left[\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t \right]$$

Time origin is assumed to be at $t = T_1 = 17.75 \mu s$

$$V_{out}(t=0) = |V_{TH2}| \rightarrow K = 1$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\textcircled{a} \quad V_{out} = \frac{V_{DD}}{2} \quad T_2 = \frac{\ln (3 - 4|V_{TH2}|/V_{DD})}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)}$$

$$= \frac{\ln (3 - 4 \times 0.5 / 1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-15}} \times \frac{6}{0.18} \times (1.8 - 0.5)}$$

$$T_2 = 1.467 \times 10^{-11}$$

$$T_0 \rightarrow V_{DD/2} = T_1 + T_2 = 17.75 + 14.67$$

$$T_0 \rightarrow V_{DD/2} = 32.43 \mu s$$

34. $|V_{TH2}| < V_{out} < 0.95V_{DD}$ M₂ in Triode

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\frac{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|) t}{V_{DD} - V_{out}}}$$

$$\textcircled{a} \quad V_{out} = 0.95V_{DD}, \quad T_2 = \frac{\ln(39 - 40|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)}$$

$$= \frac{\ln(39 - 40 \times 0.5 / 1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-15}} \times \frac{6}{0.18} \times (1.8 - 0.5)}$$

$T_2 = 7.68 \times 10^{-11}$


$T_1 = 17.75 \text{ ps from previous problem}$

$T_0 \rightarrow 0.95V_{DD} = T_1 + T_2 = 17.75 + 76.8$


$T_0 \rightarrow 0.95V_{DD} = 94.55 \text{ ps}$

$(T_0 \rightarrow 0.95V_{DD}) / (T_0 \rightarrow V_{DD/2}) \approx 3$

35.

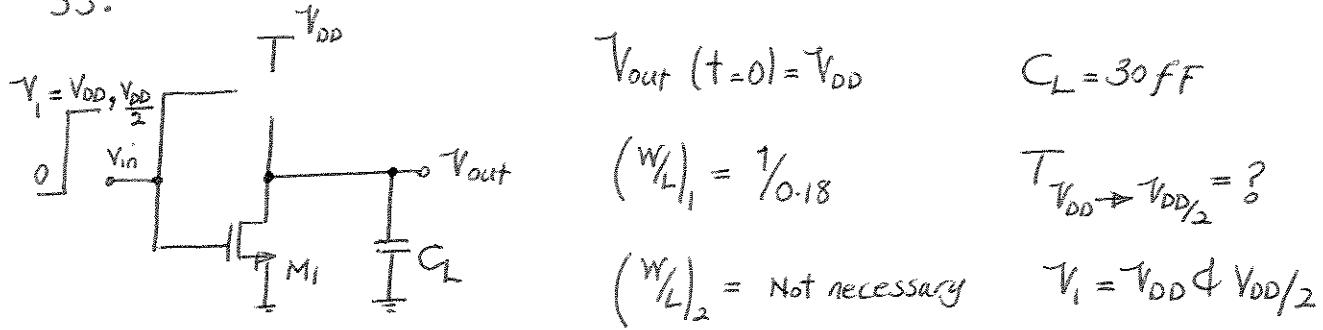
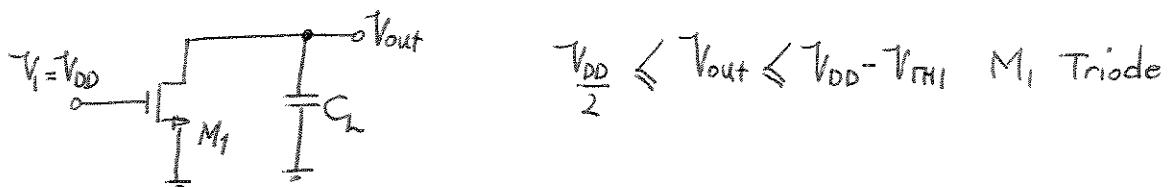
$$(a) \quad V_i = V_{DD} \quad V_{DD} - V_{TH1} \leq V_{out} \leq V_{DD} \quad M_1 \text{ saturation}$$



$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2 = 5.44 \times 10^{-4} \text{ A}$$

$$dV_{out} = -\frac{I_{D1}}{C_L} \cdot dt$$

$$V_{out}(t) - V_{DD} = -\frac{I_{D1}}{C_L} t \rightarrow V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{-I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ s}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{TH1})V_{out} - V_{out}^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - V_{TH1})V_{out} - V_{out}^2} = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 dt$$

$$\frac{1}{[2(V_{DD} - V_{TH1}) - V_{out}]V_{out}} = \frac{1}{2(V_{DD} - V_{TH1})} \left[\frac{1}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{1}{V_{out}} \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left[\frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right) dt$$

$$-\ln \left[2(V_{DD} - V_{TH1}) - V_{out} \right] + \ln V_{out} = -\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1}) t + C$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = K \cdot \exp \left[-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1}) t \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1} \quad \text{Note that time origin is assumed to be } 2 \cdot 2 \times 10^{11}$$

$$K = 1 \rightarrow$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1}) t}$$

$$V_{out} = \frac{V_{DD}}{2} \rightarrow \frac{\frac{V_{DD}}{2}}{2(V_{DD} - V_{TH1}) - \frac{V_{DD}}{2}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1}) T} \quad (V_{DD} - V_{TH1}) \rightarrow V_{DD}/2$$


$$T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2} = \frac{\ln \left(3 - \frac{2V_{TH1}}{V_{DD}} \right)}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1})}$$

$$= \frac{\ln (3 - 4 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} \times (1.8 - 0.4)} = 2.88 \times 10^{-11} \text{ s}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} + T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = 5 \times 10^{-11} = 50.86 \text{ ps}$$

$$(b) V_i = V_{DD}/2$$

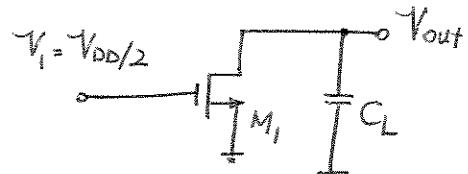

$$V_{DD}/2 - V_{TH1} < V_{out} < V_{DD} \quad M_1 \text{ in saturation}$$

$$V_{DD}/2 < V_{out} < V_{DD} \quad M_1 \text{ in Saturation}$$


$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left(V_{DD}/2 - V_{TH1} \right)^2 = -\frac{1}{2} \times 100 \times 10 \times \frac{1}{0.18} (0.9 - 0.4)^2 = 6.949 \times 10^{-5}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD}/2 = V_{DD} - \frac{I_{D1}}{C_L} \times T \quad (V_{DD} \rightarrow V_{DD}/2) \rightarrow T_{(V_{DD} \rightarrow V_{DD}/2)} = \frac{(V_{DD}/2) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD}/2)} = 3.888 \times 10^{-10}$$

36.

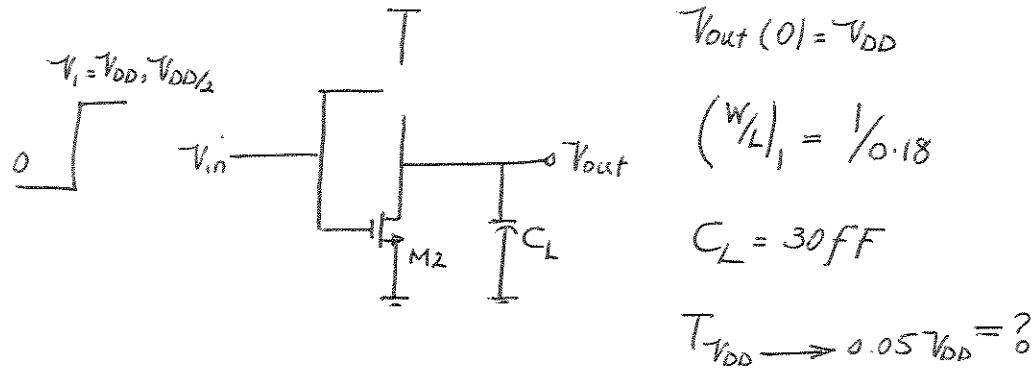

$$(a) V_i = V_{DD} \quad V_{DD} - V_{TH1} < V_{out} < V_{DD} \quad M_1 \text{ in Saturation}$$

$$0.05 V_{DD} < V_{out} < V_{DD} - V_{TH1} \quad M_1 \text{ in Triode}$$

$$C_L = \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(V_{DD} - V_{TH1}\right)^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2$$

$$= 5.44 \times 10^{-4} A$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} S$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left(\frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right) = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$$V_{out}(t=0) = V_{DD} - V_{TH1} \quad \text{Note that time origin is assumed to be } 2.2 \times 10^{-11} S$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1}) t}$$

$$V_{out} = 0.05 V_{DD}$$

$$\frac{0.05 V_{DD}}{2(V_{DD} - V_{TH1}) - 0.05 V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) / T_{(V_{DD} - V_{TH1}) \rightarrow 0.05 V_{DD}}}$$

$$\begin{aligned} T_{(V_{DD} - V_{TH1}) \rightarrow 0.05 V_{DD}} &= \frac{\ln(39 - 40 V_{TH1} / V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})} \\ &= \frac{\ln(39 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} (1.8 - 0.4)} \end{aligned}$$

$$T_{(V_{DD} - V_{TH1}) \rightarrow 0.05 V_{DD}} = 131.33 \text{ pS}$$

$$\begin{aligned} T_{(V_{DD} \rightarrow 0.05 V_{DD})} &= T_{(V_{DD} \rightarrow V_{DD} - V_{TH1})} - T_{(V_{DD} - V_{TH1} \rightarrow 0.05 V_{DD})} \\ &= 2.2 \times 10^{-11} + 1.3133 \times 10^{-10} \end{aligned}$$

$$T_{(V_{DD} \rightarrow 0.05 V_{DD})} = 153.33 \text{ pS}$$

$$(b) V_i = V_{DD/2} \quad V_{DD/2} - V_{TH1} < V_{out} < V_{DD} \quad M_1 \text{ in saturation}$$

$$0.05 V_{DD} < V_{out} < V_{DD/2} - V_{TH1} \quad M_1 \text{ in Triode}$$

$$\begin{aligned} C_L \frac{dV_{out}}{dt} = -I_{D1} &= -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD/2} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2 \\ &= 6.944 \times 10^{-5} \text{ A} \end{aligned}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD/2} - V_{THI} = V_{DD} - \frac{I_{D1}}{C_L} T_{(V_{DD} \rightarrow V_{DD/2} - V_{THI})}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{THI})} = \frac{(V_{DD/2} + V_{THI}) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{THI})} = 5.616 \times 10^{-10}$$

for $0.05V_{DD} < V_{out} < V_{DD/2} - V_{THI}$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD/2} - V_{THI}) V_{out} - V_{out}^2 \right]$$

$$\frac{V_{out}}{2(V_{DD/2} - V_{THI}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{THI}) t}$$

$$V_{out} = 0.05V_{DD} \Rightarrow \frac{\frac{0.05V_{DD}}{2(V_{DD/2} - V_{THI}) - 0.05V_{DD}}}{e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{THI}) \times T}}$$

$$\begin{aligned} T_{(V_{DD/2} - V_{THI} \rightarrow 0.05V_{DD})} &= \frac{\ln(19 - 40V_{THI}/V_{DD})}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{THI})} \\ &= \frac{\ln(19 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} (0.9 - 0.4)} \\ &= 2.5 \times 10^{-10} \end{aligned}$$


$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = T_{(V_{DD} \rightarrow V_{DD/2} - V_{THI})} + T_{(V_{DD/2} - V_{THI} \rightarrow 0.05V_{DD})}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = 5.616 \times 10^{-10} + 2.5 \times 10^{-10} = 811.5 \text{ ps}$$

By decreasing V_{in} from V_{DD} to $V_{DD}/2$, the time it takes the output to reach $0.05V_{DD}$ will be 5.3 times larger!

$$\frac{T(V_{DD} \rightarrow 0.05V_{DD}) (V_{in} = V_{DD})}{T(V_{DD} \rightarrow 0.05V_{DD}) (V_{in} = V_{DD}/2)} = \frac{811.5 \mu}{153.33 \mu} \approx 5.3$$

37.

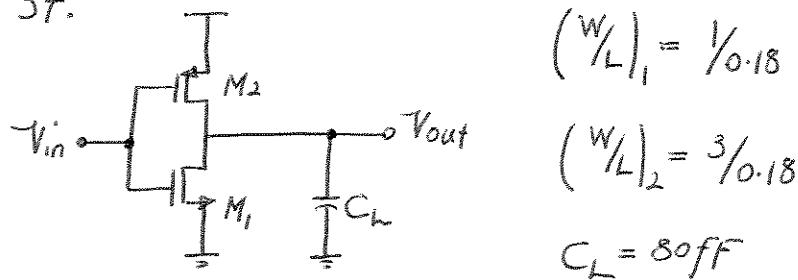

$$(W/L)_1 = 1/0.18$$

$$(W/L)_2 = 3/0.18$$

$$C_L = 80 \text{ fF}$$

$$T_{PHL}, T_{PLH} = ?$$

To calculate T_{PLH}

$$0 < V_{out} < |V_{TH2}| \quad M_2 \text{ in Saturation}$$

$$|V_{TH2}| < V_{out} < V_{DD}/2 \quad M_2 \text{ in Triode}$$

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$\begin{aligned} V_{out}(t) &= \frac{|I_{D2}|}{C_L} t \\ &= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2 t. \end{aligned}$$

$$V_{out}(T_{PLH1}) = |V_{TH2}|$$

$$T_{PLH1} = \frac{|V_{TH2}| \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2}.$$

for M_2 operating in Triode region

$$C_L \frac{dV_{out}}{dt} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 dt.$$

Defining $V_{DD} - V_{out} = u$ and noting that $\int \frac{du}{au-u^2} = \frac{1}{a} \ln \frac{u}{a-u}$,

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \quad \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 T_{PLH2} \\ V_{out} = |V_{TH2}| \end{array} \right.$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)} \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{ALH} = T_{PLH1} + T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$T_{PLH} = \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} (1.8 - 0.5)} \left[\frac{2 \times 0.5}{1.8 - 0.5} + \ln \left(3 - 4 \frac{0.5}{1.8} \right) \right]$$

$$T_{PLH} = 1.0377 \times 10^{-10}$$

To calculate T_{PHL} $V_{DD} - V_{TH1} < V_{out} < V_{DD}$ M₁ in Saturation

$V_{DD}/2 < V_{out} < V_{DD} - V_{TH1}$ M₁ in Triode

$$T_{PHL1} = \frac{-\Delta V_{out} \times C_L}{I_{D1}} = \frac{V_{TH1} \times C_L}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})^2}$$

after this point in time.

$$C_L \frac{dV_{out}}{dt} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1}$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ = -\frac{1}{2} \mu_n \frac{C_{ox}}{L} \left(\frac{W}{L} \right) T_{HL2} \\ V_{out} = V_{DD} - V_{TH1} \end{array} \right.$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1})} \times \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right) (V_{DD} - V_{TH1})} \times \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$T_{PHL} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)} \times \left[\frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \frac{0.4}{1.8} \right) \right]$$

$$T_{PHL} = 1.3563 \times 10^{-10}$$

$$38. \quad V_{DD} = 1.8 + 1.8 \times 0.1 = 1.98$$

$$\begin{aligned} T_{PLH} &= \frac{C_L}{\mu_n C_o x \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right] \\ &= \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} \times (1.98 - 0.5)} \times \left[\frac{2 \times 0.5}{1.98 - 0.5} + \ln \left(3 - 4 \times \frac{0.5}{1.98} \right) \right] \\ T_{PLH} &= 8.846 \times 10^{-11} \end{aligned}$$

$$\begin{aligned} \text{Decrease in } T_{PLH} &= \left| \frac{8.846 \times 10^{-11} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100 \\ &= 14.75\% \end{aligned}$$

$$\begin{aligned} T_{PHL} &= \frac{C_L}{\mu_n C_o x \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right] \\ &= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (1.98 - 0.4)} \left[\frac{2 \times 0.4}{1.98 - 0.4} + \ln \left(3 - 4 \frac{0.4}{1.98} \right) \right] \end{aligned}$$

$$T_{PHL} = 1.1767 \times 10^{-10}$$

$$\begin{aligned} \text{Decrease in } T_{PHL} &= \left| \frac{1.1767 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100 \\ &= 13.24\% \end{aligned}$$

$$39. \quad V_{DD} = 0.9 \text{ V}$$

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$\begin{aligned} T_{PLH} &= \frac{\Delta V_{out} \times C_L}{I_{D2}} = \frac{(V_{DD}/2) \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2} \\ &= \frac{0.45 \times 80 \times 10^{-15}}{\frac{1}{2} \times 50 \times 10^{-6} \times \frac{3}{0.18} \times (0.9 - 0.5)^2} \end{aligned}$$

$$T_{PLH} = 5.4 \times 10^{-10} = 540 \text{ ps}$$

$$\begin{aligned} T_{PHL} &= \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right] \\ &= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (0.9 - 0.1)} \times \left[\frac{2 \times 0.4}{0.9 - 0.4} + \ln \left(3 - 4 \frac{0.4}{0.9} \right) \right] \end{aligned}$$

$$T_{PHL} = 5.186 \times 10^{-10} = 518.6 \text{ ps}$$

$$\begin{aligned} \text{Increase in } T_{PLH} &= \left| \frac{5.4 \times 10^{-10} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100 \\ &= 420.38 \% \end{aligned}$$

$$\begin{aligned} \text{Increase in } T_{PHL} &= \left| \frac{5.186 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100 \\ &= 282.36 \% \end{aligned}$$

$$40. \quad T_{PLH} = T_{PHL} = 80 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1, \quad \left(\frac{W}{L}\right)_2 = ?$$

$$T_{PLH} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \times (1.8 - 0.5) \times \left(\frac{W}{L}\right)_2} \times \left[\frac{2 \times 0.5}{1.8 - 0.5} + \ln \left(3 - 4 \times \frac{0.5}{1.8} \right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{2.4}{0.18}}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \times (1.8 - 0.4) \times \left(\frac{W}{L}\right)_1} \times \left[\frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \times \frac{0.4}{1.8} \right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{1}{0.18}}$$

A1.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L} \right) \left(V_{DD} - V_{THI} \right)} \left[\frac{2V_{THI}}{V_{DD} - V_{THI}} + \ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right) \right]$$

$$V_{THI} = 0.4$$

$$\frac{2V_{THI}}{V_{DD} - V_{THI}} = \ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right) \rightarrow V_{DD} = V_{THI} \left[1 + \frac{2}{\ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right)} \right]$$

$$V_{THI} = 0.4 \rightarrow \boxed{V_{DD} = 1.57}$$

$$\frac{2V_{THI}}{V_{DD} - V_{THI}} = 0.1 \times \ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right) \rightarrow V_{DD} = V_{THI} \left[1 + \frac{20}{\ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right)} \right]$$

$$V_{THI} = 0.4 \rightarrow \boxed{V_{DD} = 8.16}$$

$$42. \quad \left(\frac{W}{L}\right)_1 = 1/0.18 \quad T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$T_{PHL} = 100 \text{ pS}$$

$$C_L = 80 \text{ fF}$$

$$V_{DD} = ?$$

$$100 \times 10^{-12} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (V_{DD} - 0.4)} \times \left[\frac{2 \times 0.4}{V_{DD} - 0.4} + \ln \left(3 - 4 \frac{0.4}{V_{DD}} \right) \right]$$

$$V_{DD} = 0.4 + 1.44 \left[\frac{0.8}{V_{DD} - 0.4} + \ln \left(3 - \frac{1.6}{V_{DD}} \right) \right]$$

$V_{DD} = 2.22$

$$43. \quad T_{DHL} = 120 \text{ ps} \quad (W/L)_1 = ?$$

$$C_L = 90 \text{ fF} \quad V_{TH1} = ?$$

$$V_{DD} = 1.8$$

$$T_{DHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$V_{DD} = 1.5 \text{ V}$$

$$C_L = 90 \text{ fF}$$

$$120 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.8 - V_{TH1})} \times \left[\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.8} \right) \right] \quad (1)$$

$$160 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.5 - V_{TH1})} \times \left[\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right) \right] \quad (2)$$

Dividing Equations (1) and (2) yields :

$$0.75 = \frac{\frac{1.5 - V_{TH1}}{1.8 - V_{TH1}} \times \frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.8} \right)}{\frac{1.5 - V_{TH1}}{1.5 - V_{TH1}} \times \frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right)}$$

$$-V_{TH1} = 1.8 - \left(\frac{1.5 - V_{TH1}}{0.75} \right) \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.8} \right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right)}$$

This equation does not lead to a real value for V_{TH1} so we use another derivation

$$-V_{TH1} = 0.45 \times \left\{ 3 - e^{\left[0.75 \frac{1.8 - V_{TH1}}{1.5 - V_{TH1}} \times \left[\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{1.5} \right) \right] - \frac{2V_{TH1}}{1.8 - V_{TH1}} \right]} \right\}$$

$$V_{TH1} = 0.39$$

$$\left(\frac{W}{L}\right)_1 = \frac{1.26}{0.18}$$


44.

$$T_{PHL} = \frac{C_L}{\mu_n C_o x \left(\frac{W}{L} \right) \left(V_{DD} - V_{THI} \right)} \left[\frac{2V_{THI}}{V_{DD} - V_{THI}} + \ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right) \right]$$

$\ln \left(3 - 4 \frac{V_{THI}}{V_{DD}} \right)$ is meaningless if $V_{DD} < 4V_{THI}/3$.

Let's consider the case where $V_{DD} = \frac{4}{3}V_{THI}$; then, T_{PHL} is the time it takes for the output to drop from $V_{DD} = \frac{4}{3}V_{THI}$ to $\frac{V_{DD}}{2} = \frac{2}{3}V_{THI}$. However, $(V_{in} = V_{DD} = \frac{4}{3}V_{THI}) - (V_{out} = \frac{2}{3}V_{THI}) = \frac{2}{3}V_{THI} < V_{THI}$. In other words, M_1 never enters the triode region in the region where T_{PHL} is calculated. The logarithmic term is derived from equation in which M_1 was assumed to be in Triode region. Therefore the logarithmic term is meaningless for $V_{DD} < \frac{4}{3}V_{THI}$.

45.

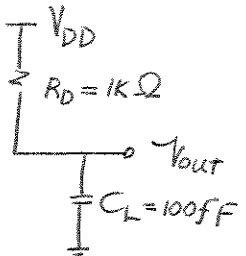

$$V_{R_D} = (V_{DD} - V_{out})$$

$$I_{R_D} = C_L \frac{dV_{out}}{dt}$$

$$P_{R_D}(t) = V_{R_D} \cdot I_{R_D} = C_L (V_{DD} - V_{out}) \frac{dV_{out}}{dt}$$

$$\begin{aligned} E_{R_D} &= \int_{t=0}^{\infty} P_{R_D}(t) dt = \int_{V_{out}=0}^{V_{DD}} (V_{DD} - V_{out}) dV_{out} = \frac{1}{2} C_L V_{DD}^2 \\ &= \frac{1}{2} \times 100 \times 10^{-15} \times (1.8)^2 \\ \boxed{E_{R_D} = 0.162 \text{ pJ}} \end{aligned}$$

46. 10^6 Gates

$$f = 2 \text{ GHz}$$

20% of gates switch in every clock cycle

$C_L = 20 \text{ fF}$ for each gate

$$P_{av} = ?$$

$$P_{av, \text{gate}} = f_{in} C_L V_{DD}^2$$

$$P_{av, \text{total}} = 0.2 \times 10^6 \times f_{in} C_L V_{DD}^2$$

$$= 0.2 \times 10 \times 2 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$\boxed{P_{av, \text{total}} = 25.92 \text{ W}}$$

$$47. f = 2 \text{ GHz}$$

5×10^6 Transistors with $W = 1 \mu\text{m}$, $L = 0.18 \mu\text{m}$, $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$

$$C_{gate} = WL C_{ox}$$

$$C_{Load} = 5 \times 10^6 C_{gate}$$

$$= 5 \times 10^6 \times WL C_{ox}$$

$$= 5 \times 10^6 \times 1 \mu\text{m} \times 0.18 \mu\text{m} \times 10 \text{ fF}/\mu\text{m}^2$$

$$C_{Load} = 9 \text{ pF}$$

$$P_{av} = f_L C_L V_{DD}^2$$

$$= 2 \times 10^9 \times 9 \times 10^{-9} \times (1.8)^2$$

$$P_{av} = 58.32 \text{ W}$$

48.

$$V_{DD} = V_{DD} + 0.1 \quad V_{DD} = 1.98$$

$$(W/L)_1 = 2/0.18$$

$$(W/L)_2 = 4/0.18$$

$$\frac{I_{Peak}}{V_{DD}=1.8} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left(\frac{V_{DD} - V_{TH}}{2} \right)^2 \left(1 + \lambda_1 \frac{V_{DD}}{2} \right)$$

$$= \frac{1}{2} \times 100 \times 10 \times \left(\frac{2}{0.18} \right) \left(0.9 - 0.4 \right)^2$$

$$\frac{I_{Peak}}{V_{DD}=1.8} = 1.388 \times 10^{-4}$$


$$\frac{I_{Peak}}{V_{DD}=1.98} = \frac{1}{2} \times 100 \times 10 \times \left(\frac{2}{0.18} \right) \left(0.99 - 0.4 \right)^2$$

$$\frac{I_{Peak}}{V_{DD}=1.98} = 1.9338 \times 10^{-4}$$

$$\text{Change in Crowbar Current} = \frac{1.9338 \times 10^{-4} - 1.388 \times 10^{-4}}{1.388 \times 10^{-4}}$$

$$\boxed{\text{Change in crowbar current} = 39.24\%}$$

49.

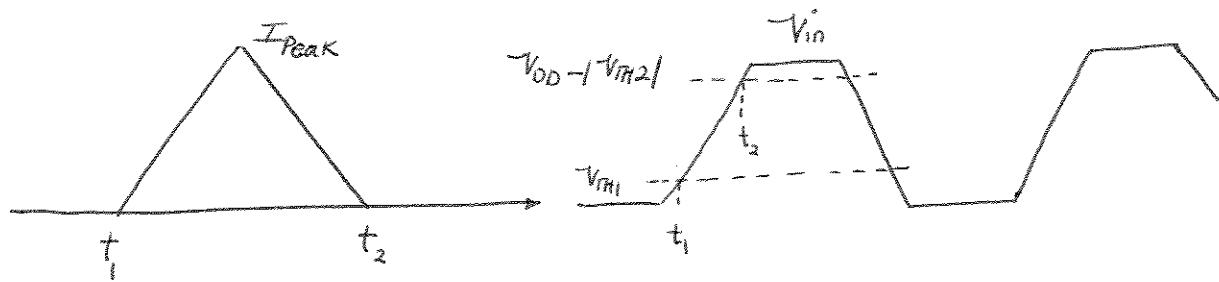

Total Energy drawn from V_{DD} during the interval $[t_1, t_2]$ is:

$$E = V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

In a period the total energy is:

$$E_{tot} = 2 \times V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

$$P_{av} = V_{DD} I_{Peak} (t_2 - t_1) f_i$$

$$\text{Slope of input voltage} = \frac{0.9V_{DD} - 0.1V_{DD}}{t_r} = \frac{0.8V_{DD}}{t_r}$$


$$(t_2 - t_1) = \frac{(V_{DD} - V_{TH1} - |V_{TH2}|)}{0.8V_{DD}} \times t_r$$

$$P_{av} = V_{DD} \times \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left(\frac{V_{DD}}{2} - V_{TH1} \right)^2 \times \frac{(V_{DD} - V_{TH1} - |V_{TH2}|)}{0.8V_{DD}} t_r \times f_i$$

$$P_{av} = \frac{1}{1.6} \mu_n C_{ox} \left(\frac{W}{L} \right) \left(\frac{V_{DD}}{2} - V_{TH1} \right)^2 (V_{DD} - V_{TH1} - |V_{TH2}|) f_i t_r$$

$$P_{av} = 1.4 \times 10^{-5} \left(\frac{W}{L} \right) \times t_r \times f_i$$


50.

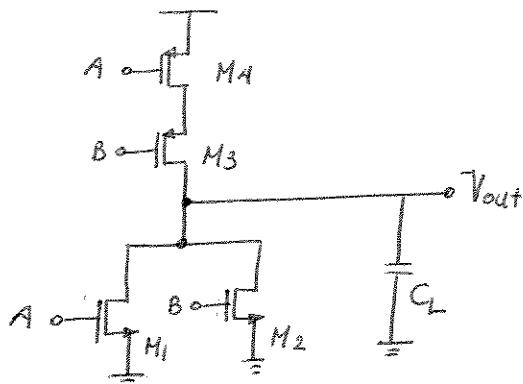

$$C_L = 20 \text{ fF}$$

$$f_i = 500 \text{ MHz}$$



$$P_{av} = ?$$

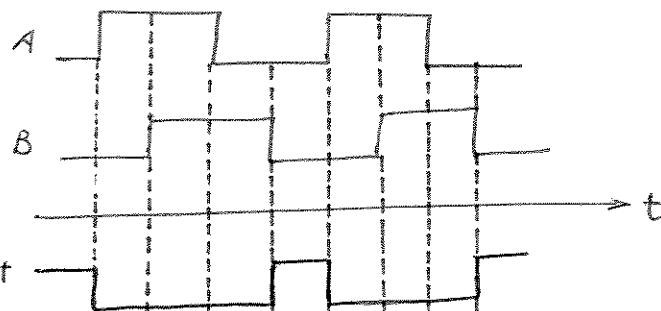

$$\begin{aligned} P_{av} &= f_i n C_L V_{DD}^2 \\ &= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2 \end{aligned}$$

$$\boxed{P_{av} = 3.24 \times 10^{-5} \text{ W}}$$


51.

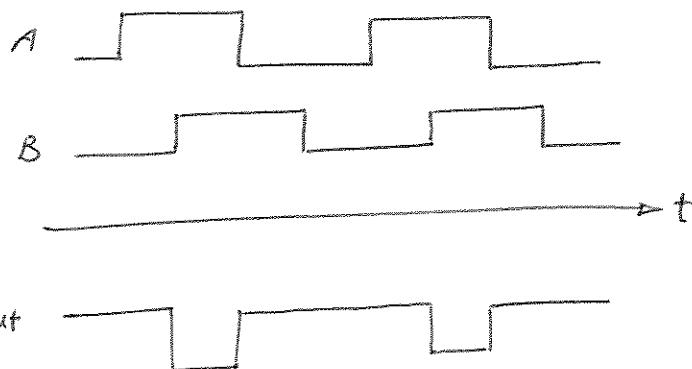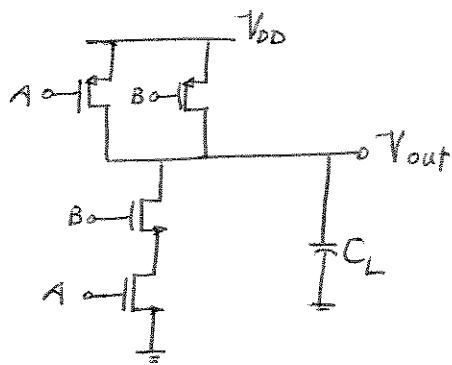


$$P_{av} = f_{in} C_L V_{DD}^2$$
$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$


52.

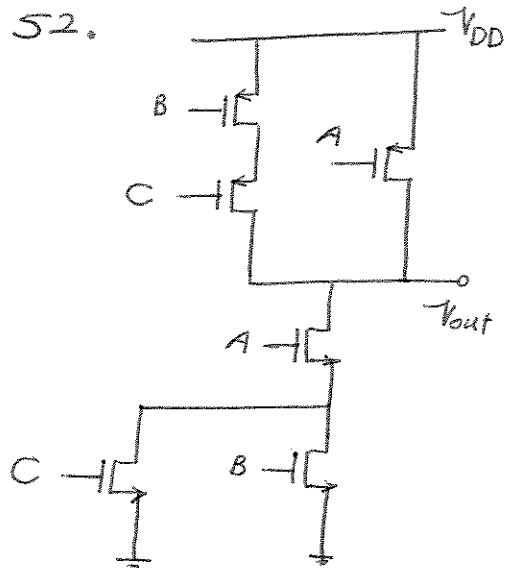


$$V_{out} = \overline{(B+C)A}$$

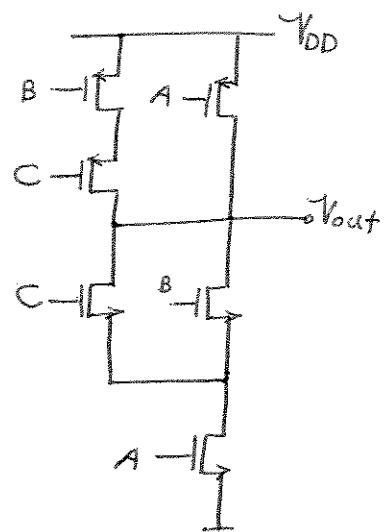


$$V_{out} = \overline{(B+C).A}$$

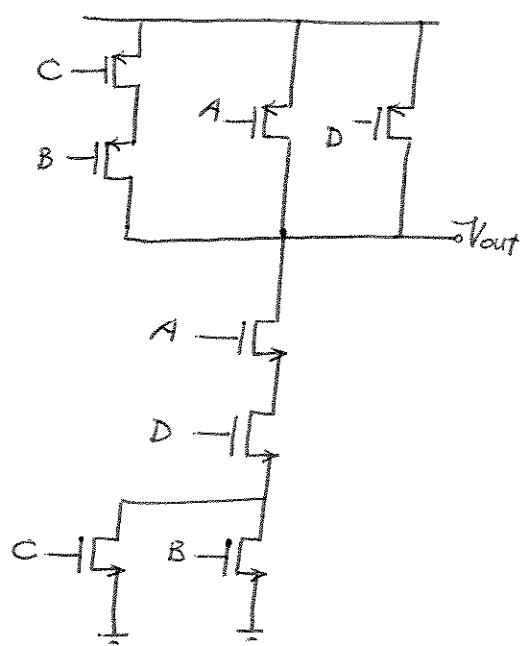

$$V_{out} = \overline{(B+C)D.A}$$

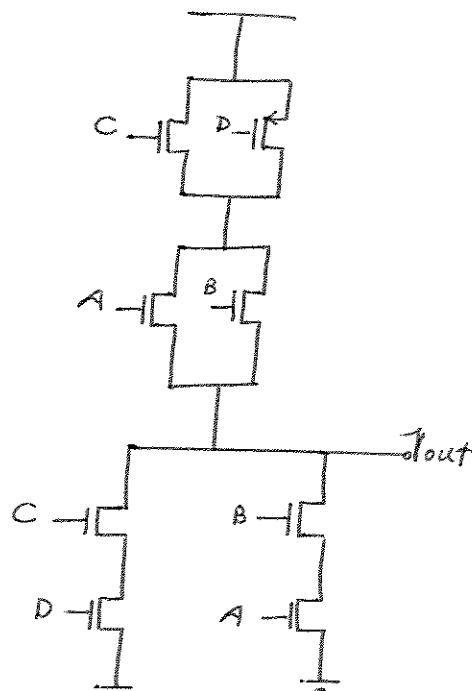


$$V_{out} = \overline{A.B + C.D}$$

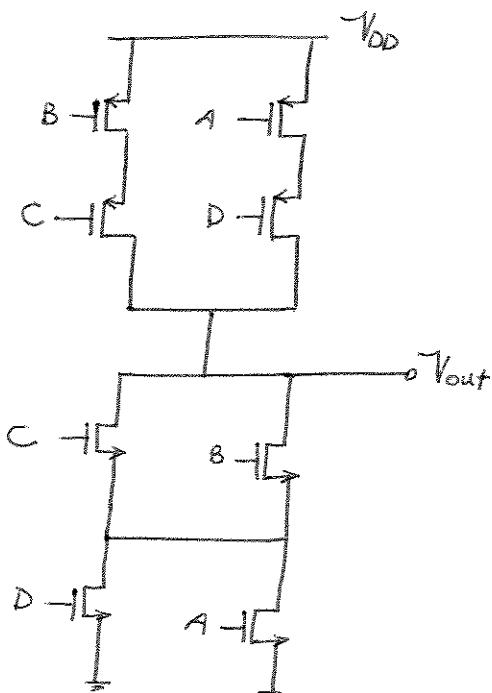

$$V_{out} = \overline{(A+D) \cdot (B+C)}$$

53.

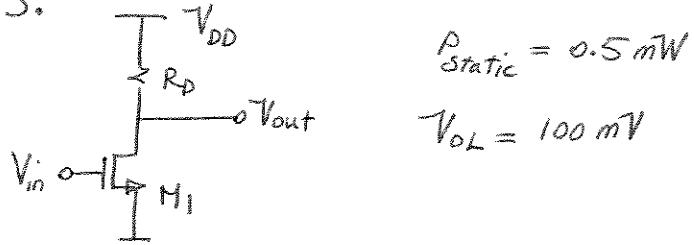

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{(1.8 - 0.1)^2}{R_D} + 0.1 \times \frac{1.8 - 0.1}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{1}{R_D} \times 3.06 = 0.5 \times 10^{-3}$$


$$R_D = 6120 \Omega$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{DD} - V_{TH1}) / V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 \times \left[2(1.8 - 0.1) / 0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{6120}$$

$$\left(\frac{W}{L} \right)_1 = \frac{3.7}{0.18}$$

54.

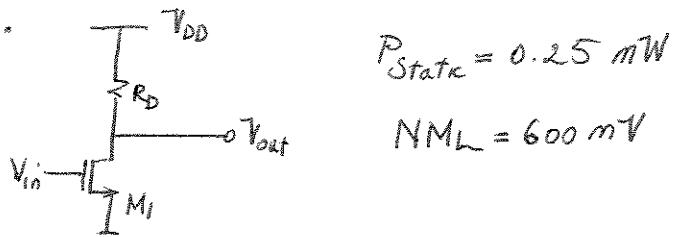

$$P_{\text{Static}} = 0.25 \text{ mW}$$

$$NML = 600 \text{ mV}$$

$$\text{Small Signal gain} = -g_m R_D$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{TH})$$

$$\mu_n C_{ox} \frac{W}{L} (V_{IL} - V_{TH}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right) R_D} + V_{TH}$$

$$NML = V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right) R_D} + V_{TH}$$

$$\frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right) R_D} = (NML - V_{TH}) \rightarrow \left(\frac{W}{L} \right) R_D = \frac{1}{\mu_n C_{ox} (NML - V_{TH})}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \mu_n C_{ox} \frac{1}{\mu_n C_{ox} (NML - V_{TH})} \times \left[2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = (V_{DD} - V_{OL})$$

$$2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 = 2(NML - V_{TH}) (V_{DD} - V_{OL})$$

$$-V_{OL}^2 - 2(V_{DD} - V_{TH}) V_{OL} - 2(NML - V_{TH}) V_{OL} + 2(NML - V_{TH}) V_{DD} = 0$$

$$-V_{OL}^2 - 2(V_{DD} + NML - 2V_{TH}) V_{OL} + 2(NML - V_{TH}) V_{DD} = 0$$

$$V_{OL}^2 - 3.2 V_{OL} + 0.72 = 0$$

$$V_{OL} = 0.2435$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.25 \times 10^{-3}$$

$$\frac{(1.8 - 0.24)^2 + 0.24 \times (1.8 - 0.24)}{R_D} = 0.25 \times 10^{-3}$$


$$R_D = 11206.55 \Omega$$

$$\left(\frac{W}{L}\right) = \frac{1}{\mu_n C_{ox} (N_{ML} - V_{THI}) R_D}$$

$$\left(\frac{W}{L}\right) = \frac{0.8}{0.18}$$

$$\left(\frac{W}{L}\right) = \frac{1}{100 \times 10^{-6} (0.6 - 0.4) 11206.55}$$

55.

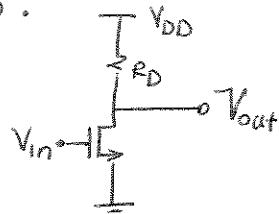

$$V_{OL} = 100mV \quad P_{av} = 0.25mW$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + \frac{V_{OL}(V_{DD} - V_{OL})}{R_D} = P_{av}$$

$$\frac{(1.8 - 0.1)^2 + 0.1 \times (1.8 - 0.1)}{0.25 \times 10^{-3}} = R_D$$


$$R_D = 12240$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) \left[2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right) \times \left[2(1.8 - 0.4) \times 0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{12240}$$

$$\left(\frac{W}{L} \right) = \frac{1.85}{0.18}$$

56.

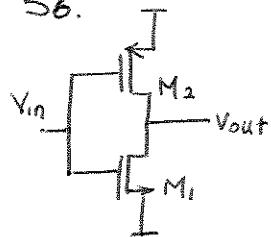

$$V_{in} = V_{out} = 0.8 \text{ V}, I_{D1} = I_{D2} = 0.5 \text{ mA}$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$\lambda_p = 0.2 \text{ V}^{-1}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_n V_{out}) = I_{D1}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L} \right)_1 (0.8 - 0.4)^2 (1 + 0.1 \times 0.8) = 0.5 \times 10^{-3}$$


$$\boxed{\left(\frac{W}{L} \right)_1 = \frac{10.4}{0.18}}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_p (V_{DD} - V_{out})] = I_{D2}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L} \right)_2 (1.8 - 0.8 - 0.5)^2 [1 + 0.2 \times (1.8 - 0.8)] = 0.5 \times 10^{-3}$$

$$\boxed{\left(\frac{W}{L} \right)_2 = \frac{12}{0.18}}$$

57.

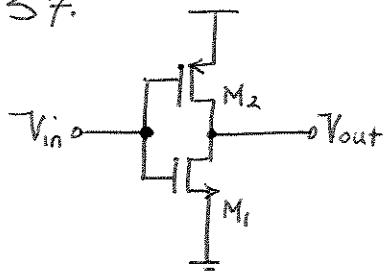

$$NM_L = NM_H = 0.7 \text{ V}$$

NM_L : M_1 in Saturation and M_2 in triode

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 [2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2] \quad (1)$$

Differentiating both sides with respect to V_{in}

$$2\mu_n \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1}) = \mu_p \left(\frac{W}{L} \right)_2 [-2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}}] \quad (1)$$

$$(a) \quad V_{in} = V_{IL} \quad \frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\mu_n \left(\frac{W}{L} \right)_1 (V_{IL} - V_{TH1}) = \mu_p \left(\frac{W}{L} \right)_2 (2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD}) \quad (2)$$

Obtaining V_{OH} from (2), substituting in (1), we arrive at

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L} \right)_1}{\mu_p \left(\frac{W}{L} \right)_2}$$

NM_H , M_1 in triode and M_2 in Saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 \left[2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

Differentiating both sides with respect to V_{in} :

$$\mu_n \left(\frac{W}{L} \right)_1 \left[2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 2\mu_p \left(\frac{W}{L} \right)_2 \times$$

Assuming $\frac{\partial V_{out}}{\partial V_{in}} = -1$, $V_{in} = V_{IH}$, and $V_{out} = V_{OL}$ obtaining $(V_{in} - V_{DD} - |V_{TH2}|)$

$$V_{IH} = \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$V_{IL} = NM_L = 0.7$$

$$V_{IH} = V_{DD} - NM_H = 1.8 - 0.7 = 1.01$$

$$0.7 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$0.7(a-1) = \frac{1.8 - \sqrt{a}}{\sqrt{a+3}} - \frac{1.3 - 0.4a}{1}$$

$$0.7a - 0.7 + 1.3 - 0.4a = \sqrt{\frac{a}{a+3}} \times 1.8$$

$$\frac{0.6 + 0.3a}{1.8} = \sqrt{\frac{a}{a+3}} \rightarrow a^3 + 7a^2 - 20a + 12 = 0$$

$$a = \begin{cases} -9.3 \\ 1.3 \\ 1 \end{cases} \rightarrow \boxed{a = 1.3}$$

$$1.1 = \frac{2a(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{1+3a}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$1.1(a-1) = \frac{1.8a}{\sqrt{1+3a}} - 1.3 + 0.4a$$

$$1.1a - 1.1 + 1.3 - 0.4a = \frac{1.8a}{\sqrt{1+3a}}$$

$$0.2 + 0.7a = \frac{1.8a}{\sqrt{1+3a}}$$


$$147a^3 - 191a^2 + 40a + 4 = 0 \rightarrow \begin{cases} a_1 = 1 \\ a_2 = 0.37 \\ a_3 = -0.073 \end{cases} \rightarrow \boxed{a = 0.37}$$

No it is not possible to design a CMOS inverter with $NM_L = NM_H = 0.7$.

The reason is that each value of $a = \frac{\mu_n C_{ox}(W/L)_1}{\mu_p C_{ox}(W/L)_2}$ specifies a unique set of noise margins (NM_L, NM_H).

Remember, the relative strength of NMOS and PMOS determines the noise margins interdependently.

58.

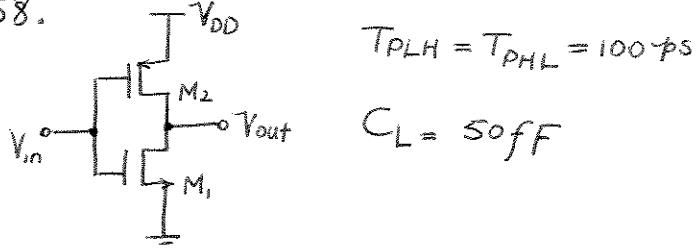

$$T_{PLH} = T_{PHL} = 100 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

 T_{PLH}

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$\begin{aligned} V_{out}(t) &= \frac{|I_{D2}|}{C_L} + \\ &= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2 t. \end{aligned}$$

$$T_{PLH1} = \frac{2 |V_{TH2}| / C_L}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)^2}.$$

$$|I_{D2}| = C_L \frac{dV_{out}}{dt}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 \left[2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] = C_L \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 dt$$

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ V_{out} = |V_{TH2}| \end{array} \right. = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L} \right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)} \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2}$$

$$= \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[\frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left(3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$100 \times 10 = \frac{\frac{-12}{50 \times 10}}{\frac{-6}{50 \times 10} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)} \left[\frac{2 \times 0.5}{1.8 - 0.5} + \ln \left(3 - 4 \frac{0.5}{1.8} \right) \right]$$

$$\left(\frac{W}{L}\right)_2 = \frac{1.9}{0.18}$$

$$T_{PHL}$$

$$T_{PHL1} = \frac{2V_{TH1}C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right] = -C_L \frac{dV_{out}}{dt}$$

$$\frac{-1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \quad \begin{cases} V_{out} = V_{DD}/2 \\ V_{out} = V_{DD} - V_{TH1} \end{cases} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 T_{PHL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[\frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$100 \times 10 = \frac{\frac{-12}{50 \times 10}}{\frac{-6}{100 \times 10} \times \left(\frac{W}{L}\right)_1 \times (1.8 - 0.4)} \times \left[\frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \times \frac{0.4}{1.8} \right) \right], \quad \boxed{\left(\frac{W}{L}\right)_1 = \frac{0.85}{0.18}}$$